Voltmeters are always useful as far as anybody interested in electronics is concerned. Junior Computer owners can use this straightforward circuit and program to convert their computer into an excellent digital voltmeter.

The basis of the circuit is an A/D converter from Intersil. This IC has binary outputs and will convert the input signal

plete voltmeter circuit for a 3% digit display including automatic polarity indication. This means the whole circuit can be very straightforward.

Figure 1 shows the circuit diagram. The voltmeter IC contains a 12 bit A/D converter with tri-state outputs. The outputs B1...B8 are displayed in two bytes. Which byte is displayed depends

using the Junior Computer as a voltmeter

With the addition of a small circuit and the aid of the accompanying program the Junior Computer can be used as a digital voltmeter . . . and a good one at that! The voltmeter has 3¾ digits and an automatic polarity indicator, even though the program is less than 180 bytes long.

level into the BCD code. Since the IC has tri-state outputs, it is suitable for use with microprocessors.

The circuit

The Intersil ICL 7109 contains a com-

on the address decoder IC2. The low order byte contains the eight least significant bits and the high order byte the four most significant bits plus an overflow bit and a polarity bit.

Using the given specifications, the

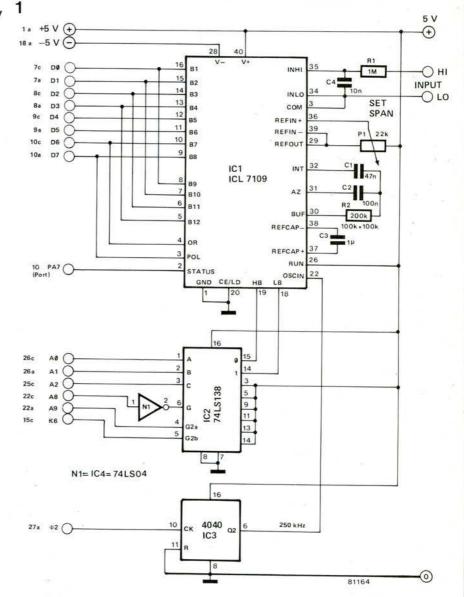


Figure 1. The digital voltmeter circuit diagram which enables the Junior Computer to measure DC voltages. IC1 takes care of the whole process, converting an analogue input signal into a 12 bit code for the computer.

G. Sullivan

input voltage for 'full scale deflection' will be 4.096 V. The conversion speed is about 30 per second. The input range can be varied by changing the value of R2 and by modifying the reference voltage which is set by P1. Thus,

$$R2 = \frac{Ufull \text{ scale}}{20 \mu A} \text{ and}$$

$$Ufull \text{ scale} = 2 \cdot U_{\text{ref}}.$$

The value of C1 and C2 is determined by the oscillator frequency used, where

C1 =
$$\frac{2048 \cdot \text{period} \cdot 20 \,\mu\text{A}}{3.5 \,\text{V}}$$

and C2 = 2 · C1.

The 250 kHz frequency that is used for the converter is derived from the microprocessor clock. For this IC3 is connected as a divide-by-four. If required, the converter may be run at a different frequency by choosing a different output of IC3. This will also alter the number of conversions per second. Because of the converter's high input impedance, input attenuators can be included fairly easily to provide several voltage ranges.

The program

The program which enables the JC to be used as a digital voltmeter is shown in table 1. This will read in the two bytes produced by the converter, after which a binary-to-decimal conversion takes place and the result is then shown on the display. In the case of a negative input signal the status of the polarity flag is detected and a minus sign is shown on the display. If the maximum input voltage of the converter is exceeded, the display will indicate OL (overload) together with the polarity.

In the circuit diagram in figure 1 the converter is connected in the 'free run mode'. This means it will start with the next conversion as soon as an analog-to-digital conversion has been completed. This is fine under normal circumstances, but it may prove necessary to detect the actual moment a conversion has ended and then read in the data to avoid this happening while the data is changing.

This can be done by connecting the status output of IC1 to PA7 of the port connector and by using the negative-going edge of this output to enable an interrupt (IRQ) at the end of a conversion. The interrupt routine can then read in and store the two bytes before the following conversion comes to an end. An example of this interrupt routine is provided in table 2.

Once the two programs have been loaded beginning with address \$200, the

Table 1.				= 17 %	
LIHE	LOC	OBJECT	SOURCE		
0001 0002 0003 0004 0005 0006 0007 0008 0009 0010 0011 0012	0000 0000 0000 0000 0000 0000 0000 0000 0005 0005		ACUM SUM DELAY TMPX DEFINE	AL VOLTMETER FRO ATERSIL ICL 7109 R.G.SULLIVAN * = \$0000 *=*+2 *=*+1 *=*+1 *=*+1 E A/D CONVERTER. * = \$1800	
0014 0015 0016 0017 0018 0019 0020 0021 0022 0023 0024 0025	1800 1801 1802 1802 1802 1880 1881 1882 1883 1884 1884 1884		HB. LB. DEFINE PRA DDRA FRB DDRB SCANDI	# = \$1880	,HIGH NIBLE + FLAGS ,LOW BYTE ,DATA A REG. ,A DIRECTION REG. ,DATA B REG. ,B DIRECTION REG. ,DISPLAY I BYTE
0027 0028 0029 0030 0031 0032 0033 0034 0035 0036 0037 0038 0039 0041 0042	0200 0200 0200 0203 0205 0208 020B 020F 0212 0215 0217 0217 0219 0218	2C 00 18 70 06 20 24 02 4C 12 02 A2 0C A0 03 20 49 02 AD 00 18 30 07 A2 08 A0 00 20 49 02 20 73 02 4C 00 02	MAIN OL NOL	BMI NOT LDX #\$08 LDY #\$00 JSR DISTAT	TEST OVERANGE BIT
0057 0058 0059 0060 0061	023F 0241	D0 DC	LOOP	LDY ##FF INY LDA ACUM,Y JSR SCAND1 CPX ##14 BNE LOOP LDA HB BMI NXT LDX ##08 LDY ##00 JSR DISTAT INC DELAY BNE DISVLT RTS	,SET PIA TO OUTPUT ,ADDRESS OF FIRST BYTE ,GET BYTE ,LIGHT DISPLAY ,TEST IF TWO BYTES YET ,TEST POLARITY ,SHOW - IF NEG. ,DELAY ON DISPLAY
0063 0064 0065 0067 0068 0069 0072 0072 0074 0075 0076 0077 0078 0081 0082 0083 0083	0249 0248 0241 0253 0256 0258 0258 0258 0262 0264 0267 0267	89 60 92 30 14 30 80 1A 30 80 1A 30 80 1A 30 80 1A 30 82 1A 40 82 1A 50 82 1A 50 75 50 75 50 80 60 80	DLY2 ENDD CHART	BMI ENDD STA PRA STX PRB STX TMPX LDX ##FF DEX BNE DLY2 LDX TMPX	\$ 80

0272 0273 0083 กัก84 0273 0273 0085 CONVERT BINARY TO BCD 0086 MA HEXBCD LDA #\$00 0087 0275 85 DØ STA ACUM CLEAR ACCUMULATOR 85 Di 0088 STA ACUM+1 0089 18 HE 01 LDX LB 0090 F0 0B BEQ HIGH 0091 027E A0 01 LODEL LDY #\$01 CONVERT LOW BYTE 0092 TYA 8093 85 STA SUM JER 0094 0283 9E 02 ADD 0095 DEX 0096 0287 DØ F5 BNE LOOP1 0097 0289 AD 00 18 HIGH LDA HB CONVERT HI BYTE 29 F0 0098 0280 ME AND #\$0F REMOVE FLAGS 0099 028E ØD BEQ LAST 0100 0290 ÄĤ TAX 0101 0291 A9 08 LDA ##08 0102 85 D2 STA SUM 0103 HØ. 20 L00P2 LDY #\$20 0104 20 9E 02 JSR ADD 0105 029A DEX 0106 029B DØ F8 BNE LOOPS 0107 029D 60 LAST RTS 0108 HDD SED ADD 1 OR 256 TO ACUM 0109 029F LOOP3 CLC 0110 02A0 LDA SUM 65 D1 85 D1 ADC ACUM+1 STA ACUM+1 02A2 0112 02A4 0113 02A6 00 LDA #\$00 0114 65 DØ 85 DØ 02A8 ADC ACUM 0115 0266 STA ACUM 0116 02AC DEY 0117 DØ FØ 02AD BHE LOOPS 0118 02AF D8 CLD 0119 02B0 60 RTS 0120 02B1 FND

ERRORS 0000

SYMBOL TABLE

ACUM DDRB DLY2 HIGH LOOP1 NOL PRA TMPX	00D0 1A83 025D 0289 027E 0212 1A80 00D4	ADD DELAY ENDD LAST LOOP2 NOT PRB	029E 00D3 0267 029D 0295 021E 1A82	CHART DISTAT HB LB LOOP3 NXT SCAND1	026D 0249 1800 1801 029F 0244 1DCC	DDRA DISVLT HEXBOD LOOP MAIN OL SUM	1881 0224 0273 022D 0200 0208 00D2	

END OF ASSEMBLY

Table 2.

IRQ service routine:

1110	er vice routine	•	
Ø38Ø	48	INTS: PHA	; save A
Ø381	8A	TXA	; save X
Ø382	48	PHA	# 157 E38
Ø383	98	TYA	; save Y
Ø384	48	PHA	(*)
Ø385	AD 85 1A	LDA 1A 85	; reset IRQ
Ø388	AD ØØ 18	LDA 18 00	; read high byte
Ø38B	85 DØ	STA DØ	; store it
Ø38D	AD Ø1 18	LDA 18 Ø1	; read low byte
Ø39Ø	85 D1	STA D1	; store it
Ø 392	68	PLA	; restore all registers
Ø393	A8	TAY	
0394	68	PLA	
0395	AA	TAX	
Ø396	68	PLA	
Ø397	40	RTI	; return to main program
			, Is main program

IRQ vector has to be specified:

1A7E 8Ø 1A7F Ø3


Finally, the initialisation routine which is needed whether or not the interrupt routine is used:

0000 8D 86 1A STA 1A 86 0003 58 CLI 0004 4C 00 02 JMP-MAIN

Now a reference voltage is connected to the input of the meter circuit (4 V, for instance) and P1 is adjusted so that the display indicates the value of the reference voltage. In the absence of a known voltage, any DC voltage of about 4 V can be used instead and the display can be compared to that of another, accurate meter.

These instructions make sure the PIA produces a negative-going edge at PA7 and that the interrupt-disable bit is restored once the processor is reset. When this has been done and the circuit in figure 1 is connected to the Junior Computer, the program can be started at address 0000.

The Junior Computer ...

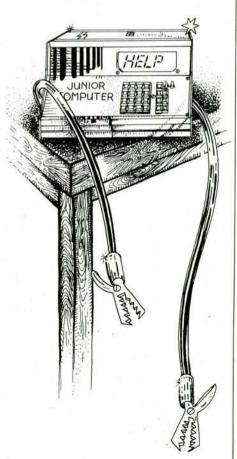

... as a voltmeter