

# A 6502 Personal System Design:

David Brader  
POB 483  
Electric City WA 99123

## Documenting Kompuutar — A Guide to the Details

*The design information included with this article, together with the excellent documentation provided by MOS Technology on the 6502 design, should be complete enough to enable the advanced experimenter to build a similar Kompuutar. The details provided here cover a basic processor, but do not include a detail design of a programmable memory board which is a necessary part of a usable system. David Brader is currently working on an 8 K dynamic memory board, with invisible refresh, to be used in Kompuutar. The details of the wiring and construction of Kompuutar are shown in the several figures, tables and photographs, as well as listing 1. As a short guide to these materials here is a detailed table of contents to the article.*

**Front Panel Assembly:** *This is the circuit with various displays and switches, which is mounted on the front panel, and talks to the front panel interface module via a multiconductor cable from P2 to J2.*

<i>Photo 1: User's view of the front panel.</i>	<i>page 95</i>
<i>Figure 1: Front panel block diagram.</i>	<i>page 104</i>
<i>Figures 1.1 to 1.8: Show circuit details.</i>	<i>pages 106 to 114</i>
<i>Photo 2: Rear of the front panel.</i>	<i>page 100</i>
<i>Figure 1.9: Physical layout drawing of front panel (same view as photo 2).</i>	<i>page 116</i>

**Front Panel Interface Module:** *This is the logical interface between the processor's backplane bus and the front panel. It is the home of address decoding and the read only memory with the front panel service programs.*

<i>Photo 2: Shows the cables from the front panel interface module to the front panel assembly (at the left).</i>	<i>page 100</i>
<i>Figures 2.1 to 2.4: Show circuit details.</i>	<i>pages 118 to 124</i>
<i>Figure 2.5: Shows the physical layout on a Vector #3677-2 prototyping board.</i>	<i>page 126</i>
<i>Table 4: Shows the wiring definitions of the J2-P2 cable from this board to the front panel assembly.</i>	<i>page 102</i>

**Central Processing Module:** *This is the heart of the Kompuutar system, a board which contains the 6502 processor, and associated buffering and clocking circuitry which defines the backplane bus structure of the system.*

<i>Photo 3: Shows the component side of the central processing module, the second card from the left.</i>	<i>page 102</i>
<i>Figure 3.1: Shows the logic diagram of the processor card.</i>	<i>page 127</i>
<i>Figure 3.2: Shows the physical layout of the processor module on a Vector #3662 prototyping card.</i>	<i>page 128</i>
<i>Table 2: Details the backplane pin definitions (P1 of each card) for the bus of Kompuutar.</i>	<i>page 98</i>

**TIM Interface Module:** *This card is provided so that the MOS Technology "Terminal Interface Monitor," or TIM program, can be used with Kompuutar.*

<i>Figure 4.1: Shows the logic diagram of the TIM Interface Module.</i>	<i>page 130</i>
<i>Figure 4.2: Shows the physical layout of the TIM module on a Vector #3662 card.</i>	<i>page 132</i>

## Miscellaneous Items:

<i>Table 5: Shows a master list of all integrated circuits, where they appear by figure, wiring, map locations for the physical layouts shown, and power wiring connections.</i>	<i>page 134</i>
<i>Table 1: Shows the allocations of memory for Kompuutar, as implemented here.</i>	<i>page 96</i>
<i>Listing 1: Shows the front panel control program which can be used to manipulate Kompuutar without any other monitor program.</i>	<i>pages 136-137</i>

# Kompuutar

 


Photo 1: The completed Kompuutar, viewed towards its front panel. The controls of the front panel are chosen with the Data General NOVA's front panel as a mental model. In addition to the binary data display, there is a 4 digit hexadecimal address display (black rectangle) and an 8 bit binary flag display. The control panel is serviced by a read only memory routine.

## Kaveat Kompuutar

*It is with some trepidation that we present the details of the Kompuutar design. The design is complete and comprehensive, but Murphy is addicted to complete and comprehensive designs. Thus we'd like readers to be aware that there is a nonzero probability that errors exist in this magazine representation of author David Brader's design. We suggest that serious homebrewers of Kompuutar treat these pages as a detailed design guide, to be used with the standard design documentation of the chips involved. But as with any road map, do not be afraid to question and verify what you see with your own knowledge and experience.*

*David Brader reports that a local friend of his has built a second Kompuutar from the same set of blueprints which were the source of the circuit in this article. The experiences of the second builder were reflected in his corrections and changes to the drawings which are part of the normal "author proof" cycle applied to articles. Based on our own experiences with microprocessors, this report from David, and a tremendous amount of "desk debugging" of the article, we believe the information presented here is complete and buildable. However we highly recommend that readers who attempt to duplicate the design have sufficient experience with digital hardware and logic so that detailed understanding of its operation is possible. This is not a novice's project.*

It all started at WESCON 1975, in San Francisco. It was there that I discovered what a "hospitality suite" is. In a hotel not far from the convention site, MOS Technology Inc had set up their WESCON hospitality suite. A hospitality suite is a bit like Las Vegas: some refreshments, a couple of elegantly decorative ladies, flashing lights and shiny gizmos, and the age old desire to persuade you and your money to part company.

I decided to stop and at least get a free drink. A man by the bar said, "Help yourself," so, being afraid of a one drink limit, I poured a double. As I left the bar area, I spotted a friend. We struck up a conversation about common friends and assignments, which lasted through half my drink and all of my clearheadedness. As our conversation ended, I noted some blinking LEDs and shiny new printed circuit boards. These boards were surrounded by several professional looking guests, giving the hardware an illusion of significance. So I went over to investigate.

I listened, wide eyed, to the saga of the MCS6502 as I slowly finished my drink. After the story ended, everyone seemed to be forming a line in a different part of the suite. Feeling part of the group now, I moved to the line. A little bit later, I remember being at the head of the line and the last thing I recall was handing two 20 dollar bills to a very pretty lady.

That evening, after sobering up, I discovered what I had done. There on my bed, stark naked, was a bright new MOS Technology Inc MCS6502 microprocessor chip and its manuals. Well, now the only



Backplane (P1) Pin Designation	Logic Diagram Mnemonics	Description	Backplane Pin Designation	Logic Diagram Mnemonics	Description
A	+5 V	voltage supply	1	GND	ground
B	IRQ 1	interrupt 1	2	IRQ 5	interrupt 5
C	A 0	address bus lines (even)	3	A 1	address bus lines (odd)
D	A 2		4	A 3	
E	A 4		5	A 5	
F	A 6		6	A 7	
H	A 8		7	A 9	
J	A 10	interrupt 2	8	A 11	interrupt 6
K	A 12		9	A 13	
L	A 14		10	A 15	
M	IRQ 2		11	IRQ 6	
N	IRQ 3	interrupt 3	12	IRQ X	any interrupt pending
P	D 0	data bus lines (even)	13	D 1	data bus lines (odd)
R	D 2		14	D 3	
S	D 4		15	D 5	
T	D 6		16	D 7	
U	SO	set overflow flag	17	SYNC	synchronize
V	PHCLK	$\Phi$ 1 clock	18	PH2CLK	$\Phi$ 2 clock
W	MASRST	master reset	19	RDY	ready
X	R/W	read and write	20	PANRST	panel reset
Y	IRQ 4	interrupt 4	21	NMI	nonmaskable interrupt
Z	GND	ground	22	+5 V	voltage supply

Table 1: Kompuutar bus list. This table gives the backplane socket pin identifications, mnemonics used in the logic diagrams, and a short description of the line's use. The pin designations are the standard ones printed on the Vector prototyping cards and embossed in the typical 44 pin sockets.

thing to do was to build a computer with the chip. After several days reading, I realized that building a computer was not going to be all that easy. I also realized that the initial \$36.75 investment was but a drop in the proverbial bucket of costs.

#### Designing the Kompuutar System

Since my \$36.75 investment was going to need considerable financial and design support, it was clear that making a project out of the computer would require planning. The first thing I had to accomplish was a specification of the features I wanted in my machine. I had had a good deal of experience with the Data General NOVA 1200 minicomputer, which led me to favor its functional front panel switch setup. With this input, I decided that the new machine would have the front panel functions of master reset, halt, program run, single instruction step, memory examine, examine the next memory location, deposit, deposit to the next memory location, load processor register, and enter data or address information from switches. I also knew that I wanted to be able to display the information on the data lines and address lines. I decided to use hexadecimal LED displays for the address bus information, but not for the data bus. My reasoning was that the address bus is always considered to be a numerical value, whereas the data bus is sometimes considered to be numeric data, but is sometimes viewed as a combination of individual bits. (If the data bus was showing hexadecimal E6 and you wanted to know if bit 5 was on or off,

you would probably have to think for a while to make sure.) Another argument in favor of discrete LED indicators for each bit is the fact that hexadecimal displays are a bit more expensive.

After reading more about the MCS6502, a trait common to the other single chip processors revealed itself. The status register, accumulator, index register X, index register Y and stack pointer register do not come out of the chip on their own sets of pins. All that information was going to be hidden from the operator (me) sitting in front of the machine. I knew I would have to design digital logic to get that information out of the chip and displayed upon some sort of front panel. I even decided to go one step further and build in the capability to set or reset the status flags from the front panel. Being able to throw a switch and set the carry flag, for example, is a very handy capability when debugging a conditional branch in some program.

I decided to use toggle switches for the 16 data inputs because the state of individual switches could then be tested in software and used to control options in a program. This complicates the entry of an address (which is displayed in hexadecimal) but gains an ability to write applications programs which can be modified by the state of these input switches.

With these considerations in mind, the front panel design was firmed up as a starting point for the processor. I then started to work on the detailed logic design of what came to be called Kompuutar in my lexicon. After a month's work, I realized that the

front panel logic was going to contain nearly 220 TTL integrated circuits if I implemented it with a conventional logic design. After that false start, I thought about a simplification made possible by a read only memory program, or "firmware" as it is sometimes called. I could replace most of the front panel logic with a program burned into a single read only memory integrated circuit. With a PROM program and 16 bytes of volatile programmable memory, the 6502 processor itself would operate the front panel of the system. The integrated circuit count for the front panel including the programmable read only memory and 16 bytes of volatile solid state memory was now reduced to just over 50 packages.

#### System Design Philosophy

During the process of designing the front panel, I worked out a total system

design philosophy which goes like this:

- There would be a central processing unit and peripherals. The peripherals would be interfaced to the processor with a minimum of hardware by using memory address interfaces wherever possible.
- The system would be modular. A common backplane would be defined. Each module would be connected to the other modules through this backplane. Each socket on the backplane would be wired pin by pin to every other socket on the backplane.
- An address allocation map for the system would be defined. This would define addresses for hardware (peripherals), firmware (read only memory programs) and main programmable memory use.

The front panel design I had already created follows the first point of this philosophy quite well. It has several separate peripherals. Some are input devices, some are output devices, and some are a combination of both functions. Each is interfaced as a memory address and operated by firmware with a minimum of supporting hardware. Details of front panel operation will be discussed a little later in this article.


The physical arrangement of the design implements the details of the second point in the philosophy. The front panel assembly is connected to the top of a Vector prototyping card which contains the programmable read only memory with the front panel servicing routines. This card in turn plugs into the backplane bus which is implemented with a Vector card cage and edge connectors. By pulling the front panel card out of the backplane, the Kompuutar system can be isolated from the front panel completely. Similarly, the rest of the Kompuutar system is fabricated on Vector 3662 cards. Each card module contains one complete section of the system. These modules include the central processing unit card with the 6502 and bus interfacing chips, and a terminal interface card. Eventually 8 K byte programmable (volatile) memory cards will be part of the system. The cage I used has room for eight memory cards for a total of 64 K bytes. Since the backplane is wired from pin to corresponding pin of each socket, the cards can be placed in any available socket in the card cage. Table 1 shows the definitions of all the bus pins. In developing the system, I used an extender card plugged into the backplane so that I could have access to the various modules with an oscilloscope probe.

The third part of the design philosophy

Address Range	Type of Hardware	Usage of Region
0000 to 3FFF	Volatile programmable memory	This is the general programmable memory region for user applications programs. Locations 0000 to 01FF are dedicated to scratch pad and stack use by the architecture of the 6502 processor.
4000 to 6FFF	Unimplemented	This region is reserved for 12 K of general user memory expansion.
7000 to 73FF	TIM read only memory	When the TIM monitor interface card is in the system, this area is reserved.
7400 to 7FFF	Unimplemented	
8000	Scratch pad memory with external visibility	Current accumulator value maintained by front panel service program
8001	Scratch pad memory with external visibility	Current X register value
8002	Scratch pad memory with external visibility	Current Y register value
8003	Scratch pad memory with external visibility	Current processor flag values
8004	Scratch pad memory	
8005	Scratch pad memory with external visibility	Current stack pointer value
8006	Scratch pad program begins here	
8007 to 8008	Scratch pad	Current address register value, displayed through locations 8014 and 8015
8009 to 800C	Scratch pad program area	
800D	Scratch pad memory with external visibility	Current data at memory location in address register locations 8007 to 8008
800E-800F	Scratch pad	
8010	Read only data input	Front panel request register (see table 3)
8011	Read only data input	Low order address and data switch register
8012	Read only data input	High order address switch register
8013	Write only display	Flag data latch and binary display
8014	Write only display	Low order address display latch
8015	Write only display	High order address display latch
801F	Idle command address	References cause processor to idle
8020 to 80FF	Peripherals	Unimplemented hardware device addresses
8100 to EFFF	Unimplemented	
F000 to FFFF	Programmable read only memory allocations for systems programs	This area is expected to be used by interrupt service routines, utility subroutines and the like, programmed into read only memory parts.
FE00 to FFFF	Read only memory	This region is allocated to the firmware which controls the front panel. The 6502's interrupt vectors are programmed into the last portion (see listing 1).

Table 2: A memory allocation map for Kompuutar. When interfacing both peripherals and programming to a single memory address space, it helps to make a memory map to keep track of allocations.

Photo 2: The reverse side of the front panel assembly for Kompuutar. The various switches, indicators and the front panel electronics board are seen in this picture. The P2-J2 cables run to the front panel interface module at right.

 

was implemented by picking address allocations. (See table 2 for a detailed list of the allocations.) I decided early in the project that 16 K bytes of memory would be a good start for general programming uses. I had to allocate this volatile user oriented programmable memory, as well as all the addresses for peripheral hardware and "firmware" read only memory programs. The address range of the 6502 is from 0 to 65,535 (0000 to FFFF in hexadecimal). Since the architecture of the chip itself uses addresses 0000 to 01FF for dedicated functions which must be in programmable memory, I assigned the 16 K byte block of main memory to the lowest part of the addressing range, from hexadecimal 0000 to 3FFF. I was interested in the possibility of occasionally using the MOS Technology TIM monitor, so I reserved locations 7000 to 73FF for use by that program's read only memory. I allocated the control panel scratch memory and peripheral ports starting at address 8000 hexadecimal, with the addresses starting at 8020 reserved for general peripheral use as I expand the system. At the end of the address range, I reserved the 4096 bytes from addresses F000 to FFFF for read only memory containing various systems routines. The high end of this range is reserved for the control panel support program and the interrupt vectors of the MOS Technology 6502 design.

## Backplane

The backplane of the card cage (see table 1) carries the address bus, the bidirectional data bus, six vectored interrupt lines, and other functional signals as detailed in table 1. All signals that pass through the backplane are interpreted to be logical 1 or "true" in a low voltage (TTL 0) state. A high voltage (TTL 1) state is interpreted as a logical 0 or "false" state. Each module which connects to the backplane uses TTL inverting buffer circuits for signals sent or received. The +5 V (VCC) and ground (GND) connections are arranged on the card edge connectors such that by plugging a module into the backplane upside down, polarity to the card will not be reversed. This simple arrangement eliminates the need for keying the cards; while it prevents physical destruction of the card due to inadvertent reversal of orientation, the system should not, of course, be expected to work with one or more cards reversed relative to the balance of the cards in the system.


The vectored interrupt lines of the backplane are defined by some logic implemented on the central processing unit card (see figures 3). This card contains logic necessary to cause hardware vectoring of interrupt levels to one of the six possible interrupt service routines. The vectoring

Table 3: Control request word layout. The control request word, located at address 8010 in memory address space, is an input to the processor with this format. It is used by the front panel service program of listing 1 to govern the operation of the panel based on settings of various switches.

Bit 7	Bit 6	Bit 5	Bit 4	Bit 3	Bit 2	Bit 1	Bit 0
Flag Select Bits			Flag Control	Control Request Functions			
0 = CARRY flag 1 = ZERO flag 2 = IRQ DIS flag 3 = DECIMAL flag 4 = BRK CMD flag 5 = Not used 6 = OVRFLW flag 7 = NEG flag			"1" = set flag "0" = reset flag	0 = Null command (pass NMI) 1 = FLAG MODIFICATION 2 = DEPOSIT NEXT 3 = DEPOSIT 4 = EXAMINE NEXT 5 = EXAMINE 6 = STEP 7 = HALT 8 = REG LOAD 9 to 15 = Unused			



Photo 3: The front side of the backplane framework with card guides. This picture shows the front panel interface module at the left, the central processor module, a gap of several card slots, then the TIM interface module's edge with cables dangling.

 

is accomplished by using the selected service routine address for the interrupt vector requested by the 6502 processor during its interrupt sequence. The service routines are assumed to reside in programmable read only memory chips located in a separate module elsewhere on the backplane bus. The processor hardware also incorporates a priority arrangement of these six interrupts. Thus when two interrupts occur simultaneously the system has no problem: the higher priority one is serviced first. This becomes important when several interrupt driven peripherals are used with the system. An automatic reset function initializes the system when power is turned on, a separate interrupt for the 6502 which is supported on the processor board.

As an alternative to the front panel logic, the memory map of table 2 shows allocations for the MOS Technology TIM monitor integrated circuit, MCS6530-004. This "Terminal Interface Monitor" allows the user

to use an ASCII serial device such as a Teletype or other terminal. In making a board to support TIM, I also included an 8 bit parallel interface to allow the possibility of using a high speed paper tape reader with Kompuutar. Details of the TIM module are shown in figures 4.

#### Front Panel Logic

Getting into more of the details of the system, I'll concentrate mainly on the place where I started my design, the front panel. The front panel logic is composed of input devices, output devices, 16 bytes of scratch pad memory, logic of the ready and nonmaskable interrupt timing, address decoders, switch debouncers, a data bus multiplexer, command encoder, line buffers and the control program in a programmable read only memory. The overall design of the front panel is found in figure 1, with details spread out in figures 1.1 thru 1.9. Photos 1 and 2 give further details.

There are four input sources of data in the front panel design. Each source is selected by the address decoding logic, which in turn allows the proper source to be input through the data bus multiplexer. The first source of input is the control request register. This source carries data from the command encoder, the flag selection switch, the flag modification switch and the register load switch. Table 3 shows the bit assignments of this source, which is located at hexadecimal address 8010 in memory address space.

The second source of input is the low

Text continued on page 112

Wire	Logic Diagram Mnemonic	Description	Wire	Logic Diagram Mnemonic	Description
1 to 4	+5 V	voltage source	21	X800X	address selection lines
5	D0	data bus lines	22	X800F	
6	D1		23	X8013	
7	D2		24	X8014	
8	D3	phase 1 clock	25	SEL 1	multiplexer select lines
9	$\Phi$ 1 CLK		26	SEL 2	
10	$\Phi$ 2 CLK		27	BSOUT	multiplexer disable
11	IROX	any interrupt pending	28	—	
12	A3	address bus line	29	X8015	address selection lines
13	D4	data bus lines	30	XFEEA	
14	D5		31	X801F	
15	D6		32	—	front panel reset ready nonmaskable interrupt ground
16	D7		33	—	
17	A2	address bus lines	34	REST	
18	A1		35	RDY	
19	A0		36	NMI	
20	R/W	read/write	37 to 40	GND	

Table 4: Wiring list for the J2-P2 cable. This cable runs from the front panel interface board in the card cage to the front panel assembly, as seen in photos 2 and 3. [In the author's version of Kompuutar, the wiring was direct without use of a plug and jack; in order to simplify nomenclature in presenting the article, we've used a numerical identification of signal paths as if a 40 wire cable and connectors had been used . . .CH/

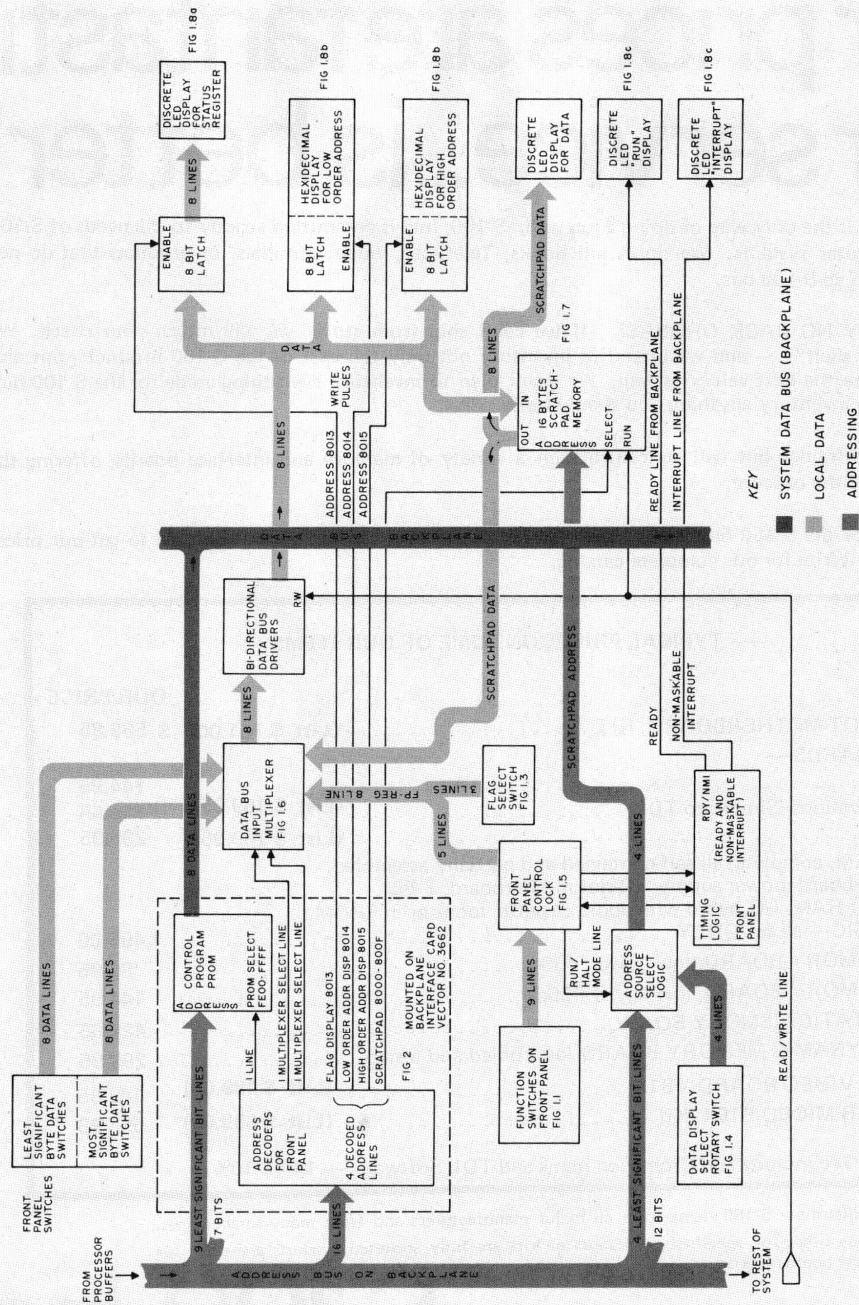


Figure 1: Block diagram of Kompuutar's front panel logic. The Kompuutar design uses a read only memory program to manipulate the contents of memory interactively using function switch inputs and solid state display outputs. This diagram serves as a functional road map to the various components of the display and its interface board.

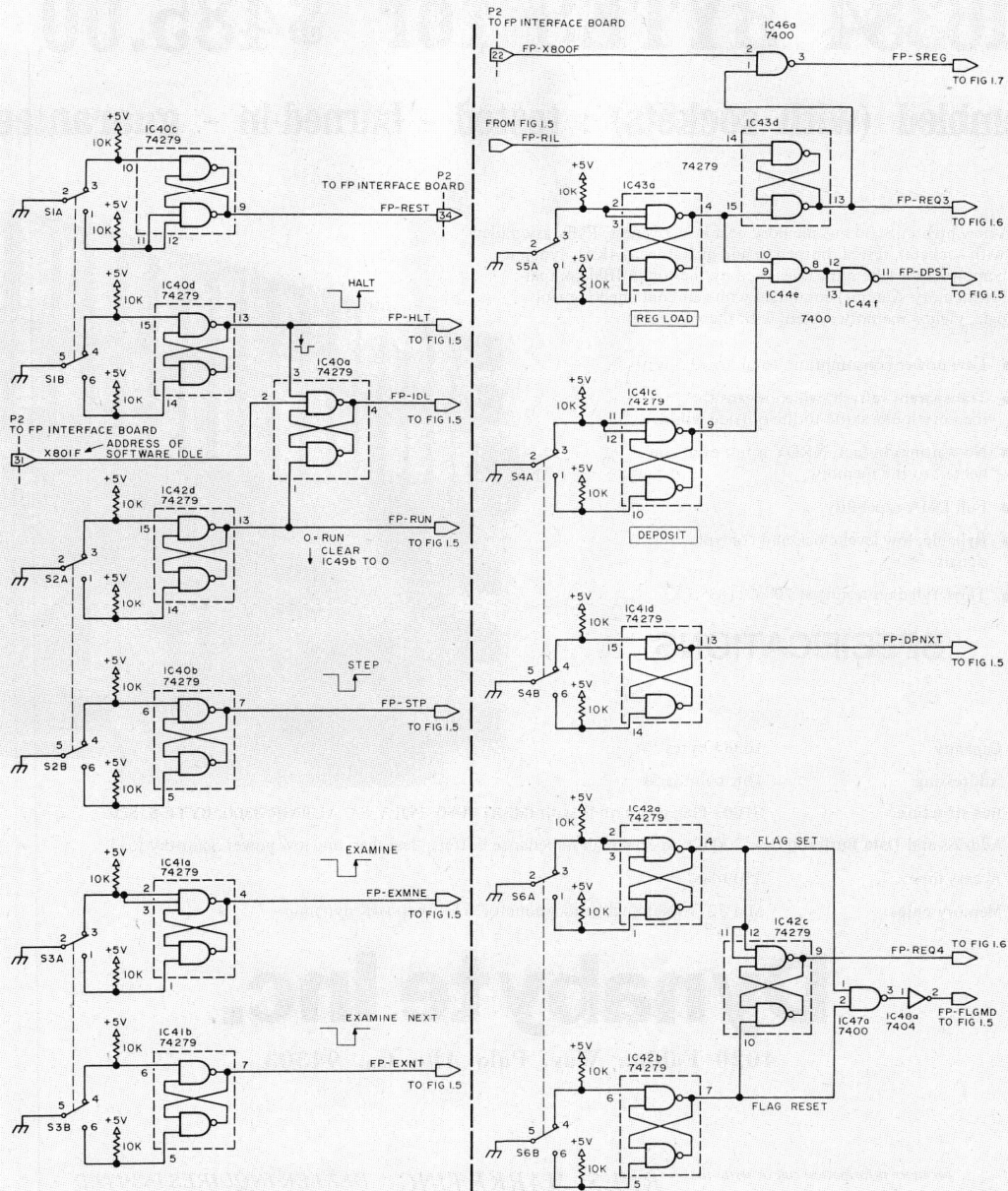


Figure 1.1: Switch debouncing logic. This is a detail logic diagram suitable for construction of Kompuutar. As in all the logic of this design, all resistors are 1/4 W unless otherwise noted, and standard TTL integrated circuits are used for miscellaneous functions. Debouncing is done with set-reset flip flops contained in the 74279 part, which we have noted in the discrete logic form internal to dotted lines. The flip flops can be wired out of gates (7400, 7410) if desired, should the 74279 be unavailable in the builder's parts bin. Integrated circuit power wiring for the entire design is summarized by IC number in table 5.



Figure 1.2: Flag selection switch. The control panel service program of Kompuutar uses the binary encoded 3 bit value on the output of this switch to determine which processor flag is to be set or reset using an appropriate function selection. This switch is a rotary switch which has three poles and eight positions.

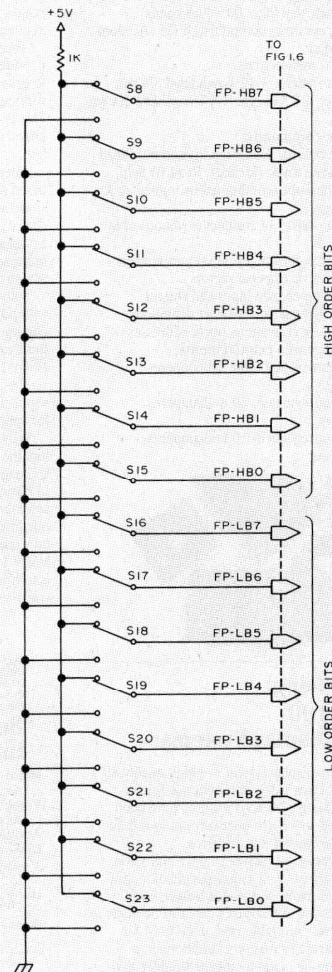


Figure 1.3: Front panel data entry switches. The entry of static data is accomplished by 16 toggle switches. These switches are connected to either logical 1 (+5 V through a 1 K resistor) or logical 0 (ground).


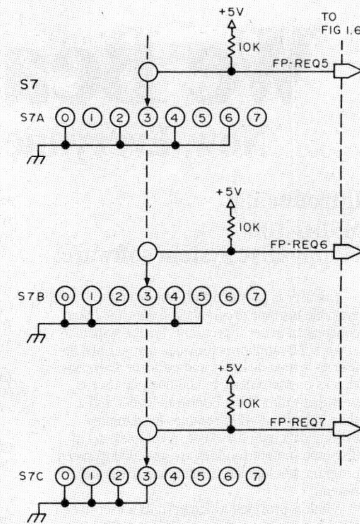


Figure 1.4: Display data selection switch. The control panel service program uses the binary encoded 4 bit value on the output of five possible words for default display from the control panel scratch pad located at addresses 8000 to 800F. The five addresses selected are for the accumulator (0), X index (1), Y index (2), stack register (5) or data register (D).

 

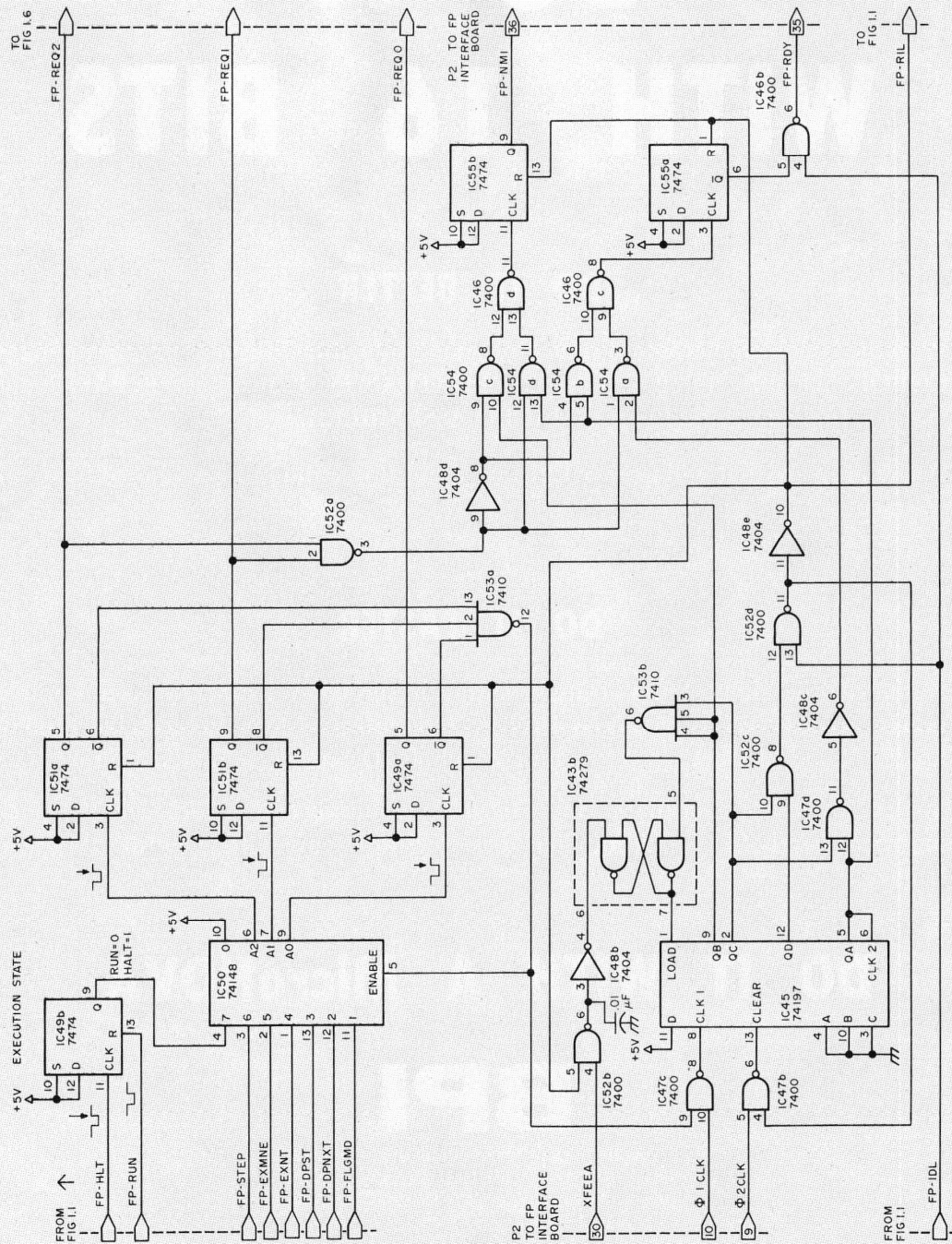


Figure 1.5: Control logic for front panel functions. This logic generates the function request code (read from address 8010 bits 0 to 2), and controls the NMI line of the 6502 to implement single step execution of the processor.

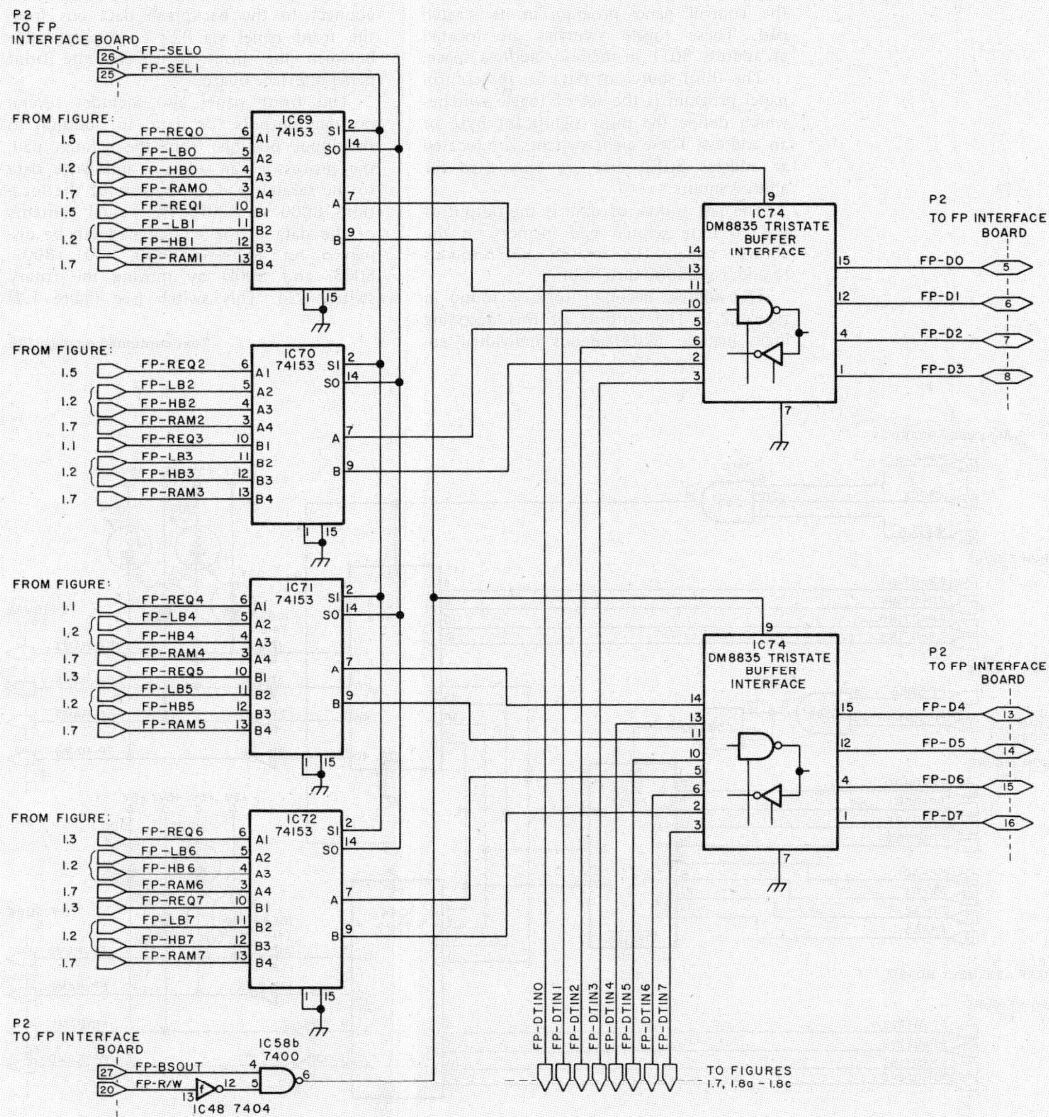


Figure 1.6: Data source multiplexer and bus interface. The sources of data read from the front panel logic are four: the two 8 bit data entry switch registers of figure 1.3, the 8 bit control request word from figure 1.5, and the output of the scratch pad programmable memory (lines labeled "RAM") from figure 1.7. These are selected by a 2 bit addressing code generated on the front panel interface board of figures 2.



Text continued from page 102

order byte of the data entry switches. The eight toggle switches of this switch register are used to enter a byte into the data bus or into the least significant byte of the address register which is maintained by the control panel program in its scratch pad. These toggle switches are located at address 8011 in memory address space.

The third source of data for the control panel program is the set of toggle switches which define the most significant byte of an address. These eight switches are located at address 8012, and are only used for address inputs.

The last source of data is the output of the 16 byte scratch pad memory in the control panel. The scratch pad responds to addresses 8000 thru 800F.

The address decoding logic is found in figure 2.1. The outputs of this decoding logic include miscellaneous individual ad-

dress selections, plus the selection signals which are used to control the data input multiplexer found in figure 1.6. The selection signals are generated by the priority encoder IC35, and are used to pick one of the four sources for routing to the bus interface gates IC73 and IC74. These gates connect to the backplane data bus from the front panel via P2's connecting cable between the front panel and the front panel interface board.

The front panel also includes several possible outputs for data. In addition to the input possible from the scratch pad, the processor can address and write data to the scratch pad in any one of the locations 8000 to 800F. The actual contents of the data in the scratch pad can be displayed for addresses 8000, 8001, 8002, 8003, and 800D by moving the rotary switch S24. This switch (see figure 1.4)

Text continued on page 116



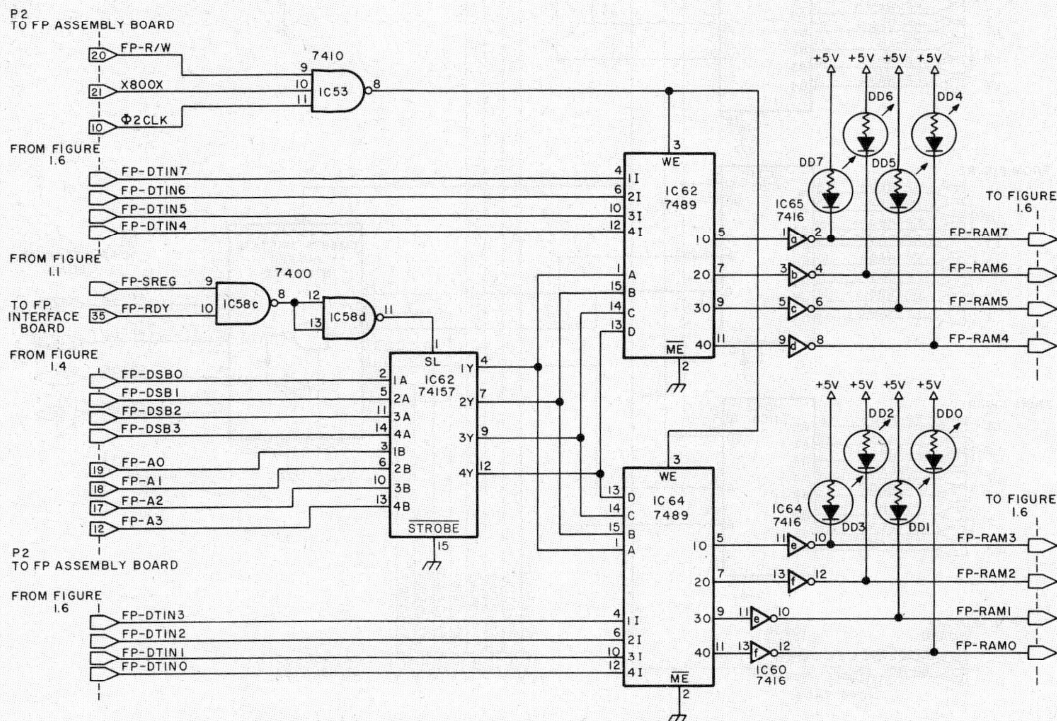


Figure 1.7: Front panel scratch pad programmable memory. The front panel implements a 16 byte scratch pad programmable memory at addresses 8000 to 800F. This memory is used for data storage and for storage of a scratch pad program segment which is modified during execution of the front panel service routines.

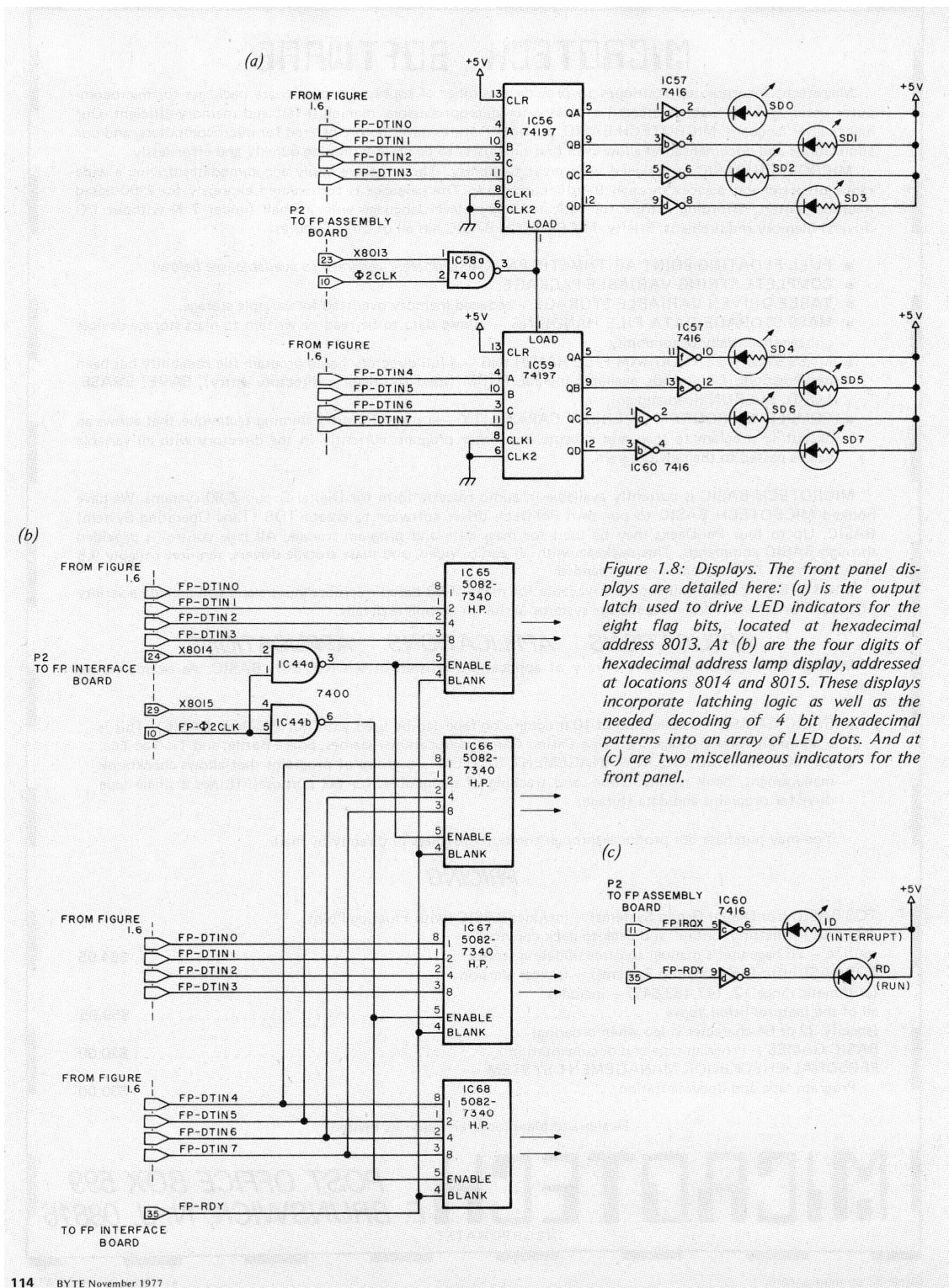

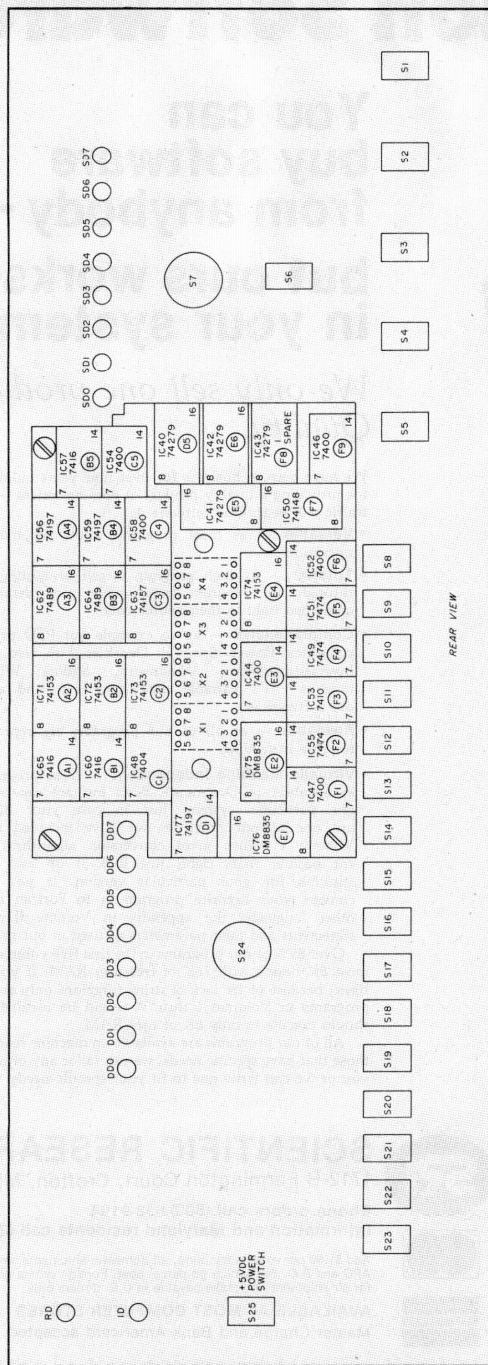

Text continued from page 112

defines an address value which is presented to the 7489 scratch pad memories IC61 and IC63 by 74157 multiplexer IC62 when the scratch pads are not being referenced by the processor. Since the control panel program references the scratch pad only occasionally, the normal state is an address selected by S24 determining which of the five scratch pad locations is seen in the display lamps for scratch pad data. Thus the scratch pad memory has several potentially visible bytes of memory address space and acts as an output device.

A second output device is an 8 bit data latch whose outputs activate eight discrete LED devices. This device, located at address 8013 in memory address space, is used to display the processor's status register bits. The front panel control program is responsible for maintaining current information in this display (as is the case with all the display outputs).

Address display information is latched into four digits of hexadecimal display provided by Hewlett-Packard HP5082-7340 parts, IC65, IC66, IC67 and IC68 in figure 1.8b. Each of these displays has a built-in 4 bit data latch which retains information defined by writing to the memory locations 8014 (low order) and 8015 (high order).

Two miscellaneous indicators are also included in the design. These single bit LED displays are connected to the processor's ready (RDY) and main interrupt (IRQ) lines. The RUN indicator lights


Text continued on page 119

Figure 1.9: Front panel mechanical layout. This is a detail drawing to scale of the physical layout of the front panel as seen in the photographs, along with the front panel electronics board which is mounted on standoffs behind the panel.

## NOTES:

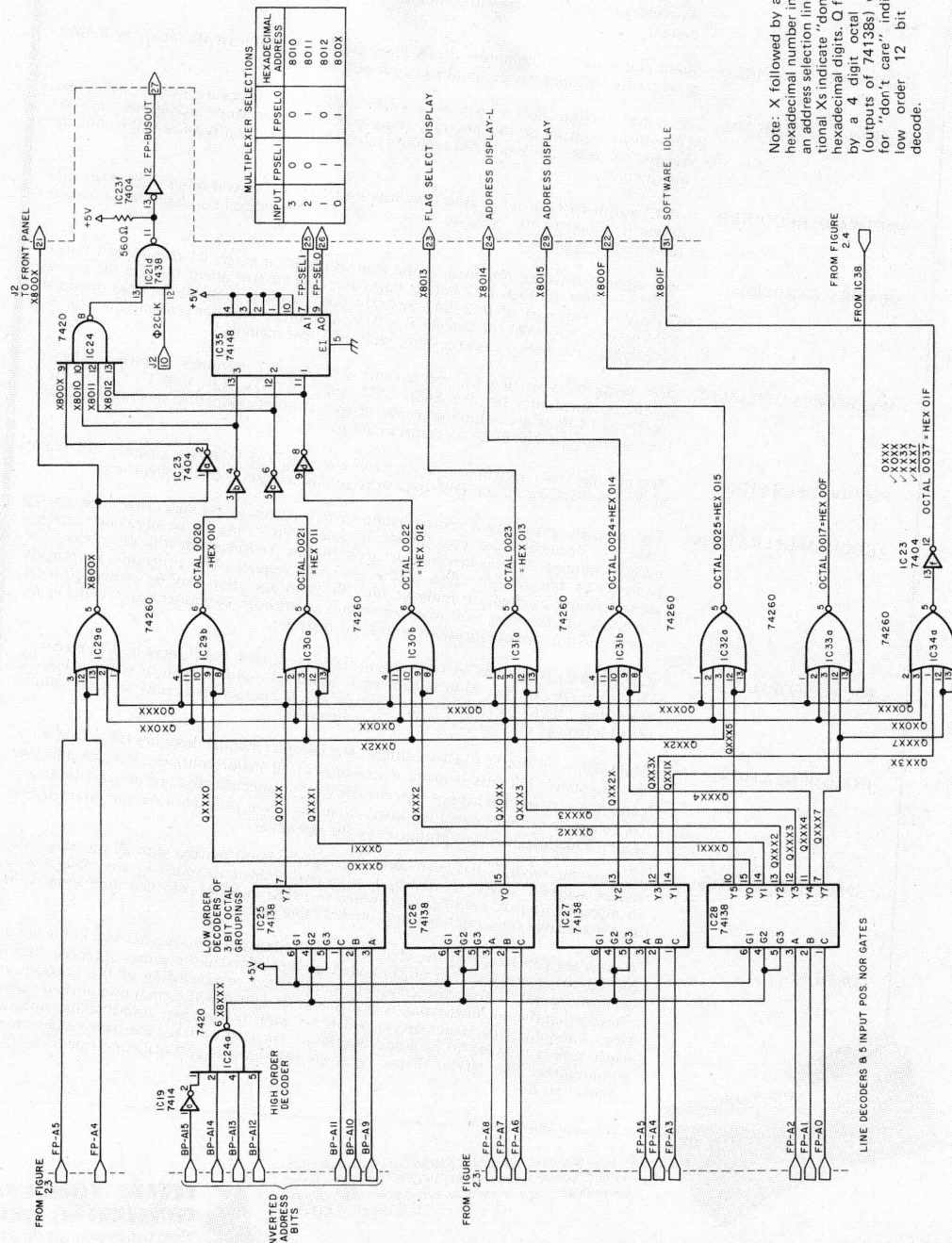1. All ICs except locations E1 and E2 are Texas Instruments SN74XXX series TTL logic. E1 and E2 are three-state bidirectional bus drivers made by National.
2. Switches S1 thru S6 are Alco model MTF-206SA.
3. Switches S8 thru S23 are Alco model MTF-106D.
4. Switch S7 is a Centralab model PA-2009 rotary.
5. Switch S24 is a Centralab model PA-2011 rotary.
6. RD, ID, DD0 to DD7 and SD0 to SD7 are discrete LED displays. HP model 5082-4860.
7. X1-X4 are dot matrix hexadecimal LED displays. HP model 5082-7340.
8. All pull up resistors shown on schematics in conjunction with front panel switches are mounted on those switches.





Text continued from page 116

up when the machine is in the run mode, and the interrupt indicator remains lit while an interrupt is pending. Interrupt control logic is contained in the devices requesting an interrupt, with the processor's priority encoder defining the backplane signal IRQX (backplane pin 12) which indicates that some interrupt is pending (and also signals the processor through its IRQ input, pin 4.) Thus when interrupt driven IO is used, the interrupt indicator lamp will flicker if appreciable interrupt processing wait states occur as various devices request attention.

#### Other Front Panel Functions

The front panel logic includes logic of the ready (RDY) and nonmaskable interrupt (NMI) timing, shown in detail in figure 1.5. These lines are used to generate signals which affect the processor in a manner very similar to interrupts. The HALT and single STEP switch are used to generate signals for these lines. This timing logic causes the 6502 processor and its control program to implement fairly conventional single stepping and program halt or restart functions. HALT or STEP switches are used to cause the processor to complete the present instruction, then execute one more instruction. Any other switch activated on the front panel causes this logic to allow the processor to complete only its present instruction. The hardware protocol of this logic locks out all front panel functions when the processor is running, except for the HALT switch.

The front panel's interfaces to human fingers are through various function switches. These switches are debounced using set-reset flip flops which come four to a package in the 74279 part. The debouncing logic guarantees that only one pulse is received for each activation of a switch.

#### Getting Kompuutar Into Operation

The operation of the front panel's control logic with respect to the actual processor

Figure 2.2: Buffering of processor control signals at the front panel interface module.

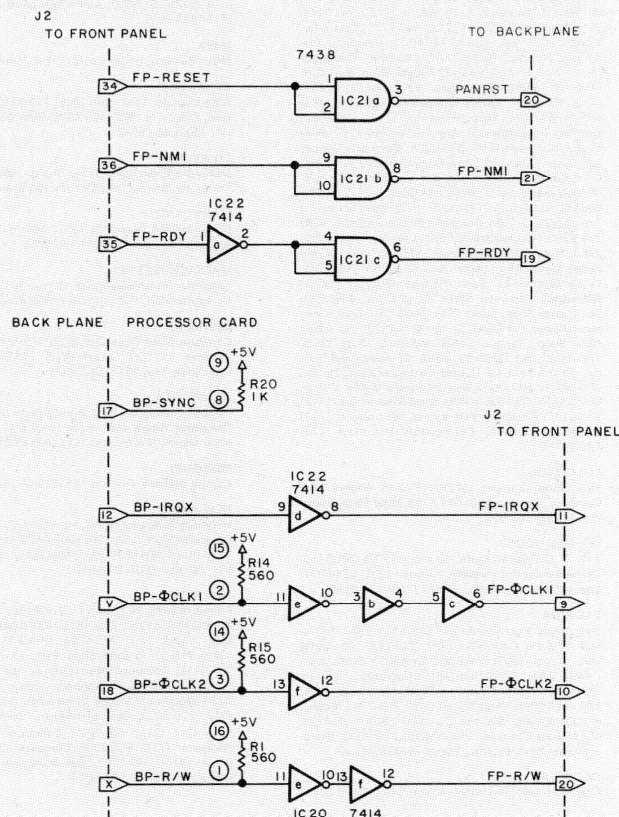


Figure 2.1: Front panel interface module address decode logic. This logic decodes the several addresses in the 8000 to 801F range which are used by the front panel design of Kompuutar. Since 3 bit decoders are used, octal intermediate terms are used to symbolize the outputs of the 74138s prior to logical sums performed by the 74260 OR gates. Outputs of the circuit are discrete select lines for several addresses, plus two source selection lines for the data bus input multiplexer of figure 1.6.

can be illustrated by walking verbally through a typical sequence of operations. First, let's assume that the machine is in RUN mode, which is indicated by a low level on the output of the execution state flip flop, IC49b pin 9. This is the normal situation for a fully executing 6502 program contained in the system's main program-

mable memory region. Next, press the front panel's HALT switch, S1. Upon release of the HALT switch the debounce logic completes one HALT pulse which is processed by the command encoding logic of figure 1.5. When the HALT line makes

Text continued on page 128

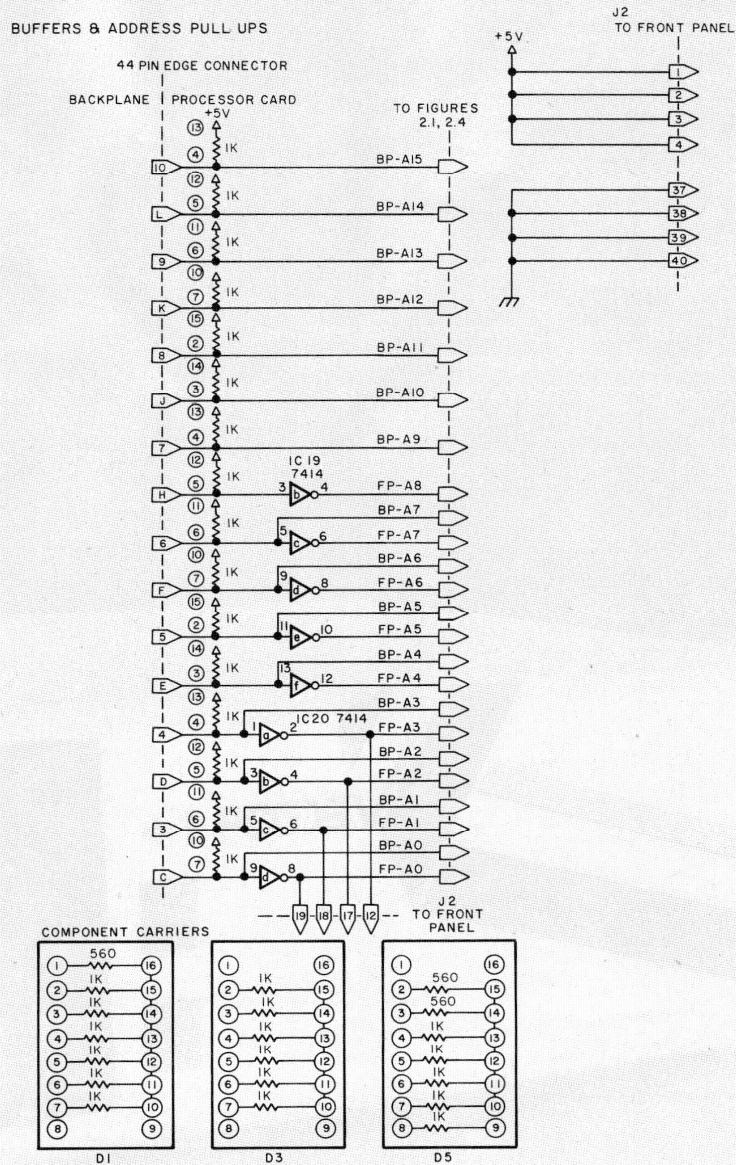


Figure 2.3: Pull up resistors for backplane address lines, and inverting receivers for local use in the front panel interface.





Figure 2.5: Mechanical layout of the front panel interface module. This board is built on a standard Vector Electronic Co prototyping card, and plugs into the 44 pin backplane connector (two sides with 22 pins each).


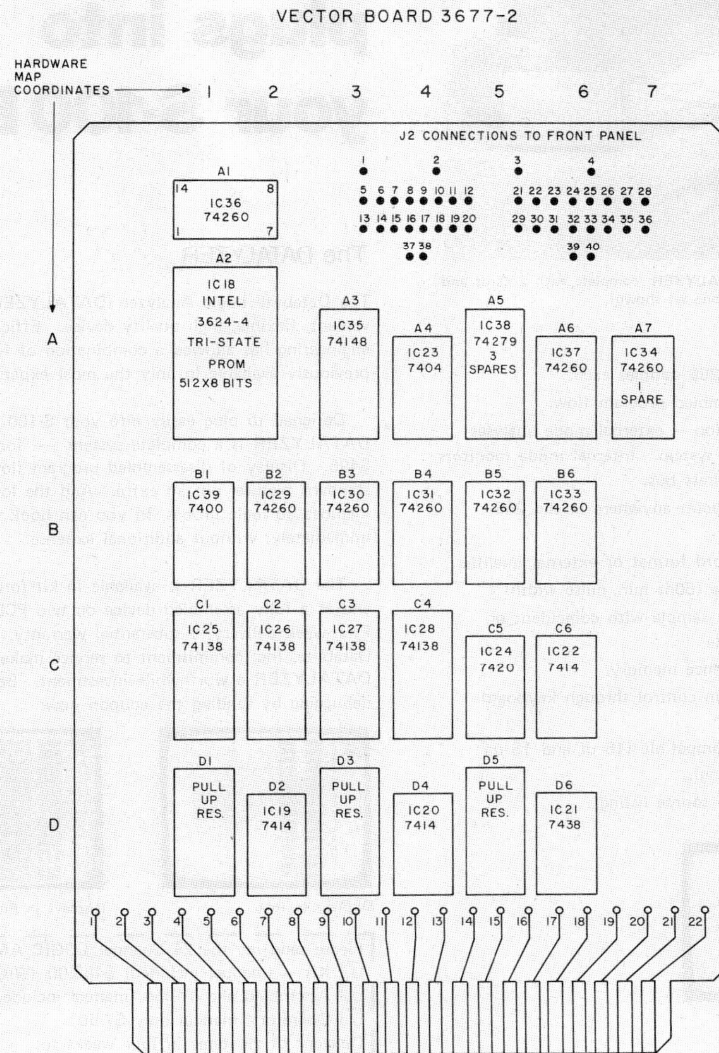


Figure 3.1: Processor module diagram. The 6502 processor module contains the 6502, its data bus and address bus buffering logic, and logic of the priority interrupt structure which substitutes one of six interrupt vector addresses on the low order address lines based on the priority of an interrupt. This overrides the processor generated address of FFFE or FFFF for an interrupt via the IRQ input. IRQ interrupt vectors are located at addresses FFE4 to FFE0 in memory address space, with six priority levels. Note that the BRK instruction maps to vector FFE0 (see listing 1).

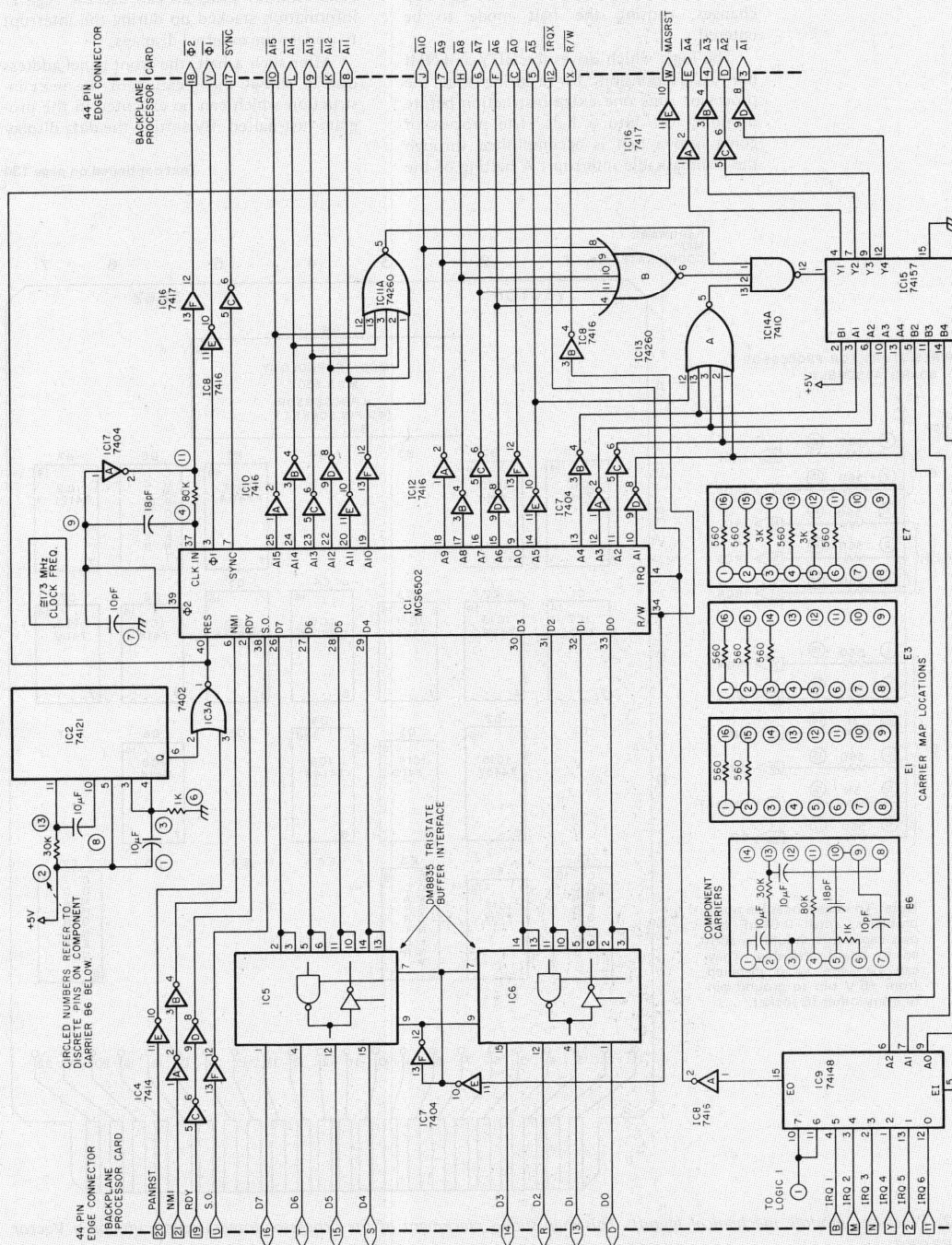



Text continued from page 122

its rising transition at the end of the pulse, the state of the execution state flip flop changes, causing the halt mode to be entered.

The logic which drives the RDY and NMI lines is responsible for assuring that the processor runs one extra instruction before dropping off into a halt. The process of going into a halt is accomplished through the nonmaskable interrupt. A halting of the

user program really means return to the front panel control program through the NMI signal generated here, so that the front panel control program can use the register information stacked up during the interrupt to update the external displays.

After such a halt, the front panel address display shows the location of the next instruction which can be executed in the program just halted. By setting the data display

Text continued on page 134

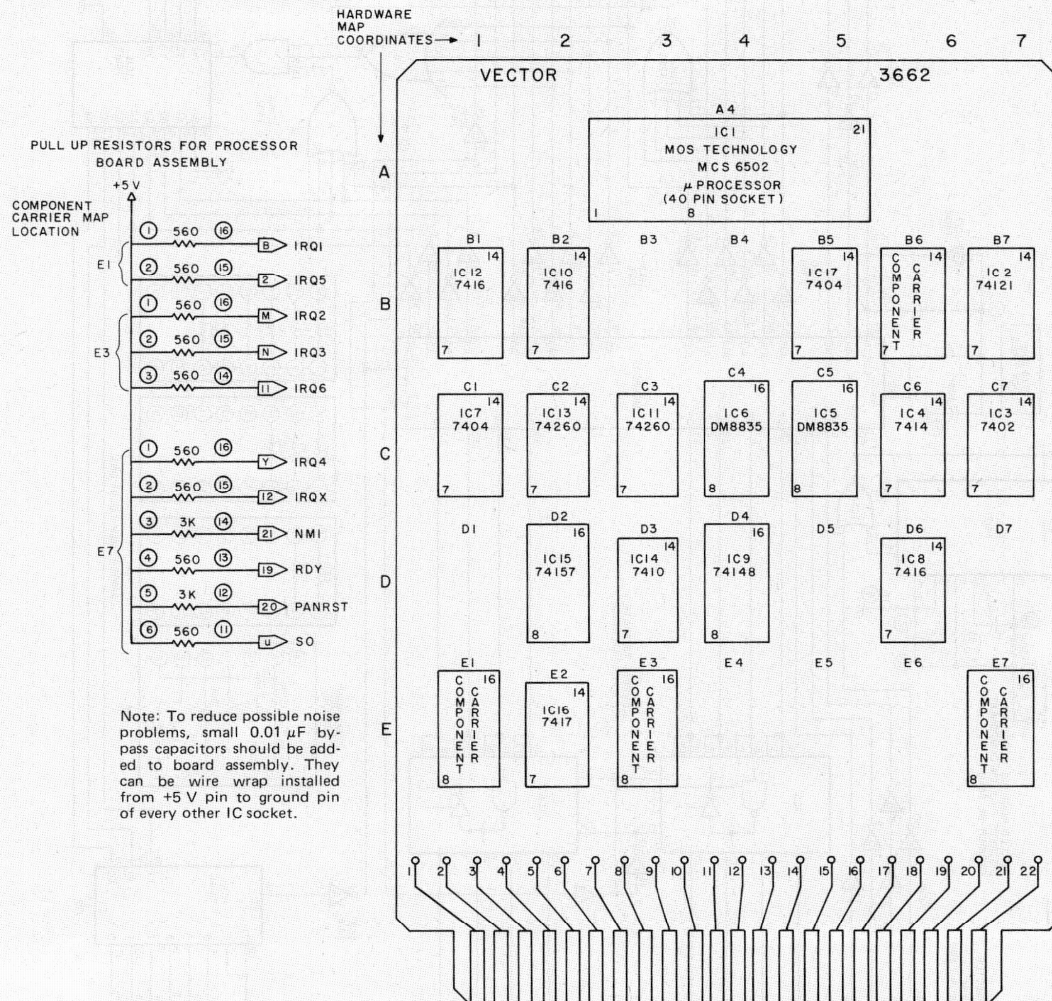


Figure 3.2: Processor module mechanical layout. This map shows placement of the processor integrated circuits on a Vector prototyping card.

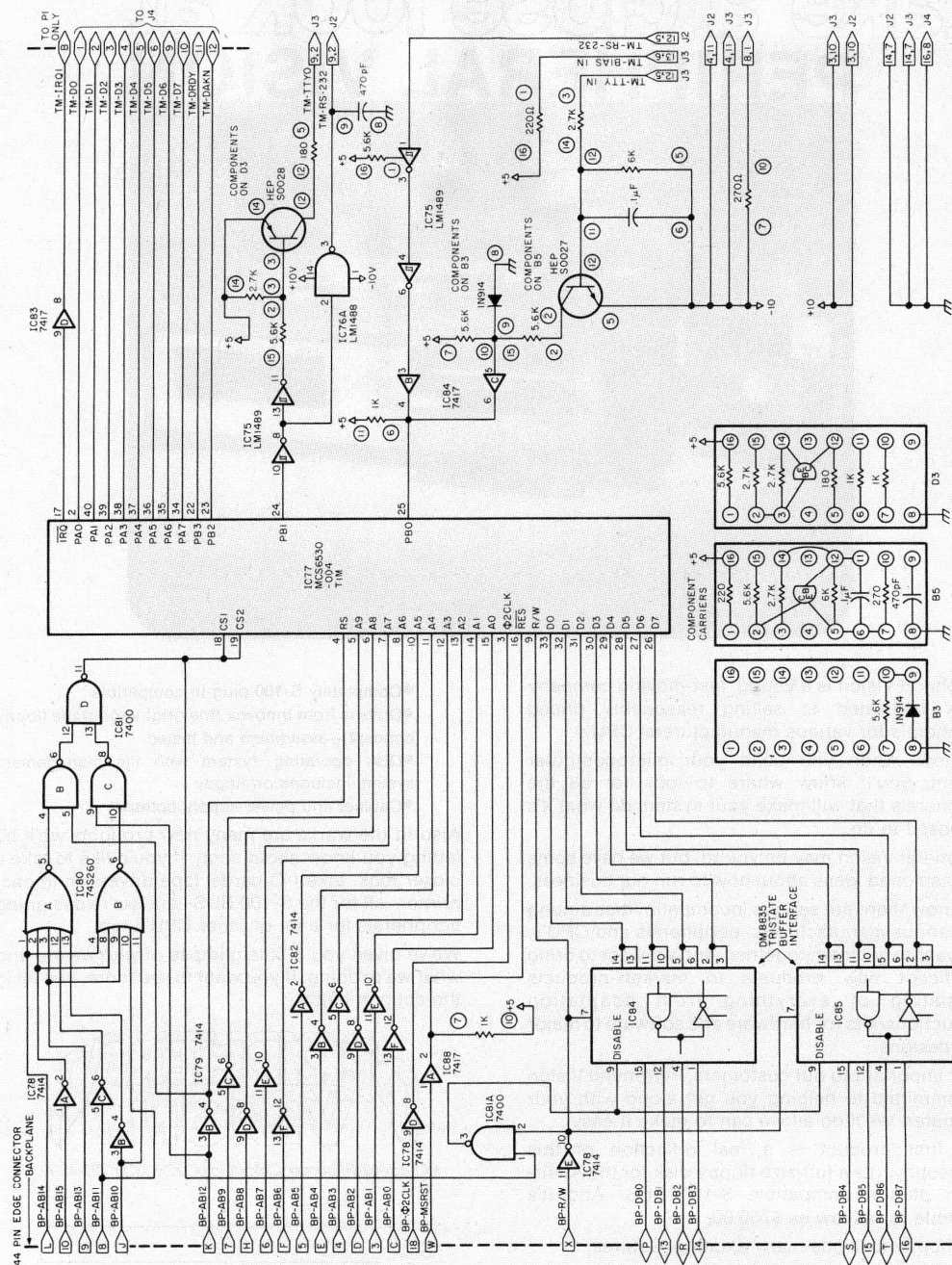


Figure 4.1: TIM interface module details. The MOS Technology TIM monitor program resides in a single MCS6530 ROM and peripheral interface circuit. The TIM interface module allows Kompuutar to be used with any serial terminal.

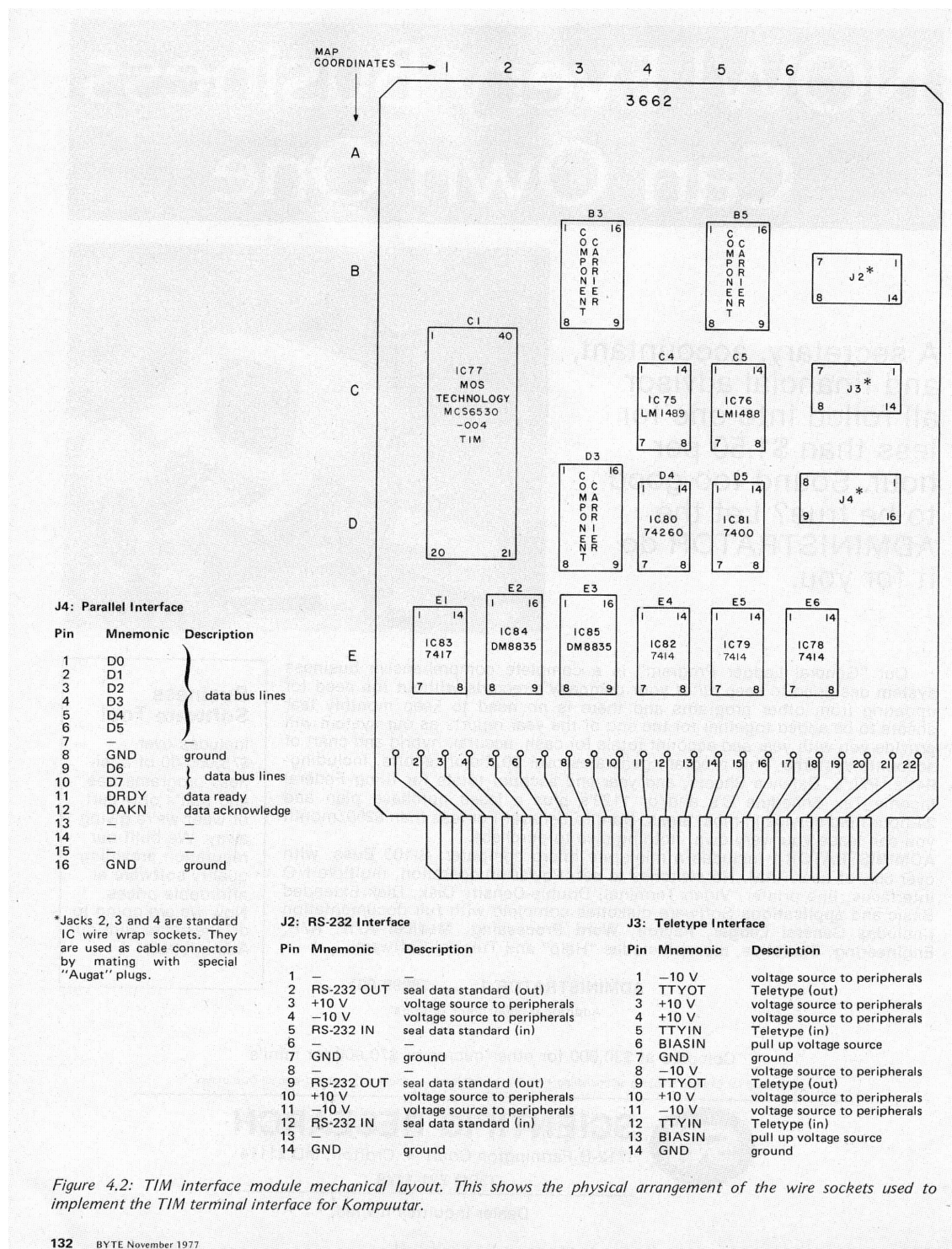


Figure 4.2: TIM interface module mechanical layout. This shows the physical arrangement of the wire sockets used to implement the TIM terminal interface for Kompuutar.



Text continued from page 128

selection switch to point to the DATA position, the contents of memory at this location are displayed, having been transferred to the front panel scratch pad location 800D by the service program during the halt operation. At other positions of the switch, it is possible to view copies of the X register, Y register, accumulator A or the stack pointer register. The current contents of the processor status register are shown in the eight

discrete LED outputs at location 8013 in memory address space.

If it is desired to modify a status flag, the flag select switch can be rotated to the desired bit, and the flag set or flag reset function be used to alter the flag state. If desired, memory can be examined or altered using the deposit, deposit next, examine or examine next routines activated by appropriate panel switches. Pressing RUN con-

Text continued on page 137

					Front Panel Assembly Circuits									
					IC	Type	+5 V	GND	Map Location in Figure 1.9					
Central Processor Module Integrated Circuits														
IC	Type	+5 V	GND	Map Location in Figure 3.2										
1	MSC6502	8	1, 21	A3, 4, 5	40	74279	16	8	D5					
2	74121	14	7	B7	41	74279	16	8	E5					
3	7402	14	7	C7	42	74279	16	8	E6					
4	7414	14	7	C6	43	74279	16	8	F8					
5	DM8835	16	8	C5	44	7400	14	7	E3					
6	DM8835	16	8	C4	45	74197	14	7	D1					
7	7404	14	7	C1	46	7400	14	7	F9					
8	7416	14	7	D6	47	7400	14	7	F1					
9	74148	16	8	D4	48	7404	14	7	C1					
10	7416	14	7	B2	49	7474	14	7	F4					
11	74260	14	7	C3	50	74148	16	8	F7					
12	7416	14	7	B1	51	7474	14	7	F5					
13	74260	14	7	C2	52	7400	14	7	F6					
14	7410	14	7	D3	53	7410	14	7	F3					
15	74157	16	8	D2	54	7400	14	7	C5					
16	7417	14	7	E2	55	7474	14	7	F2					
17	7404	14	7	B5	56	74197	14	7	A4					
					57	7416	14	7	B5					
					58	7400	14	7	C4					
					59	74197	14	7	B4					
					60	7416	14	7	B1					
					61	7489	16	8	A3					
					62	74157	16	8	C3					
					63	7489	16	8	B3					
					64	7416	14	7	A1					
					65	HP-5082-7340	7	6	X1					
					66	HP-5082-7340	7	6	X2					
					67	HP-5082-7340	7	6	X3					
					68	HP-5082-7340	7	6	X4					
Front Panel Interface Module Circuits														
IC	Type	+5 V	GND	Map Location in Figure 2.3										
18	Intel3624-4	22, 24	12	A2	69	74153	16	8	A2					
19	7414	14	7	D2	70	74153	16	8	B2					
20	7414	14	7	D4	71	74153	16	8	C2					
21	7438	14	7	D6	72	74153	16	8	E4					
22	7414	14	7	C6	73	DM8835	16	8	E2					
23	7404	14	7	A4	74	DM8835	16	8	E1					
24	7420	14	7	C5										
25	74138	16	8	C1										
26	74138	16	8	C2										
27	74138	16	8	C3										
28	74138	16	8	C4										
29	74260	14	7	B2										
30	74260	14	7	B3										
31	74260	14	7	B4										
32	74260	14	7	B5										
33	74260	14	7	B6										
34	74260	14	7	A7										
35	74148	16	8	A3										
36	74260	14	7	A1										
37	74260	14	7	A6										
38	74279	16	8	A5										
39	7400	14	7	B1										
										TIM Interface Module Circuits				
					IC	Type	+5 V	+10 V	−10 V	GND	Map Location in Figure 4.2			
					75	LM1489	14	—	—	7	C4			
					76	LM1488	—	14	1	7	C5			
					77	MCS6530	20	—	—	1	C1			
					78	7414	14	—	—	7	E6			
					79	7404	14	—	—	7	E5			
					80	74S260	14	—	—	7	D4			
					81	7400	14	—	—	7	D5			
					82	7404	14	—	—	7	E4			
					83	7417	14	—	—	7	E1			
					84	DM8835	16	—	—	8	E2			
					85	DM8835	16	—	—	8	E3			

Table 5: Integrated circuit summary for Kompuutar. This table summarizes the 85 integrated circuits used in Kompuutar, arranged in groupings by the circuit modules of the system. The column labelled "Map Location" identifies the physical position of the circuits on the various boards of the system, as shown in the physical layout diagrams in the figures. Note that the physical layouts represent a good workable arrangement of sockets. There is no logical requirement that the particular map positions used in these diagrams be followed to the letter in another implementation of the system.

Hexadecimal Address	Hexadecimal Code	Label	Op	Operand	Commentary	FE93	8D	15	8D	FE	STP	HADDR
						FE96	4C	9D	FE		JMP	CONTINUE
						FE99					* CONTROL	PANEL MONITOR EXIT POINT
						FE99	38				EXITCP	SEC [Set carry to indicate end of monitor];
FE00	8D 00 80	PNMI	STA	SVACC	[Save state of processor registers at interrupt];	FE9A	4C	9E	FE		JMP	SETSTAK
FE03	8E 01 80	STX SVX				FE9D	18				CONTINUE	CLC [Clear carry to continue monitor];
FE06	8C 02 80		STY	SVY								
FE08		* RECOVER PROCESSOR STATUS & RETURN ADDRESS AT INTERRUPT				FE9E					* BEGIN ROUTINE TO SET UP STACK AND TEMPORARILY LEAVE MONITOR	
FE09	68	UNSTK	PLA			FE9E	AD	08	80		SETSTAK	LDA SVADDR+1
FE0A	68		TAX			FEA1	48				LDA	SVADDR
FE0B	68		PLA			FEA2	AD	07	80		LDA	SVADDR
FE0C	A8		TAY			FEA5	48				LDA	SVPLFG
FE0D	68		PLA			FEA6	AD	03	80		LDA	SVPLFG
FE0E		* SAVE STATUS, RETURN ADDRESS & STACK IN SCRATCH PAD				FEA9	48				LDA	SVPLFG
FE0E	8E 03 80	SAVERET	STX	SVPLFG		FEAA	AE	05	80		LDX	SVSTK
FE11	8C 07 80		STY	SVADDR		FEAD	CA	DE			DEX	
FE14	8D 08 80		STX	SVADDR+1		FEAE	CA	DE			DEX	
FE17	8A		TSX			FEAF	CA				DEX	
FE18	8E 05 80		STX	SVSTK		FE80	9A				TXS	
FE18		* INTERRUPT CONTROL FUNCTION REQUEST REGISTER				FE81	AE	01	80		LDX	SVX
FE18	AD 10 80	LDA	REQST			FE84	AC	02	80		LDX	SVY
FE1E	0A	ASL				FE87	AD	00	80		LDA	SVACC
FE1F	0A	ASL				FE8A	8D	0E	80		STA	LSTACC
FE20	0A	ASL				FE8D	8D	0C			BCS	LEAVE
FE21	0A	ASL										
FE22	8D 04 80		STA	SVAAA		FE8F					* MANIPULATIONS FOR SINGLE STEP CASE FOLLOW	
FE25	A9 20	LDA	\$S20			FE8F	A9	FF			LDA	\$SFF
FE27	2C 04 80	BIT	SVAAA			FE91	4D	00	80		EOR	SVACC
FE2A	10 03	BPL	*+5		If request greater than 7 then go do register load routine;	FE94	8D	00	80		STA	SVACC
FE2C	4C 7F FF	JMP	REGLD		Else if 4 < request < 7 then halt, step, examine or exam next;	FE97	A9	FF			LDA	\$SFF
FE2F	70 1C	BVS	XHSEE		Else if 2 < request < 3 then deposit or deposit next;	FE9C	AD	01	80		EOR	SVX
FE31	0D 0D	BNE	XDDN			FE9C	8D	01	80		STA	SVX
FE31		* CONCLUDE REQUEST IS 0 OR 1				FE9F	4D	02	80		EOR	\$SFF
FE33	A9 10	LDA	\$S10		[Set up mask for bit test].	FE9F	AD	02	80		EOR	SVY
FE35	2C 04 80	BIT	SVAAA		Is request 0?	FE9F	8D	02	80		STA	SVY
FE38	D0 03	BNE	*+5		Is request = 0 then leave control program via normal NMI;	FE9F	A9	FF			LDA	\$SFF
FE3A	4C 99 FE	JMP	EXITCP		If request = 1 then go do FLAG function service;	FE9F	AD	05	80		EOR	SVSTK
FE3D	4C 36 FF	JMP	FLAG			FE9F	8D	05	80		STA	SVSTK
FE40	A9 10	XDDN	LDA	\$S10	Is request 2?	FE9F	A9	FF			LDA	\$SFF
FE42	2C 04 80	BIT	SVAAA		If request = 2 then go do DEPOSIT NEXT service;	FE9F	AD	00	80		EOR	SVDATA
FE45	D0 03	BNE	*+5		Is request 3 then go do DEPOSIT service;	FE9F	4D	00	80		EOR	SVDATA
FE47	4C 29 FF	JMP	DPSNXT		If request = 4 then go do EXAMINE NEXT;	FE9F	8D	00	80		STA	LSTACC
FE4A	4C 1E FF	JMP	DEPOSIT		If request = 5 then go do EXAMINE NEXT;	FE9F	4D	00	80		EOR	SVDATA
FE4D	DO 0D	XHSEE	BNE	XHLSS	If request = 6 or request = 7 then go do HALT or STEP;	FE9F	8D	00	80		STA	LSTACC
FE4D		* CONCLUDE REQUEST IS 4 TO 7				FE9F						

Text continued from page 134

tinues execution of the program at the currently displayed address.

After building the design, I found a couple of subtle points in the operation of the control panel. The first point to note is that when using the RESET switch, the processor must be in the RUN mode of the RUN versus STEP switch. Second, bit 5 of the status display is useless and unimplemented in the 6502 hardware. The register load switch (REG LOAD) is best used for modifying the contents of the accumulator, index registers, but not the stack pointer. Using the register load switch to modify the stack pointer can result in problems when resuming execution of a program. Once whatever memory loading or register alteration chores required by a program have been accomplished, execution can be resumed using the RUN switch to cause the control panel program to return from interrupt using the register contents stored in the control panel scratch area.

#### A Versatile Configuration

The design of Kompuutar is quite readily adaptable to the 6800 processor as a substitute for the 6502 if personal programming preferences or availability of chips dictates such a switch. The similarities between the two processors are quite extensive, and in fact were the bone of contention of a lawsuit (since settled) shortly after the 6502 came out. At the system level, here are the major differences to be aware of:

- The pinouts of the 40 pin package used for each processor are different, but the signal definitions of NMI, data bus lines, IRQ, reset, address bus, etc, are equivalent.
- The 6800 uses four read only memory interrupt vectors at addresses FFF8 to FFFF in memory address space, whereas the 6502 uses only three interrupt vectors; the definitions of the interrupt vectors for reset, non-maskable interrupt and maskable interrupts are similar.
- The instruction sets differ, so the front panel service programs shown with this article would need to be recoded if a 6800 is used.
- The definition of the clock used by the processor differs in the details of its drive circuit.

The major features of either a 6502 or 6800 system at the level of the backplane bus defined here would be nearly identical. ■

Listing 1, continued:

Hexadecimal Address	Hexadecimal Code	Label	Op	Operand	Commentary
FF33	4C FF FE		JMP	ADVANCE	
FF36					
FF36	AD 10 80				* FLAG REGISTER CHANGE SERVICE ROUTINE
FF36			LDA	REQST	FLAG
FF39					* ALIGN THE FLAG SELECTION BITS WITH FOUR RIGHT SHIFTS
FF39	4A		LSR		
FF3A	4A		LSR		
FF3B	4A		LSR		
FF3C	4A		LSR		
FF3D	8D 04 80		STA	SVAAA	
FF40	A9 01		LDA	#S1	
FF42	2C 04 80		BIT	SVAAA	Is flag data bit on?
FF43	F0 05		BEQ	SETYZER	If flag data = 0 then Y:=0;
FF47	A0 FF		LDY	#SFF	Else Y:= SFF;
FF48	4C 4E FF		JMP	PROCFLAG	
FF4C	A0 00		SETYZER	LDY #S00	
FF4E	4E 04 80		PROCFLAG	LSR SVAAA	[Final right shift aligns the 3 bit flag code];
FF51	A2 07		LDX	#S07	[Load loop count];
FF53	EC 04 80		FLGLOOP	CPX SVAAA	
FF56	F0 04		BEQ	FCHANGE	If SVAAA = X then go change this flag;
FF58	CA		DEX		
FF59	4C 53 FF		JMP	FLGLOOP	
FF5C	A9 01		FCHANGE	LDA #S01	
FF5E	E0 00		* LOOP	ALIGN MASK ON PROPER FLAG BIT	
FF60	F0 05		FLOOK	CPX #S00	
FF62	0A		BEQ	*7	
FF63	CA		ASL		
FF64	4C 5E FF		DEX		
FF67			JMP	FLOOK	
FF67					* AT END OF LOOP WITH MASK IN PLACE, CHANGE FLAG BIT
FF67	C0 00		CPY	#S0	Is data 0?
FF69	D0 0B		BNE	SETFLG	If not then go set flag;
FF6B	49 FF		EOR	#SFF	
FF6D	2D 03 80		AND	SVFPLG	[Turn off the flag bit with inverted mask];
FF70	8D 03 80		STA	SVFPLG	
FF73	4C 77 FE		JMP	SETTRAP	
FF76	0D 03 80		SETFLG	ORA SVFPLG	[Turn on the selected bit from mask];
FF79	8D 03 80		STA	SVFPLG	
FF7C	4C 77 FE		JMP	SETTRAP	
FF7F					* REGISTER LOAD SERVICE ROUTINE
FF7F					* REGISTER LOAD SERVICE ROUTINE
FF7F	A9 0F		REGLD	LDA #S0F	
FF81	8D 0A 80		STA	DUMMY3	
FF84	A9 AE		LDA	#SAE	[Define LDX as first operation of scratch pad program];
FF86	8D 06 80		STA	DATATRAP	
FF89	A9 FF		LDA	#SFF	
FF8B	4D 0D 80		EOR	SVDATA	[Invert data];
FF8E	8D 0D 80		STA	SVDATA	
FF91	AD 11 80		LDA	DSWLOW	
FF94	4C 7C FE		JMP	SETUP	
FFA0	A2 FF		RESET	LDX #SFF	unused space
FFA2	9A		TXS		[Initialize stack pointer];
FFA3	4C 06 70		JMP	TIM	[Jump to TIM monitor on system RESET];
FFE0	00 F0		BRK	Instruction vector	unused space
FFE2	XX XX				Not used
FFE4	00 FC		IRQ6	Lowest priority	
FFE6	00 FB		IRQ5		
FFE8	00 FA		IRQ4		
FFEA	00 F9		IRQ3	Interrupt vectors	
FFEC	00 F8		IRQ2		
FFEE	00 F7		IRQ1	Highest priority	
FFFA	00 FE				NMI interrupt vector location
FFFC	A0 FF				RESET interrupt vector location
FFFE	xx xx				

#### Kompuutar Peripheral and Scratch Pad Data Symbols:

Address	Symbol	Description
8000	SVACC	Saved accumulator value, scratch pad
8001	SVX	Saved X index register value, scratch pad
8002	SVY	Saved Y index register value, scratch pad
8003	SVFPLG	Saved processor flag register value, scratch pad
8004	SVAAA	Scratch value
8005	SVSTK	Saved stack register value
8006	DATATRAP	First operation of scratch pad program (absolute addressing through SVADDR)
8007	SVADDR	Low order saved address value, scratch pad program absolute address for DATATRAP
8008	SVADDR+1	High order saved address value
8009	DUMMY2	
800A	DUMMY3	Balance of scratch pad program
800B	DUMMY4	
800C	DUMMY5	
800D	SVDATA	Data value at current SVADDR
800E	LSTACC	Accumulator storage temporary
800F	SVAAA	Scratch value
8010	REQST	Front panel request input word
8011	DSWLOW	Low order data switch register input (data or address information)
8012	DSWHIGH	High order data switch register input (address information only)
8013	STATUS	Status lamps output
8014	LADDR	Low order address display output
8015	HADDR	High order address display output