

An Easy-to-Use A/D Converter

Robert Daggit
1648 Hillview Rd
New Brighton MN 55112

With the addition of an analog-to-digital converter and some simple sensors, a microcomputer can monitor analog voltages, read light levels, sense temperatures, or read the analog output from laboratory instruments. The six-channel A/D

About the Author

Robert Daggit is a Senior Research Technician at the Systems and Research Center of Honeywell Inc in Minneapolis. He is interested in the application of microprocessors to small, dedicated systems for laboratory use.

(analog-to-digital) converter that I will describe reads positive voltages from 0 to 3 V, with either 8 or 10 bits of accuracy. It interfaces to the computer through an 8-bit bidirectional peripheral port whose I/O (input/output) lines are individually programmable and latched when used as outputs.

Once started, the converter operates asynchronously with respect to the computer and requires a minimum of code in the user's pro-

gram. Conversion times are voltage-dependent, with an approximate range of 1 to 2 ms (milliseconds). A sample program segment and subroutine written in 6502 assembly language are included to illustrate the use of the converter.

Major components of the A/D converter unit, shown as a schematic diagram in figure 1, are a Fairchild Semiconductor μ A9708 analog-to-digital-converter integrated circuit, a clock, a 12-bit counter, and a 16-bit output multiplexer. The μ A9708 features an analog input multiplexer, controlled by address lines A0 thru A2, that selects one of eight input sources. Address 0 selects the internal zero voltage, and address 7 selects the internal reference voltage. Addresses 1 thru 6 select user inputs I1 thru I6, as shown in figure 1. Although the manufacturer rates the μ A9708 at 8 bits of accuracy, it performs well at 10 bits of accuracy. A series of voltage readings taken at 0.1 V intervals from 0 to 3 V compared favorably with readings taken with a Fluke Model 8000A Digital Multimeter. Voltage differences ranged from 2 to 11 mV (millivolts). The greatest relative error, defined as the absolute value of the voltage difference divided by the multimeter reading, was less than 2%.

In order to read one of the analog channels, the channel address is placed on the address lines, and the ramp-start input (pin 3) is set low. The ramp-stop output (pin 7) goes high at this time. With the address lines stable for a signal-acquisition time of about 1 ms, the ramp capacitor, C1, charges to the voltage

FINDING SOLUTIONS AND BEING COMPETITIVE IS OUR BUSINESS.

Having problems and looking for a computer to help solve them? Are you finding computer dealers come in one of two ways? Either Full system support with Full price or Take it or Leave it with Low price. At Omega we don't believe that you should have to make a choice. Yes, we're in business to sell products but also, to solve your problems. Our prices will be the lowest possible. Our support and product quality will be second to none. Check out our Mail Order prices in this ad (our retail prices will be higher). See if you don't agree with our first claim. For our second claim, call us with your data processing needs and problems. Better yet, come in and see us. Finding solutions and being competitive is our business. We never forget either of them.



APPLE II	CALL
APPLE II "PLUS" 48K	\$ 1169.95
HEWLETT PACKARD 85 or 83	CALL
APPLE II ACCESSORIES:	
Disk II with controller	\$ 535.00
Disk II 2nd drive	455.00
Graphics Tablet	665.00
Language System with PASCAL	395.00
Silentype Printer W/Int	526.00
Integer Firmware Card	152.00
Microsoft Z-80 Softcard	259.00
Videx videoterm 80 col Card	279.00
Sanyo 12" Green Monitor	269.00

Supplies:	
Scotch Diskettes - Best of Quality!	
price per box of (10)	
744-0, 10, 32	\$ 27.00
740-0 SS/DD 0 Sector	31.00
741-0 SS/DD 0 Sector	37.00
743-0 DS/DD No Format	44.00

New Products:	
Videx L/C Adapter	110.00
Microsoft 16K RAM Card	169.00
D.C. Hayes Micromodem II	315.00
Novation DCAT Modem	195.00
EPSON MX-80	CALL

Mail Order Terms of Sales: Price based on prepaid orders. NO COD's. Allow 14 working days for personal and company checks to clear. Order under \$100.00 add \$3.00 for shipping and handling. All orders (unless specified in ad) within Continental U.S. shipped U.P.S. no charge. APO or out of Continental U.S. write or call for shipping charges. All prices subject to change and all offers subject to withdrawal without notice. CA residents add 6% sales tax.

OMEGA MICRO COMPUTERS

The Problem Solving Company

3447 Torrance Boulevard • Torrance, California 90503 • (213) 370-9456

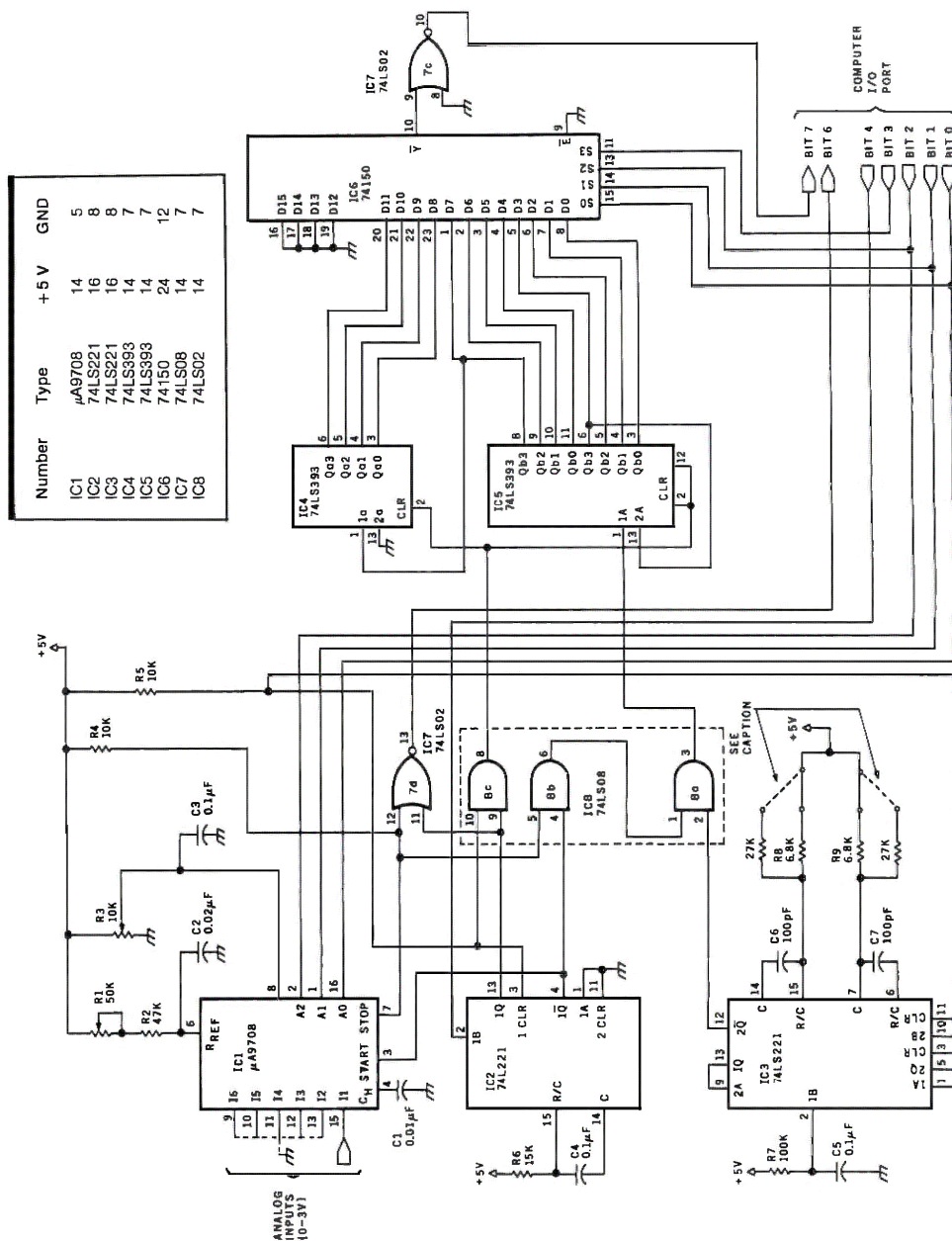


Figure 1: Schematic diagram of the A/D converter. Inputs I1 thru I6 of IC1 are the user's analog-input channels. The input voltage is converted to a binary number in the counter (IC4 and IC5), where it is retained until needed. The binary output is read in bit-serial fashion by the output multiplexer, IC6. Interface to the computer is through an 8-bit I/O port.

Easy selection of 8 or 10 bits of accuracy is accomplished by installing the clock timing components (C6, C7, R8, and R9) on a DIP header (see figure 2).

Lowest Prices on Personal Computers



800™ . \$789
ATARI® List \$1080

ATARI® 400... \$429



HP-85

NEW LOW PRICE!

\$2795

HP-85 Accessories

5 1/4" Dual Master Disc Drive List \$2500... \$2125
5 1/4" Single Master Disc Drive List \$1500... \$1275
HP 7225A Graphics Plotter List \$2050... \$1845
HP-85 16K Memory Module List \$395... \$355
HP-85 Application Paces Standard List \$95... \$85
Serial (RS-232C) Interface Module List \$395... \$355
GPIO Interface Module List \$495... \$445

new HP-83 List \$2250
\$1895

NEW! HP-41CV with five times more memory
built in. List \$325.
\$249

HP-41C List \$250
\$199

HP-32E Scientific w/Statistics — \$3.95
HP-33C Scientific Programmable — \$79.95
HP-34C Advanced Scientific Programmable — \$123.95
HP-37E Business Calculator — \$49.95

Personal Computer Systems

609 Butternut Street
Syracuse, N.Y. 13208
(315) 475-6800

Prices do not include shipping by UPS. All prices and offers subject to change without notice.

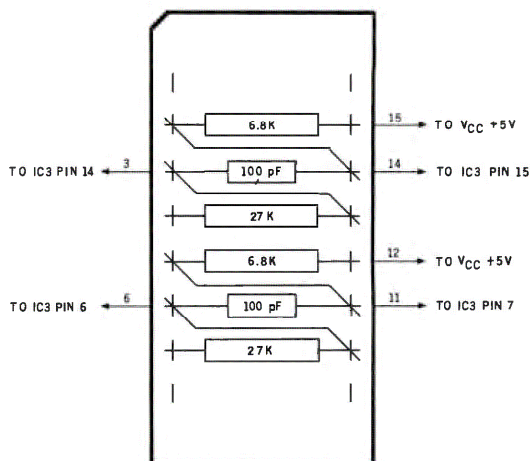


Figure 2: Wiring of the DIP header (top view). This optional feature may be installed for easy selection of 8 or 10 bits of accuracy. The clock timing components are mounted on the header in such a way that when it is reversed in its socket, the time constants of IC3 (a 74LS221 monostable multivibrator) are appropriately changed.

Listing 1: A program segment, written for the 6502 microprocessor, that illustrates use of the A/D converter. Hexadecimal 10 is added to the channel address, and this value is then written to the interfacing I/O port to start the conversion. Data from the counter is read when needed.

Address	Object Code	Label	Mnemonics	Comments
0250	A9 10		LDA H#10	;CHANNEL 0 ADDRESS
0252	8D 01 A8		STA DRA	;INITIATE A/D CONVERSION
0255	20 30 03		JSR RDADC	;READ CHANNEL 0 COUNT
0258	85 D0		STA D0	
025A	86 D1		STX D1	
025C	A9 17		LDA H#17	;CHANNEL 7 ADDRESS
025E	8D 01 A8		STA DRA	;INITIATE A/D CONVERSION
0261	20 30 03		JSR RDADC	;READ CHANNEL 7 COUNT
0264	85 C0		STA C0	
0266	86 C1		STX C1	
0268	A9 11		LDA H#11	;CHANNEL 1 ADDRESS
026A	8D 01 A8		STA DRA	;INITIATE A/D CONVERSION
026D	A9 02		LDA H#02	
026F	20 7C 05		JSR SUBM	;COUNT(REF) - COUNT(0)
0272	A5 C0		LDA C0	
0274	A6 C1		LDX C1	
0276	85 A0		STA A0	;SAVE CORRECTED REF COUNT
0278	86 A1		STX A1	
027A	20 30 03		JSR RDADC	;READ CHANNEL 1 COUNT
027D	85 C0		STA C0	
027F	86 C1		STX C1	
0281	A9 02		LDA H#02	
0283	20 89 05		JSR CMPM	;IS COUNT(1) < COUNT(0)?
0286	10 08		BPL SKIP	
0288	A5 D0		LDA D0	;SET COUNT(1)
028A	85 C0		STA C0	; TO
028C	A5 D1		LDA D1	; COUNT(0).
028E	85 C1		STA C1	;
0290	A9 02	SKIP:	LDA H#02	
0292	20 7C 05		JSR SUBM	;COUNT(1) - COUNT(0)

at the selected input. The ramp-start input is then set high. This disconnects the input voltage from the ramp capacitor, which now discharges linearly at a controlled rate through resistors R1 and R2. When the ramp capacitor is discharged, the ramp-stop output goes low. Since the capacitor's discharge time is directly proportional to the input voltage, a counter running during the interval from the conditions ramp-start-high to ramp-stop-low will, at the end, contain a count that is proportional to input voltage.

In this circuit, a low-to-high transition of peripheral-port bit 4 triggers IC2, a 74LS221 monostable multivibrator. Its Q output goes high to clear the counter, while the \bar{Q} output holds the ramp-start line low, allowing the μ A9708 (IC1) to acquire the voltage from the selected channel. Upon timing out, IC2's outputs change states, raising the ramp-start line to a high logic level and turning on the counter. When the ramp-stop line goes low, the counting stops, and peripheral-port bit 6 goes high to signal the computer that the conversion is complete. The counter value is the useful output of the converter, and is retained until it has been read and the next conversion cycle has begun.

The clock, IC3, is a multivibrator whose frequency is set to about 1 MHz by the 100 pF capacitors, C6 and C7, and 6.8 k-ohm resistors, R8 and R9, for a 10-bit count. An 8-bit count is selected by replacing R8 and R9 with 27 k-ohm resistors. If the frequency-determining components are installed symmetrically on a header, as shown in figure 2, the 8- or 10-bit counts can be selected by simply unplugging the header and reversing it.

A ripple counter and a 16-bit output multiplexer, controlled by address lines A0 thru A3, complete the circuit.

Before the circuit is used, all unused analog inputs should be grounded and the reference voltage and ramp slope should be set. The 10 k-ohm potentiometer, R3, is first adjusted until the reference voltage at pin 8 of IC1 is exactly 3 V, as in-

COMING FOR JUNE See it at COMDEX
Booth 1632

The
Multi-User
system that is
COMPLETE
and ready to run

MULTI/os™

Multi Word Processing
Multi Data Entry
Multi Inventory Control
Multi Order Entry

With a **Shared** data base
of up to
975,000,000 bytes

InfoSoft
SYSTEMS INCORPORATED
10000 WILSON BOULEVARD
LOS ANGELES, CA 90024
(213) 868-7220

SciTronics introduces . . .

REAL TIME CLOCKS

with full Clock/Calendar Functions


The Worry-free Clocks for People
Who Don't Have Time to Worry!!

What makes them worry-free?

- Crystal controlled for high (.002%) accuracy
- Lithium battery backup for continuous clock operation (6000 hrs!!!)
- Complete software in BASIC-including programs to Set and Read clock
- Clock generates interrupts (seconds, minutes, hour) for foreground/background operation

Applications:

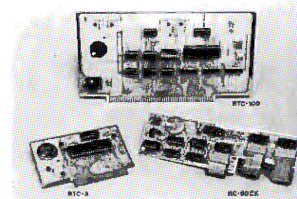- Logging Computer on time
- Timing of events
- Use it with the SciTronics Remote Controller for Real Time control of A.C. operated lights and appliances



Versions available for:

- S-100 bus computers **RTC-100 \$159**
- Apple II computer **RTC-A \$129**
- SciTronics RC-80 owners **RC-80CK \$109**

Send
Check or
money
order to:
SciTronics Inc.
523 S. Clewell St., P.O. Box 5344
Bethlehem, PA 18015
(215) 868-7220

Please list system with which you plan to use controller • Master Charge and Visa accepted. COD's accepted. PA residence add sales tax.

The reachable star.

The STAR puts a quality 300-bos RS232 modem within reach of the small computer user...the same modem selected by IBM, GE, RCA, and ADP. The price? Under \$200!

We've designed this compact modem with exclusive triple-seal acoustic cups, crystal controlled oscillator, and built-in diagnostics and indicators. It's packaged inside an attractive injection molded case...and we stand behind the STAR with a two year warranty!

STAR models are available that interface directly with RS232 machines such as APPLE, ATARI, and NORTH STAR or IEEE 488 machines such as the PET, and that operate with either U.S. or European frequencies.



Available throughout the U.S., Canada, and Europe. For information and nearest dealer, call (408) 734-9810 or TWX 910-339-9519.

PRENTICE

Prentice Corporation
266 Caspian Drive
Sunnyvale, CA 94086

indicated by an accurate voltmeter. Then the converter connected to the computer is run in a loop, repeatedly addressing and reading the reference voltage at address 7. The 50 k-ohm potentiometer, R1, is adjusted until the count is just under hexadecimal FF for an 8-bit count, or hexadecimal 3FF for a 10-bit count.

In normal use, the program must first configure the peripheral-port bits 0 thru 4 as outputs and bits 5 thru 7 as inputs, and it must clear bit 4. Voltage readings are taken by writing

the value of the channel address plus hexadecimal 10 to the peripheral port and then waiting until bit 6 goes high. The channel address should not be changed during this time. Reading of the counter data automatically clears peripheral port bit 4, enabling its low-to-high transition when the next address is written to the port. The counter is read a bit at a time by writing the address of the desired bit into the peripheral port, reading the port, and then left-shifting bit 7 (the counter data bit) into a register pair

Listing 2: RDADC, a 6502 subroutine to read data from the counter in the converter. The 16-bit counter value is returned in the accumulator and X register. Status bits reflect the condition of the high-order byte.

```

;          ***** READ A/D CONVERTER *****
;          THIS SUBROUTINE READS THE COUNTER OF THE A/D CONVERTER.
;          IT RETURNS THE HIGH-ORDER BYTE IN THE ACCUMULATOR
;          AND THE LOW-ORDER BYTE IN THE X REGISTER.
;
;          SCRATCH LOCATIONS USED: F0,F1
;
0330 A9 40   RDADC: LDA    H#40   ;LOAD MASK TO TEST BIT 6
0332 2C 01 A8 LP1: BIT     DRA    ;IS A/D CONVERSION COMPLETED?
0335 50 FB   BVC     LP1      ;IF NOT, LOOP UNTIL DONE
0337 A2 0F   LDX     H#0F      ;LOAD INDEX REGISTER/COUNTER
0339 8E 01 A8 LP2: STX     DRA    ;BIT ADDRESS
033C AD 01 A8 LDA     DRA      ;READ BIT
033F 2A      ROL     A         ;ROTATE ACCUMULATOR
0340 26 F1   ROL     F1       ;ROTATE MEMORY LOCATION F1
0342 26 F0   ROL     F0       ;ROTATE MEMORY LOCATION F0
0344 CA      DEX             ;
0345 10 F2   BPL     LP2      ;BRANCH IF POSITIVE
0347 A6 F1   LDX     F1       ;LOAD LOW-ORDER BYTE
0349 A5 F0   LDA     F0       ;LOAD HIGH-ORDER BYTE
034B 60      RTS

```

Reference Designation	Part
IC1	μA9708, A/D converter
IC2,IC3	74LS221, monostable multivibrator
IC4,IC5	74LS393, dual 4-bit binary counter
IC6	74150, 1 of 16 data selectors
IC7	74LS02, quad 2-input NOR gate
IC8	74LS08, quad 2-input AND gate
C1	0.01 μF, polyester
C2	0.02 μF, ceramic
C3,C4,C5	0.1 μF, ceramic
C6,C7	100 pF, ceramic
R1	50 k-ohm, 10-turn potentiometer
R2	47 k-ohm, 1/4 W, 5% tolerance
R3	10 k-ohm, 10-turn potentiometer
R4,R5	10 k-ohm, 1/4 W, 10%
R6	15 k-ohm, 1/4 W, 5%
R7	100 k-ohm, 1/4 W, 10%
R8,R9	6.8 k-ohm or 27 k-ohm, 1/8 W, 5%

Table 1: Parts list for circuit of figure 1. Capacitor C1 should be a low-leakage type. No precision tolerances are required.

or 2 bytes of memory that will contain the 16-bit count. The sequence is repeated for each bit, starting with the most-significant bit at hexadecimal address 0F and ending with the least-significant bit at address 00.

The most efficient operation will result when the analog-to-digital conversion is initiated at a point in the program that occurs a number of instructions before the voltage reading is required. The computer is then free to execute the intervening instructions before having to wait for completion of the conversion. The hand-assembled program segment, shown in listing 1, illustrates the use of the converter and the RDADC subroutine (see listing 2). Note the instructions inserted between the initiation of the conversion at hexadecimal address 026A and the reading of the output at address 027A.

A nonzero count is always obtained, even when reading 0 V. This count must be subtracted from the reference voltage and channel counts. Thus, the computation for a linearized and scaled voltage reading becomes:

$$V(i) = \frac{\text{Count}(\text{Channel } i) - \text{Count}(0)}{\text{Count}(7) - \text{Count}(0)} \times V_{\text{REF}}$$

where V_{REF} is the reference voltage.

Long-term drift effects are minimized by reading the zero and reference voltages each time a channel is sampled. When reading very small input voltages, the possibility exists that a channel count may be smaller than the zero count. The apparent instability resulting from this condition is avoided by simply setting the channel count equal to the zero count.

The uses for such a converter are many and diverse. For example, if you are an energy-conscious homeowner, you may wish to monitor temperatures throughout your home. Or, if you are an amateur horticulturist, you may wish to monitor light intensity and temperatures of air and soil to optimize growing conditions for plants or cuttings. Whatever the application, I hope that this converter, with its 8 bits of accuracy for table subscripts or 10 bits of accuracy for better resolution, will serve you well. ■

(212) 986-7690

MAIL ORDER ONLY

Micro Computer Your One Stop For... Quality and Huge Savings

DISCOUNT

Company

QUALITY • DELIVERY • SERVICE
60 E. 42nd St. Suite 411 New York, NY 10017


 <p>CENTRONICS CALL FOR PRICES</p>	<p>EPSON Call for Best Price & Delivery</p> 	 <p>COMMODORE</p> <p>16K - \$859 32K - \$1079 2022 - \$695 2040 - \$1079 8050 - \$1495 8032 - \$1495</p>																		
<p>ATARI 800—\$759</p> 	<p>MONITORS</p> <table style="margin: auto;"> <tr><td>Sanyo 9"</td><td>B & W —</td><td>\$180</td></tr> <tr><td>Sanyo 12"</td><td>B & W —</td><td>239</td></tr> <tr><td>Sanyo 12"</td><td>Green —</td><td>279</td></tr> <tr><td>NEC 12"</td><td>Green —</td><td>259</td></tr> <tr><td>BMC 12"</td><td>Green —</td><td>269</td></tr> <tr><td>Zenith 13"</td><td>Color —</td><td>379</td></tr> </table>	Sanyo 9"	B & W —	\$180	Sanyo 12"	B & W —	239	Sanyo 12"	Green —	279	NEC 12"	Green —	259	BMC 12"	Green —	269	Zenith 13"	Color —	379	 <p>DIABLO 630 \$ 2195</p>
Sanyo 9"	B & W —	\$180																		
Sanyo 12"	B & W —	239																		
Sanyo 12"	Green —	279																		
NEC 12"	Green —	259																		
BMC 12"	Green —	269																		
Zenith 13"	Color —	379																		

MAIL ORDER ONLY

Send Certified Check (Personal or Company Checks require 2 weeks to clear.)
We pay all shipping and insurance charges except items marked with asterisk.
VISA, MasterCard add 5% N.Y.S. Residents add appropriate sales tax.

*(DENOTES ITEMS SHIPPED F.O.B. NYC)

PHONE (212) 986-7690

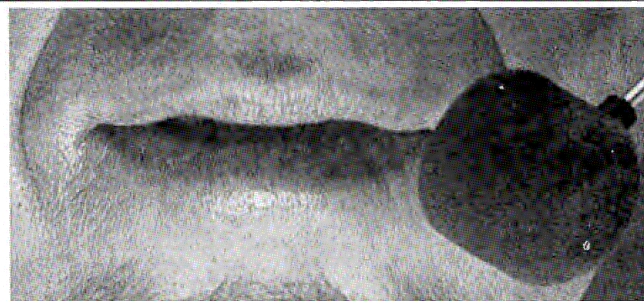

Spoken to your Apple® lately?

With the Heuristics™ 2000 speech recognition board, you can train your Apple computer to recognize 64 words or phrases of your choice (or multiples thereof). Any command for any application. The advanced Heuristics 2000, with microphone included, brings a whole new hands-off approach to data entry and program control—for a surprisingly low \$259. An optional head-set microphone (shown above) is also available.

TALK TO YOUR APPLE FOR ONLY \$259.

What's more, speech recognition is also available for S-100 computers, with our Heuristics 20S and 50 boards. The 2000 also makes a very practical starter system for the Heuristics 5000 and 7000 industrial/commercial speech recognition units. These commercial units start at \$2500.

So the next time you have data to enter, words to process or menus to select, don't work your fingers to the bone. Talk to your Apple instead.

HEURISTICS 2000

The talk of the computer industry.™

Heuristics, Inc., 1285 Hammerwood Avenue, Sunnyvale, CA 94086 • 408/734-8532