

Computer Communications Experiments

Marvin L. De Jong
Department of Mathematics-Physics
The School of the Ozarks
Pt. Lookout, MO

I. Introduction

This article describes a RS-232C interface circuit for serial input/output that can be used with any computer peripheral that uses such an interface. In this instance, the peripheral is a modem (NOVATION CAT) that can be used to transmit and receive data over telephone lines. Many modems require a RS-232C interface, hence the need for the circuit which in turn uses a 6551 ACIA (Asynchronous Communication Interface Adapter). The purpose of publishing this work is to find one or more persons who would be willing to experiment with computer communications over telephone lines. The article also describes some very simple software that can be used with a modem to transmit and receive messages over telephone lines. Later, more sophisticated load and dump routines can be written to transfer large amounts of data and/or programs from one user to another.

A true confession is that I am a beginner in the area of computer communications, and I would like to try some simple experiments before I fork-up a big subscription fee to one of the networks, only to find that my equipment or my understanding is inadequate. If you can obtain the necessary equipment and if you are in roughly the same position, write me a letter when you have said equipment operating and we will try to arrange a time to try our hardware and software on a telephone link. I might add that the software and hardware described here have *not* been tested, except in the "TEST" mode on my modem, in which case everything worked properly. I am aware that my routines are simple and slow, and I would welcome suggestions for improvement.

II. Circuits And Things

I sometimes wonder if there are any hardware enthusiasts like myself out there. You might let your editor/publisher know of your interests. My hardware fan club seems to be the null set, judging from the amount of mail I get. But here is another circuit even if no one ever builds it. You can always buy an

RS-232C interface anyway. The circuit is shown in Figure 1. It consists of three integrated circuits, a 6551 ACIA, a MC1489 RS-232 line receiver, and a MC1483 RS-232 line driver. The latter two circuits change the RS-232 signal levels to TTL levels, and TTL level signals to RS-232 signal levels, respectively. The 6551 ACIA operates at TTL levels (5 volts is logic one, zero volts is logic zero), while the modem operates at RS-232C signal levels (see Michael E. Day's RS232 Communications in COMPUTE!, September/October 1980, page 26). The power connections for the MC1488 and 1489 devices are given in Table 1.

Table 1. Power Connections for the RS-232 line driver and line receiver.

MC1488	Pin 1 = -12V	Pin 14 = +12V	Pin 7 = GND
MC1489	Pin 14 = +5V	Pin 7 = GND	

The connections to the left of the 6551 ACIA are made to the user's microcomputer system. Most of the signals are standard 6502 system bus signals, and require no explanation. Thus, address lines A0 and A1 are used to address the four registers of the 6551, and are connected to the register-select pins RS0 and RS1. (You will probably want to obtain a specification sheet from either Rockwell or Synertek when you get your 6551; in fact, I advise you not to build the circuit without a spec sheet.) The data bus connections are shown in Figure 1, as well as several of the 6502 control lines (R/W, θ_1 , RES, TRQ). A 1.8432 MHz crystal is also required. Still referring to the connections on the left-hand side of the 6551 in Figure 1, we are left with pins CS0 and CS1, the chip selects.

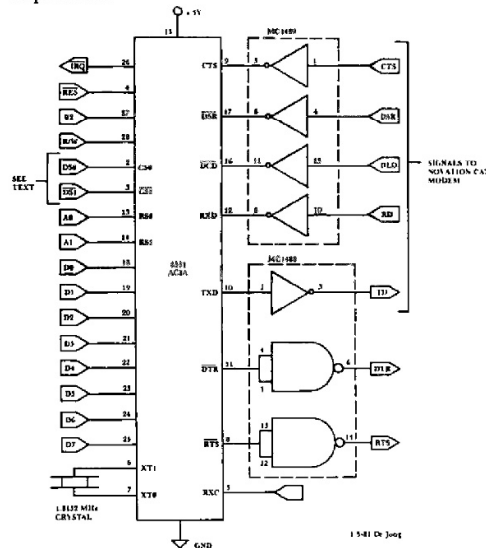


Figure 1. Circuit for the 6502-to-RS-232C-to-Modem interface.

The chip select pins must be controlled by the address decoding circuitry in your microcomputer system, or else you must add your own address decoding circuitry to produce the chip select pulses. Since I have an AIM 65 system, I used one of the device selects available on the expansion connector, namely DS9. This signal is active at logic zero for any address in the range \$9000 to \$9FFF. It was tied to CS1, the active-low chip select. If CS0 is tied to +5V, then the registers on the 6551 are selected by any address of the form \$9XX0 to \$9XX3 where XX is a "don't care" number. Thus, in the programs you will find the four 6551 registers selected by addresses \$9400 to \$9403. If you have a SYM-1 you can make use of device select DS18. If you have an Apple you must provide your own decoding circuitry. The reason lies in the fact that the device select pulses generated by the Apple for the peripheral cards have been logically ANDed with $\bar{\theta}_0$, and consequently they do not become active early enough in either the READ or WRITE cycles to work with 6500 family devices. For a discussion of address decoding see De Jong's ⁽¹⁾ book. The circuits are generally quite simple. In the case of the Apple, I suggest trying an inverter and a 74133 to generate a device pulse for say \$C08X, and perhaps a 74LS245 as a data bus buffer. Try an inverted $\bar{\theta}_0$ to replace $\bar{\theta}_1$. My familiarity with the PET does not justify suggesting any circuits, but I am sure the 6551 can be interfaced to a PET.

We turn next to the signals on the right-hand side of the 6551 as it is shown in Figure 1. The RXC input to the 6551 is the easiest to explain because it is not used in this application. The remaining pins have labels that are almost identical to the RS-232C designations. In fact, the only one that is different is the DCD which is simply CD (Carrier Detect) in RS-232C lingo. Again, refer to references (2) and (3) for a more complete explanation of the RS-232C interface.

Although the signal designations on the 6551 ACIA are almost identical to the RS-232C labels, the signal levels are not, and some arrangement must be made to transform the TTL levels of the 6551 to the RS-232C signal levels. We chose to use integrated circuits designed expressly for that task, namely the 1488 and the 1489 line driver and line receiver. Note that the 1488 requires a positive and negative supply voltage as well as ground. Also, the RS-232C ground (pin 7 on the DB-25 connector) should have the same ground as the 1488 and the 1489. The connections in Figure 1 that are found on the right-hand side of the figure made up a rather complete RS-232C serial interface that may be used to interface to a variety of peripheral devices. Furthermore, the fact that the data format and Baud rate of the 6551 are under the programmer's control makes this an extremely flexible RS-232C interface.

Since computer communication by telephone is

the subject of this article, a modem is required.

There are a variety of modems with RS-232C interfaces on the market and we do not wish to make any recommendations about them. I purchased a Novation Cat because that appears to be one of the more popular devices. Skyles Electric Works and other advertisers in COMPUTE! offer modems for sale. In any case, my Novation Cat requires the signals designated in Figure 1 in addition to the signal ground. Other modems may require the DTR and RTS signals so we have shown the correct TTL-to-RS-232C interface in the event you may need these signals.

This completes our description of the circuit and we turn next to a simple program that is supposed to allow communication to take place using the 6551 ACIA.

III. A Simple Communications Program

A program that was designed to allow two people to communicate over telephone lines with their computers is given in Listing 1 and a flowchart is shown in Figure 2. This program is very simple and very slow, and it is offered here merely as a way to test the circuit, the program, and the modem. Eventually, one would want to construct more elaborate routines to transfer information quickly. Our interest here is in experimenting for the sake of learning. Hence there is no necessity for encryption devices, bells, whistles or even parity checks.

Here is how it is supposed to work. The caller loads the program and places his modem in the **originate mode with full-duplex operation** selected. He loads the indirect jump location with the vector \$0F13 so that after the program is begun, his program will go to the transmit loop.

He makes the telephone call to an anxiously awaiting friend who also has this interface and this program operating. The friend has loaded the indirect jump location at \$0000 and \$0001 with the vector \$0F26 (remember, \$26 goes in \$0000 and \$0F goes in \$0001). The friend has also placed his modem in the **answer mode with full-duplex operation** selected. After an informal chat, both friends put their modems into action by placing the handset into the muffs (assuming acoustic modems). The originator begins to type a message.

He ends his part of the message with an 'EOT' character (Control D on your keyboard). While he is transmitting, the friend's program echoes the message back to the originator where it is read and printed by the computer. It's nice to see what you have said, and to know that it got where it was going with no mistakes. When an 'EOT' character is sent, it automatically transfers the originator's program to the receive loop and the receiver's program to the send loop, giving him a chance to retaliate. Having made no visible symbol to indicate when this changeover takes place, may I suggest sending a

0FE0 AD 01 94	RCV DAT	LDA STATUS	Read the status register to see if a word
0FE3 29 08		AND #08	has been received, otherwise wait for one.
0FE5 F0 F9		BEQ RCV DAT	
0FE7 AD 00 94		LDA RCVRG	Get the word from the receiver register.
0FEA 60		RTS	Return to the calling program.
0FF0 48	TXMIT	PHA	Save the accumulator temporarily
0FF1 AD 01 94	WAIT	LDA STATUS	Is the transmitter register empty?
0FF2 29 10		AND #10	No. Wait until it is.
0FF6 F0 F9		BEQ WAIT	
0FF8 68		PLA	Get the character from the stack.
0FF9 8D 00 94		STA TMTRG	Store it in the 6551 transmit register.
0FFC 60		RTS	Return to the calling program.

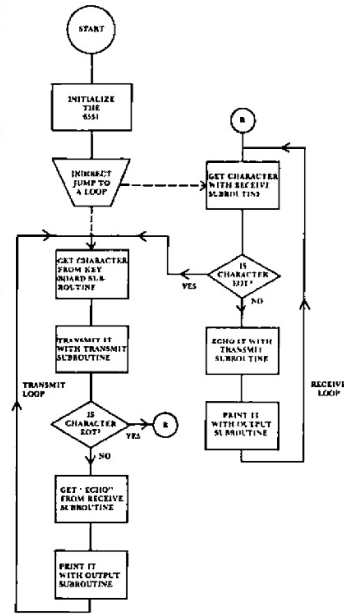


Figure 2. Flowchart of the Transmit/Receive Program. See text for details.

So back and forth the conversation goes. Once you have the transmit option in your hands nothing can stop you from talking until you send an 'EOT' and give your friend a chance to say something. Clearly, the program lacks a certain elegance (it may

Study the flowchart and the program listing. The program begins by initializing the 6551. An eight-bit word (TTY compatible) is used, with the parity check disabled, and one stop bit is sent. The Baud rate chosen here is 110, but it should be possible to go to 300 Baud. Both participants must have

the same rate. Next, the program jumps to either the receive loop or the transmit loop depending on the vector loaded into \$0000 and \$0001. This was a crude way to start, but it should work.

In the transmit loop the program first waits for an input from a keyboard read routine. The address in the program belongs to an AIM 65 monitor subroutine that returns the ASCII representation of the depressed key in the accumulator. This character is sent by calling the transmit subroutine which loads the 6551 transmit register with the character. The 6551 takes over and sends the character. The program then waits for the character to be echoed from the other telephone and computer. The echoed character is printed to make sure that what was sent was actually received. Then control returns to the keyboard subroutine to wait for the next character to be sent.

In the receive loop the program jumps to the receive subroutine that watches the 6551 until a character is in the receive data register. If this character is an 'EOT' then control goes back to the transmit loop and you may begin transmitting. Otherwise the received character is immediately echoed back to the sender and also printed with your OUTPUT routine. Again, the address of the OUTPUT routine in Listing 1 belongs to an AIM 65 subroutine. Both the KYBD and OUTPUT subroutines must be supplied by the user's monitor or the user himself, otherwise the program in Listing 1 is complete.

While in the transmit loop, the selection of the 'EOT' character by the sender will automatically transfer control out of the transmit loop into the receive loop. Note again that no bells or whistles have been programmed to occur when you send an 'EOT' character, so if you are transmitting you better let your friend know you are passing control of the system to him.

So hopefully all this will work. If it doesn't you have only me to blame, and I will not assume the cost of your labor or your equipment to conduct this experiment. Perhaps it would be best if you waited until someone else tried it; think it over before you take the plunge.


Besides, my next project is to launch a 6502 Communications Satellite using dynamite in my back yard and you may want to save your money to buy shares in that enterprise.

References

1. De Jong, Marvin L., *Programming & Interfacing the 6502, With Experiments*, Howard W. Sams & Co., Inc. Indianapolis, 1980.
2. Day, Michael E., "RS232 Communications," *COMPUTE!*, Sept/Oct 1980, 26.
3. Ciarcia, Steve, "I/O Expansion for the TRS-80," *BYTE*, June 1980, 42.

©

TAKE THE ? OUT OF SOFTWARE BUYING

 

MICRO CO-OP

- Objective reviews and comparisons of software available for your computer
- Co-op prices

Call or write for more information
and a free Buying Guide/Catalog
MICRO CO-OP
Post Office Box 432
West Chicago, Illinois 60185
(312) 231-0912

Include your name, address, and the type of computer you own.

Selectric[®] Interface System


EASILY interfaced to any IBM Selectric I, II, or III.

STOP spinning your wheels. Letter quality at an affordable price.

CONNECTS via Parallel or RS-232, accommodates varied handshaking.

ONLY \$575 to \$599. Dealer inquiries invited.

NEW design provides added features.

 

ESCON Products, Inc.
12919 Alcosta Blvd.
San Ramon, Ca., 94583
(415) 820-1256