

KIMCTR

This KIM-1 frequency counter/timer can be used with any micro with comparable features.

Clement S. Pepper
3270-96 Caminito East Bluff
La Jolla CA 92037

A low-cost frequency counter is readily constructed from an LSI counter IC and your KIM-1. KIM controls the counter, generates the one-second time base and displays the count.

If you don't have a KIM-1, read on anyway... the program is adaptable to any micro-computer on-a-board having comparable features. The prime requirements are ad-

dressable I/O ports and a hexadecimal display that can be controlled by your program.

The LS7030,¹ an 8-decade multiplexed MOS up counter, performs the counting. In addition to the counter and KIM, the design includes an input stage with threshold adjustment. I have also added circuitry for time mode measurement of both positive and negative pulses, with the widths displayed in microseconds for up to one second. I/O buffers are also provided—both to match the ports to the counter and to give protection, just in case... The KIM-1 supply provides dc power.

Features

The frequency mode provides for two ranges: 1 Hz to 1 MHz with 1 Hz resolution or 10 Hz to 10 MHz with 10 Hz resolution. The LS7030 is specified to 5 MHz so the full x10 range may not be realized. If desired, the input can include pre-scaling, which I have not included. The

time mode provides a measure of pulse width; positive- or negative-going pulses are switch selectable. The input may be a single pulse or a wave train. The sum of the positive and negative widths in a uniform train is the period. Resolution is 1 usec.

KIM provides full control of the counter via four I/O ports. Six digits of frequency or time are displayed on KIM's seven-segment readout. The display program is also the one-second time base for the frequency measurement.

Fig. 1 is a function diagram of the counter/timer. The basic functions are a high-impedance input stage with an adjustable threshold for sensitivity control, capture circuitry for the pulse width measurement, the LS7030 counter and KIM-1.

The LS7030 Counter IC

Fig. 2 is the internal circuitry of the counter. Key features of the LS7030 include dc to 5 MHz counting, multiplexed BCD and seven-segment outputs, single-power supply operation at 4.75 V dc to 15 V dc, high noise immunity, counter input latches and leading zero blanking.

The count input ripples through eight BCD counter

stages. Each stage is provided with a 4-bit latch. Data stored in the latches is connected to the internal BCD bus by multiplexed switching. The switching sequence is controlled by a scan counter and decoder. The BCD lines are internally decoded to provide seven-segment outputs. Blanking for leading zero suppression is implemented internally.

All decades are reset to zero when RESET is brought low for a minimum of 4 usec. Contents of the counter are transferred to the latches when the LOAD signal is brought low for a minimum of 4 usec and kept low until a minimum of 17 usec has elapsed from the negative edge of the preceding count pulse. Raising the LOAD signal stores the counter data in the latches.

The counter scans from the most significant digit (MSD) to the least significant digit (LSD). When SCAN RESET is brought high, the scan counter is forced to the MSD state. The scan counter decrements one count on each negative transition of the SCAN INPUT.

Leading zero blanking is employed. At the start of each MSD-to-LSD scan, the seven-segment outputs are held low until a nonzero digit appears on the BCD bus. The display un-

 


Photo 1. The first pulse of the train displayed in the lower trace has been detected and is displayed in the upper trace.

 


Fig. 1. KIMCTR function diagram.

blanks on the LSD; a zero is displayed when there is no counter input. A comment: In this program the zero is displayed on the x1 range; the entire display is blank on the x10.

All inputs are TTL compatible with +5 V operation. Outputs are CMOS compatible.

Counter Design

The complete circuitry for the counter/timer is shown in Fig. 3. The signal connects to the non-inverting input of an LM339 comparator. Input threshold is controlled by the setting of R4. The values shown yield a threshold of 0 to +2 volts. Other values may be chosen to extend the range if desired. In the frequency mode the signal is conducted through gates U1A and U1C to buffer U6A. The buffer is necessary because all the front-end circuitry operates from +12 V dc, with the counter and buffer at +5 V dc.

If frequency counting is all you need, ICs U1, U2, U3 and U4 will be omitted, along with comparators A1B, A1C and the switching.

The blanking output to PB0 shown is not used. Initially I thought it would be needed. PB5 and PB7 are shown grounded just to keep them from floating; they have no function.

Timer Circuitry

In the time mode a single pulse is plucked from the incoming train to enable gate U1B. A second input to this gate is the 1 MHz clock from KIM. This signal is counted for the duration of the pulse high time; thus the width is displayed in usec.

Now let's back up to see how the gating pulse is selected. Observe that the counter reset pulse is brought around to comparator A1C. This effects a translation from 5 volt logic to 12 volt. The trailing edge of the counter reset from KIM clocks the "D" flip-flop U2A. In so doing it places a "1" at the D input of U2B.

The next positive-going transition at pin 11 of U2B will set the Q output and enable

gate U1B. U2A is reset at this time also. With the polarity switch in the "POS" position (as shown), this is the leading edge of an incoming pulse. EX-OR gate U4B is an inverter. The trailing edge of the pulse clocks U3A, which resets U2B, thereby inhibiting the gate and also resetting U3A. The operation of this circuit ensures that one complete pulse, and one pulse only, enables U1B for each counting cycle.

You can see the action in the scope traces in Photo 1. The lower trace is the incoming

train; the upper shows that the first trace following reset has been captured.

Single pulse inputs will be accurately timed provided they occur within the one-second counting interval. With S2 in the "NEG" position, the negative portion of the wave is timed. If the pulse train is uniform, the sum of the two times is the period for one complete cycle.

The pulse width displayed corresponds to true width only for rectangular waveform inputs. For other waveforms the

width measured is dependent on the waveshape and the threshold setting because of comparator squaring.

With the threshold at zero the displayed width is that of the entire positive or negative portion of the wave. This is illustrated in the scope traces in Photos 2-4. In Photo 2 the threshold is at zero; the comparator output is very nearly a square wave. The input is only 50 mV (RMS), which is about the ultimate sensitivity.

Increasing the input by a factor of 10 (Photo 3) with the

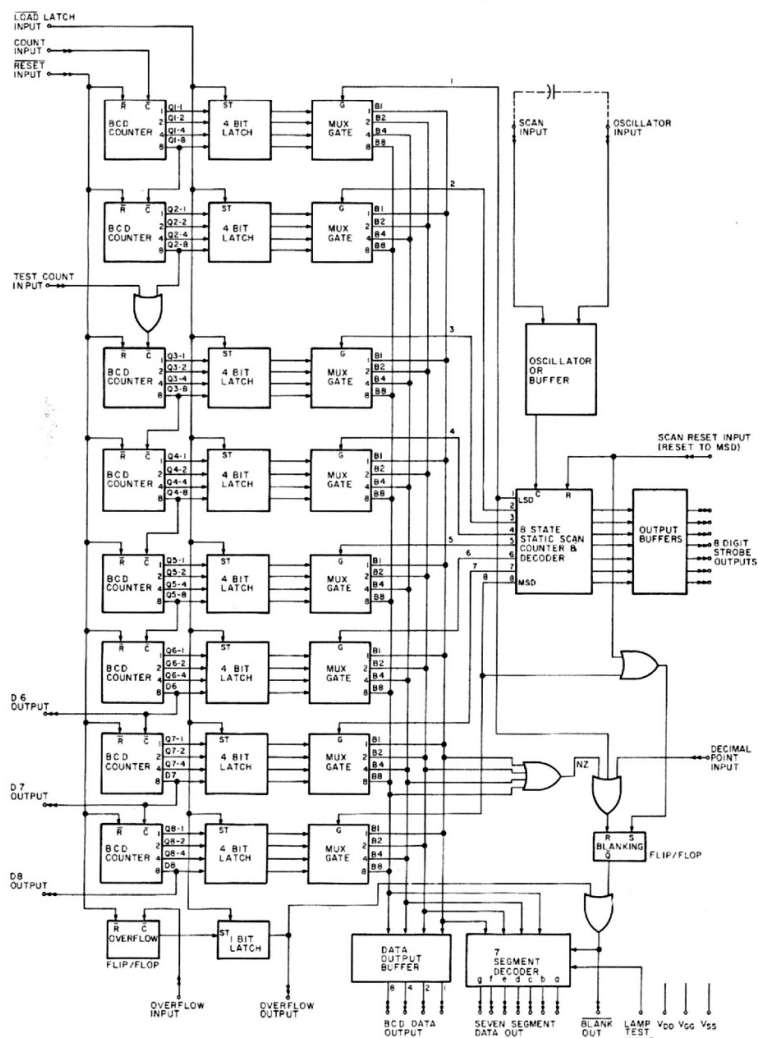


Fig. 2. Internal circuitry of the LS7030 counter. This device is ideally suited for microcomputer control.

 


Photo 2. 50 mV (RMS) sine wave and comparator output. Threshold is at 0 V; output is nearly square.

 


Photo 3. Signal increased to 500 mV (RMS); no change in threshold. Comparator output unchanged.

threshold unchanged shows little change in the output. In Photo 4 the threshold has been upped to 1.2 volts with a resulting drastic change in the output.

In Photo 5 the upper trace is the input, at 87 kHz. The measured width, that of the

lower trace, matches the width of the input to within the 1 usec resolution of the measurement.

Counter Control

Reference to Fig. 3 shows four control inputs to the LS7030: LATCH, SCAN RESET, SCAN INPUT and CTR RESET.

Control is exercised by KIM via I/O ports PB1-4. The 7408 AND gates are there to isolate the ports. Control waveforms and timing are shown in the diagram of Fig. 4. Numbers on the traces are time in usec.

Assume that the counter has accumulated data and it is time

for KIM to take a collection. The initial step is to store the counter data in the latches and to reset the scan to the MSD. These two operations are performed simultaneously. Eighteen usec were allocated to assure a valid data store.

The SCAN INPUT is next

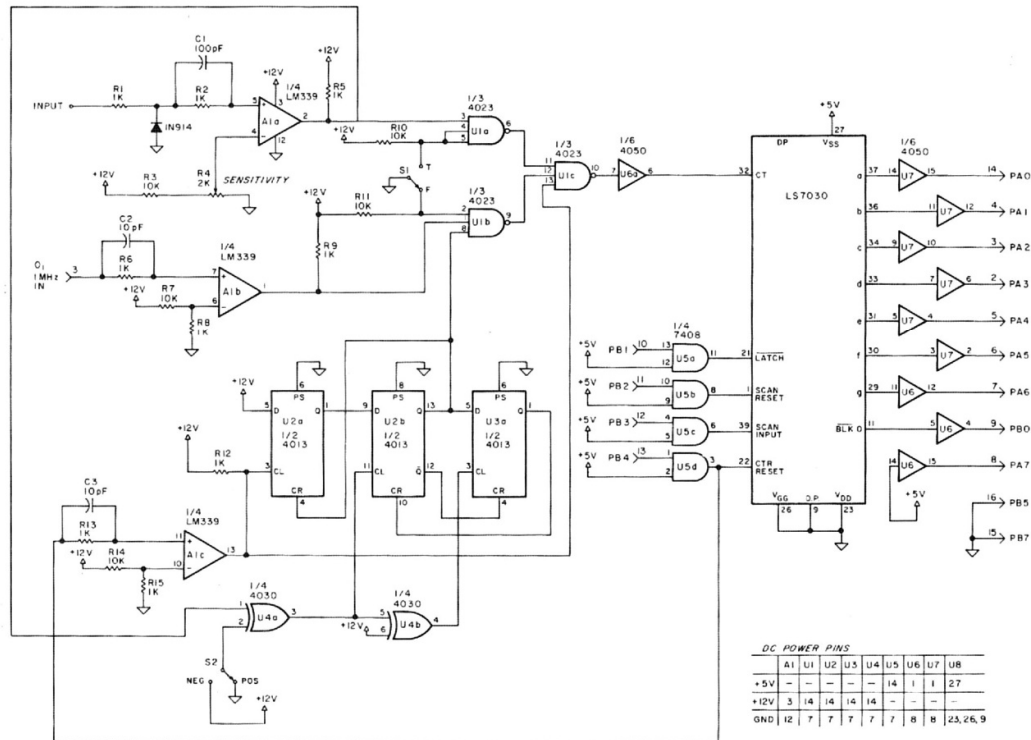


Fig. 3. Complete circuit diagram of the frequency counter/timer.

 


Photo 4. Threshold increase to 1.2 V narrows output pulse. Period is still the sum of positive and negative portions of output.

decremented to digit 7. Decrement occurs on the negative edge at 28 μsec . This diagram is for the x1 range, decade 7 is not read and a second decrement is made. Twenty-one μsec are absorbed to read and store the data from decade 6. The operation repeats until decade

1 has been read and stored. At 206 μsec the counter is reset, and 12 μsec later counting is resumed for the next update.

 


Fig. 4. KIMCTRO control timing for x1 measurements. Numbers are time in μsec .

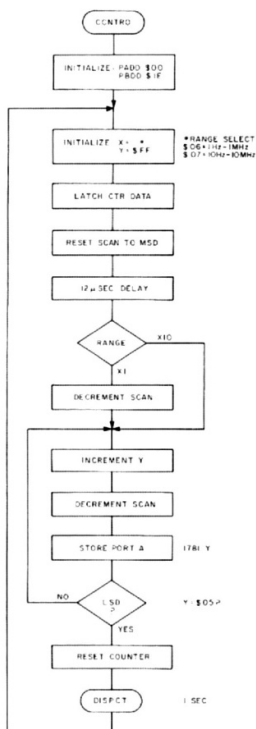


Fig. 5. CCNTRO flowchart.

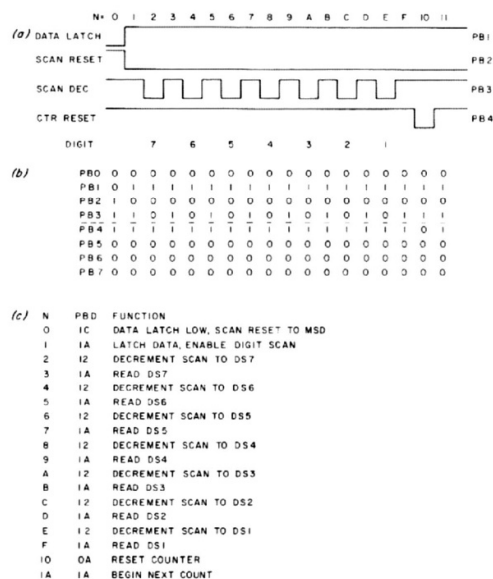


Fig. 6. (a) Sequence diagram. (b) Binary tabulation. (c) Code assignment and functions. This is the format I employ to assure true and complete I/O coding.

A flowchart for the control routine, CCNTRO, is provided in Fig. 5. The program is listed in Program A. Fig. 6 shows the sequence diagram and coding tables that I used to write the I/O instructions. I am not going into any detail on these as they are self-explanatory from the preceding descriptions after a bit of study. However, should you have any difficulty with these or any part of the system, send me a query with an SASE and I'll do my best to provide an answer.

Display and Timing

Subroutine DISPCT (Fig. 7) generates the six-digit display. The program has two delay loops (1 and 3) adjusted to yield the required one-second time base.

I suppose I could have uti-

lized KIM's SCANDS routine, but I preferred to develop my own. It is a routine I use, with variations, for other things I also do with KIM.

The seven-segment data is read out by port A I/O during the CCNTRO routine and stored in locations 1781-86. The digit select codes are stored in locations 1787-8C; be sure to enter these with the program. Port A segment coding is illustrated in Fig. 8. The listing for DISPCT is provided in Program B.

Construction

I assembled all the circuitry on pegboard; the parts layout is

 


Fig. 8. Seven-segment display coding for Port A. PA7 is held high.

 


Fig. 7. DISPCT flowchart.

0300	A9 00	INIT	LDA #500	
0302	8D 01 17		STA PADD	PORT A DIR
0305	A9 1E		LDA #51E	
0307	8D 03 17		STA PRDD	PORT B DIR
030A	A2 06	BEGIN	LDX #506	\$06=X1, \$07=X10
030C	A0 FF		LDY #5FF	
030E	A9 1C		LDA #51C	
0310	8D 02 17		STA PRD	LATCH LOW; SCAN RESET
0313	EA		NOP	DELAY
0314	EA		NOP	
0315	EA		NOP	
0316	EA		NOP	
0317	EA		NOP	
0318	EA		NOP	
0319	A9 1A		LDA #51A	
031B	8D 02 17		STA PRD	LATCH DATA
031E	E0 07		CPX \$07	X10 SELECT
0320	F0 0A		REQ LOOP1	
0322	A9 12		LDA #512	
0324	8D 02 17		STA PRD	
0327	A9 1A		LDA #51A	
0329	8D 02 17		STA PRD	
032C	C8	LOOP1	INY	BEGIN SCAN AND READ
032D	A9 12		LDA #512	
032F	8D 02 17		STA PRD	
0332	A9 1A		LDA #51A	
0334	8D 02 17		STA PRD	
0337	AD 00 17		LDA PAD	
033A	99 81 17		STA Y	STORE SEG CODE
033D	C0 05		CPY \$05	
033F	D0 EB		BNE LOOP1	NEXT DECADE
0341	A9 6A		LDA #50A	
0343	8D 02 17		STA PRD	RESET COUNTER
0346	EA		NOP	DELAY
0347	EA		NOP	
0348	EA		NOP	
0349	A9 1A		LDA #51A	
034B	8D 02 17		STA PRD	RESUME COUNT
034E	20 A0 17		JSR DISPC	DISPLAY COUNT
0351	4C DA 03		JMP BEGIN	

shown in Fig. 9. For connection to KIM, I hacksawed an AP Products #248-L terminal strip, seen in the upper right corner. Connection to KIM is by homemade ribbon cables, which connect at the far end to a similar strip. I brought out all of my KIM circuits to terminal strips for ready access when needed.


17A0	A9	7F	DISPLA	LDA #57F	
17A2	8D	41 17		STA PADD	KIM'S DISPLAY
17A5	D8			CLD	
17A6	A9	FF		LDA #5FF	
17A8	85	10		STA	LOOP 3 INDEX
17AA	EA			NOP	DELAY
17AB	E6	10	LOOP3	INC	
17AD	EA			NOP	DELAY
17AE	A2	00		LDX #506	LOOP 1 INDEX
17B0	90	06		LDY #506	LOOP 2 INDEX
17B2	A9	80	LOOP2	LDA #580	
17B4	8D	40 17		STA SAD	BLANK DISPLAY
17B7	B9	86 17		LDA Y	
17BA	8D	42 17		STA SBD	DIGIT STORE
17BD	B9	8D 17		LDA Y	
17CD	8D	40 17		STA SAD	SEGMENT STORE
17C3	E8		LOOP1	INX	
17C4	E0	F6		CPX #5F6	
17C6	D0	FA		BNE LOOP1	TIME DELAY
17C8	83			DEY	
17C9	C0	00		CPY #500	
17CB	D0	E5		BNE LOOP2	NEXT DIGIT
17CD	A6	10		LDX	
17CF	EA			NOP	FILLER
17D0	E6	5B		CPX #5B	
17D2	D0	D7		BNE LOOP3	TIME DELAY
17D4	60			RTS	RETURN TO CONTR

Display Data			
DIGIT	LOC	CODE	LOC
6	1786	13	178C
5	1785	11	178B
4	1784	0F	178A
3	1783	0D	1789
2	1782	0B	1788
1	1781	09	1787

Thus, with the program stored on cassette tape, it takes but a few minutes to have my KIMCTR perking.

Suppose you have some monostables on hand, perhaps from surplus or pulled from an ancient PC board, and you wonder if they are any good. Or perhaps you have a critical timing requirement and want to adjust the output pulse just so.

 This project is inexpensive and easy to complete. With the foregoing materials and a little time on your part, you'll soon have a micro-controlled frequency counter/timer. ■



TIMING EQUATION IS:
 $t_w = 693 RC$
 LET: $C = 1 \mu F$
 $R = 33 K\Omega$
 THEN $t_w = 2287 \mu s$
 OBSERVED = $2849 \mu s$
 TOLERANCES DO TAKE THEIR TOLL

Fig. 10. KIMCTR provides an accurate indication of monostable pulse width.