

# Super Cheap 2708 Programmer

*The advantages of programming your own 2708s are many. This easy to build programmer enables you to do the job—inexpensively.*

As a KIM owner, I have spent many enjoyable hours running and programming my micro. But as I wrote more programs, I noticed that some of the subroutines were used over and over in different programs. I began looking for a suitable PROM on which to store them. The price and availability of the Intel 2708 PROM were attractive, so I looked for a programmer. Since there were no 2708 programmers compatible with KIM, I sat down, equipped with the *Intel Memory Design Handbook*, a prototyping board and some components, and made one.

## Software

In theory, the 2708 PROM has a few simple requirements for entering data. A blank or erased 2708 has all bits in the high, or 1, state. Information is entered by selectively programming 0s into the desired locations. To enter data, the  $\overline{CS}/\overline{WE}$  pin is raised to +12 volts to put the chip into the programming mode, the address of the word is selected and the data word is presented to the data pins.

After the data has settled ( $10^{-9}$  sec.), a programming pulse

of +26 volts at 20 mA is applied to the programming pin. The next address is then selected and the process continued until

all addresses have been programmed. This is defined as one programming loop.

To determine the number of

programming loops required to ensure valid data entry, use the following formula:  $N \times t_{pw}$  greater than 100 msec, where N is the number of programming loops,  $t_{pw}$  is the programming pulse width and can be varied from 0.1 to 1.0 msec. For rapid programming,  $t_{pw}$  should approach one msec. This then requires 100 programming loops; the time required for complete

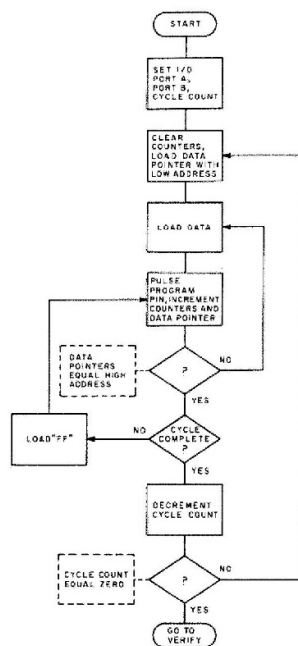


Fig. 1. Flowchart of main program.

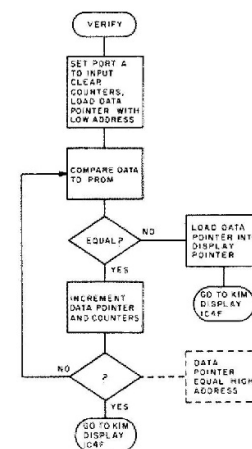


Fig. 2. Flowchart of verify program.

programming of 1K bytes is 1024 addresses times 1.0 msec times 100 programming loops, or about 103 seconds.

For KIM to perform the programming, it must control ten address lines, eight data lines, CS/WE and programming pins. To do this directly KIM would have to be able to latch 20 I/O lines, but since the addresses are stepped through sequentially and completely, counters can be used to provide the address. Then KIM can use two lines to control the counters and a third to sense the end of the programming loop.

Since KIM has 15 I/O lines, this is perfectly adequate. The counters selected were 74193s because their pin-out gives a simple PC board layout; but any binary counter could be used.

The I/O port is connected to the up-count, the clear and the output of the 11th counting stage. The program pulses the clear, then toggles the up-

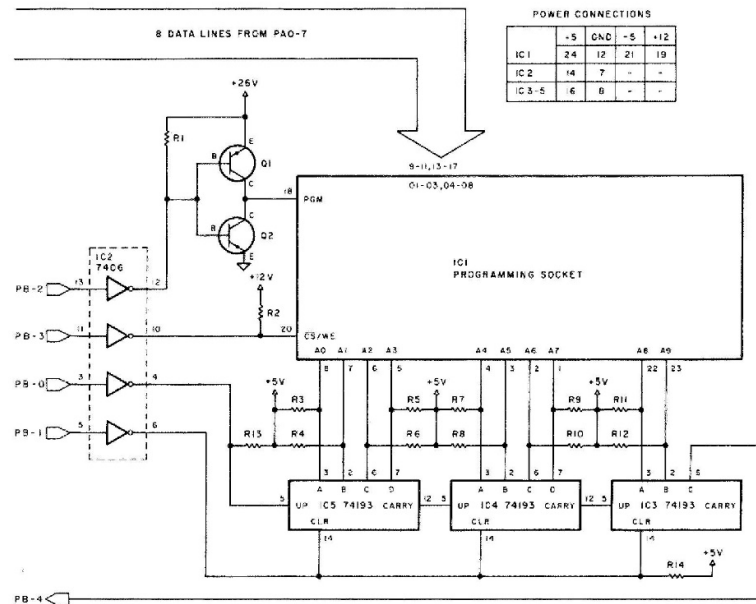


Fig. 3. Schematic diagram of programmer.

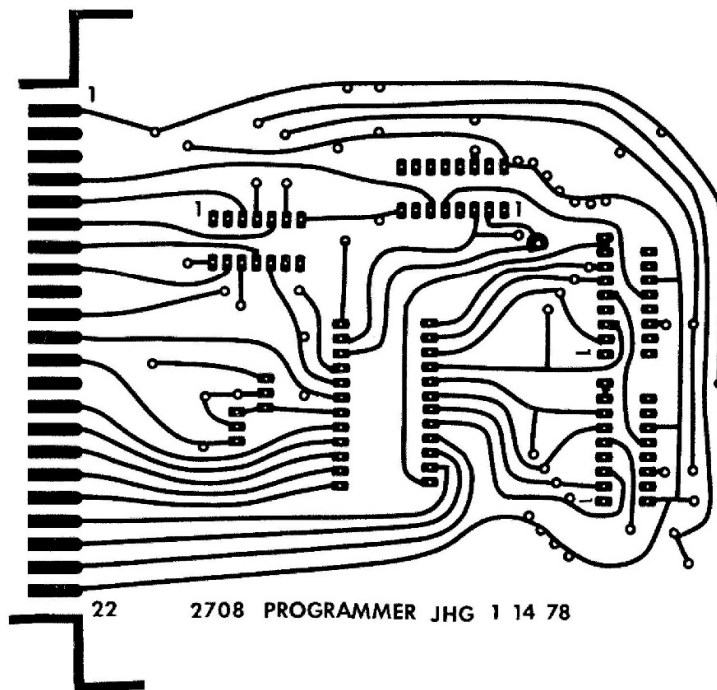


Fig. 4. Foil pattern for the PC board.

Model	Power Rating	Time of Exposure
S-68	12000uW/cm <sup>2</sup>	10 min.
S-52	12000uW/cm <sup>2</sup>	10 min.
UVS-54	5700uW/cm <sup>2</sup>	30 min.
R-52	13000uW/cm <sup>2</sup>	10 min.
UVS-11	5500uW/cm <sup>2</sup>	30 min.

All exposures are at a distance of one inch with the filter removed.

Table 1. Exposure guide for Ultra-Violet Products lamp. (Ultra-Violet Products, Inc., 5114 Walnut Grove Ave., San Gabriel CA.)

count and tests the 11th stage output. When the end of the programming loop is detected, the counters are cleared and

the cycle register, 00EE, is decremented (Fig. 1 is a flow-chart of this main program).

To control the CS/WE and programming pins, the lines are buffered with a 7406 (hex inverter with 30 volt open collectors). The programming pin requires a source of 26 volts at 20 mA and a sink of 1 to 2 mA, so push-pull transistors were used to control the actual input to the programming pin.

The program (listed in Program A) uses 00E7 through 00EE as address and counting registers on page zero and it occupies an additional 184 bytes of memory—either RAM or ROM. As written, it occupies page zero, which permits any RAM over 0200 as the source of data. It exits to the KIM monitor at 1C4F.

The body of the program consists of: an initialization routine that sets up the I/O ports, data pointer and cycle count; presentation of the data word and programming pulse; incre-

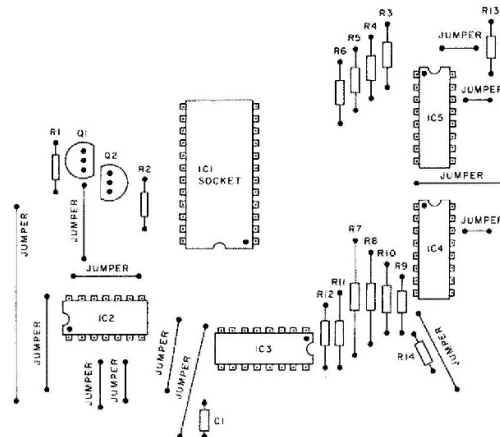


Fig. 5. Component placement.

IC1	2708 socket
IC2	7406 hex inverter (O.C.)
IC3-IC5	74193 binary counter
R1-R14	4.7k Ohm 1/4W resistor
C1	0.1 uF capacitor
Q1	2N222 or 2N3904
Q2	2N3906

Table 3. Parts list.

Programmer	
1	GND and KIM A-1
2	N.C.
3	N.C.
4	KIM A-13
5	KIM A-9
6	KIM A-10
7	KIM A-12
8	KIM A-11
9	N.C.
10	-5 volts
11	+12 volts
12	+26 volts
13	N.C.
14	KIM A-8
15	KIM A-7
16	KIM A-6
17	KIM A-5
18	KIM A-2
19	KIM A-3
20	KIM A-4
21	KIM A-14
22	+5 volts

Table 2. Connector assignments.

menting the counters and data pointer; testing for last data entry; testing for complete programming loop; and testing for end of programming.

When programming is completed, the routine jumps to a verify loop that compares the PROM contents to the data (see flowchart in Fig. 2). When the

number of data words is less than 1024, the program enters FF into the remaining addresses. This permits additional entries to be made at a later date.

During verification, if an error is detected, the program jumps to the KIM monitor and displays the address of the error. Complete programming takes just under two minutes. Additional data can be entered into addresses containing FF, but all previous data must also be entered. All addresses must be programmed during each programming cycle.

The 2708 PROM can be erased by exposure to ultra-violet light at a wavelength of 2537 Å. The recommended dosage is 10 Watt-seconds per square centimeter. This can be determined by a UV meter or by following the exposures given in Table 1.

#### Hardware

A schematic of the programmer is shown in Fig. 3. The layout shown in Figs. 4 and 5 is a minimum hardware layout using a single-sided PC board

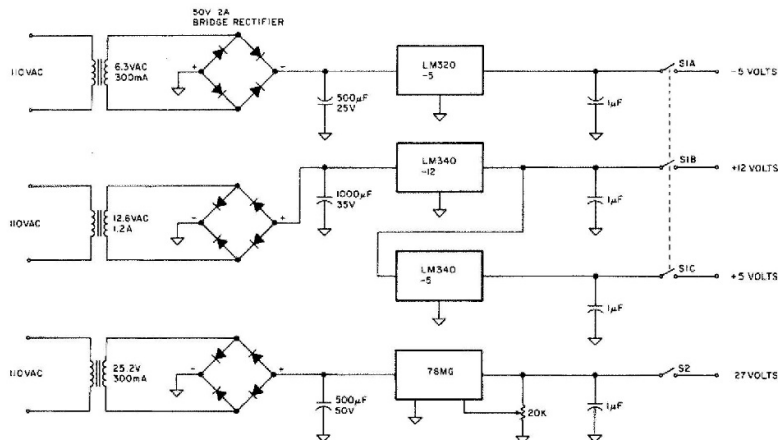


Fig. 6. Power-supply diagram. Adjust the output of the 78MG to give 26 volts after the drop across Q1.

with jumpers. It connects to the application connector supplied with KIM and the power supply. KIM's peripheral port A supplies the data to be entered; port B is used to control the counters and programming lines.

PB-0 is used to increment the counters, while PB-1 clears them. PB-2 controls the programming pulse and PB-3 controls  $\overline{CS}/WE$ . PB-4 is used to sense the completion of the programming loop by detecting a high on the C output of the high-order 74193. PB-5 and PB-7 are not used. The interface connections are shown in Table 2. Pull-up resistors are used on the TTL outputs to ensure that the logic levels required by the 2708 inputs (3.0 volts,  $V_{IH}$ ) are met.

The programmer requires four voltages, in addition to the 5 volt supply for KIM; the 2708 requires a -5 volt supply at 45 mA, +12 volts at 65 mA and +26 volts at 20 mA. The diagram in Fig. 6 illustrates a suitable supply. The power for the programmer should be controlled separately so the programmer can be turned off when the PROM is being inserted or removed.

#### Programming Procedure

1. Turn off all power. Then plug the programming board into the application connector on the KIM. Insert the PROM to be programmed into the 24-pin programming socket. Check the orientation to make sure that the number one pin is in the proper alignment.

2. Turn on the power to KIM, enter the PROM programming routine and the appropriate data. Make sure that the programming routine and the data have been entered correctly.

3. Enter the low address of the data into 00EA, 00EB, and the high address into 00EC, 00ED. The program will enter the cycle count into 00EE and use 00E8, 00E9 as the data-byte pointer. (00E7 is used as a false address during the program, so the contents will be lost.)

4. Turn on power to the programmer and examine the contents of peripheral port A

(1700). With a blank PROM in the programming socket the data byte should be FF. Go to 0000 and hit GO. The programming will take just under two minutes. When the programming finishes the display will be 0000-A0.

If there was an error detected during the verification routine, the display will light up with the address of the error. To verify

A kit for building Jim's EPROM Programmer is available from:  
O.C. Stafford Electronic Service & Development Co.  
427 South Benbow Road  
Greensboro NC 27401

	Drilled	Undrilled
PC Board (Part number KB/JHG 11478)	\$ 7.50	\$5.80
Parts kit (no board)	43.00	
Negative or positive	3.50	

Add \$1 for shipping.

#### Zero page registers:

00EE cycle count  
00EC, 00ED high data address: HDAL, HDAH  
00EA, 00EB low data address: LDAL, LDAH  
00E8, 00E9 data pointer: DPL, DPH  
00E7 Dummy counting address

#### Program:

```

0000 A0 00 LDY #00
0002 A9 64 LDA #64
0004 85 EE STA EE
0006 A9 FF LDA #FF
0008 8D 02 17 STA DRB
000B 8D 01 17 STA DDRA
000E A9 EF LDA #EF
0010 8D 03 17 STA DDRB
0013 A9 F5 LDA #F5
0015 8D 02 17 STA DRB
0018 20 6E 00 JSR MOV
001B B1 E8 LDA(Y) Data
001D 20 77 00 JSR PRGM
0020 20 90 00 JSR INCA
0023 90 F6 BCC A2
0025 F0 F4 BEQ A2

0027 A9 10 LDA #10
0029 2C 02 17 BIT DRA
002C F0 07 BEQ A4
002E C6 EE DEC EE
0030 DC E1 BNE A1
0032 4C 3D 00 JMP VRFY
0035 A9 FF LDA #FF
0037 20 77 00 JSR PRGM
003A 4C 27 00 JMP A3
003D A9 00 LDA #00
003F 8D 01 17 STA DDRA
0042 A9 FD LDA #FD
0044 8D 02 17 STA DRA
0047 20 6E 00 JSR MOV
004A AD 00 17 LDA DRA
004D D1 E8 CMP(Y) data

004F DC 12 BNE B2
0051 A9 FF LDA #FF
0053 8D 02 17 STA DRA
0056 CE 02 17 DEC DRA
005E F0 EA BEG B1
0060 4C 4F 1C JMP KIM
0063 A5 E8 LDA DPL
0065 85 FA STA KIM
0067 A5 E9 LDA DPH
0069 85 FB STA KIM
006B 4C 4F 1C JMP KIM

```

#### Subroutines:

```

006E A5 EA MOV LDA LDAL
0070 85 E8 STA DPL
0072 A5 EB LDA LDAH
0074 85 E9 STA DPH
0076 60 RTS

0077 8D 00 17 PRGM STA DRA
007A E6 E7 INC Dummy Add.
007C A9 03 LDA #03
007E 8D 02 17 STA DRB
0081 20 8A 00 JSR DELAY
0084 A9 06 LDA #06
0086 8D 02 17 STA DRB
0089 60 RTS
008A A2 F8 DELAY LDX F8
008D CA C1 DEX C1
008F 60 RTS

```

Clear Y  
Load cycle count  
and store 00EE.  
Set I/O Port B reg. to  
high state and I/O  
port A to output.  
Set I/O Port B to output  
except pin PB-4.  
Clear programming  
counters.  
Go Sub MOV.  
Load data using data pointer.  
Go Sub PRGM.  
Go Sub INCA.  
If less than or equal  
to high Data Pointer  
continue entering data.  
Bit test for end of  
cycle.  
if done go to A4.  
decrement cycle count  
and if not zero go to A1.  
Go to VRFY.  
Program FF into  
remainder of PROM.  
Go to end of cycle test.  
Set I/O Port A as  
input.  
Clear programming  
counters with CS low.  
Go Sub MOV.  
Load data word from PROM.  
compare to data word  
in RAM.  
On error go to B2.  
Toggle the  
programming  
counter.  
go to B1.  
Return to KIM program  
on error set  
KIM pointer to  
error address  
and return to  
KIM program

Move low data  
address into  
the data  
pointer and  
return.  
  
Output data to PROM.  
Delay for data setup.  
Raise PGM pin to  
26 volts.  
Go Sub DELAY.  
PGM pin returned to GND  
and counter incremented.  
Return.  
Delay for .99 msec.  
(992 clock cycles)  
and  
return

0090	E6	E8	INCA	INC	DPL		
0092	00	02		BNE	D1		Increment
0094	E6	E9		INC	DPH		data pointer
0096	A5	E9	D1	LDA	DPH		and
0098	C5	ED		CMP	HDAH		compare to
009A	90	04		BCC	D2		High Data
009C	A5	EB		LDA	DPL		address
009E	C5	EC		CMP	HDAI		and
00A0	60		02	RTS			return

PEEK routine:

00A1	A9	00	PEEK	LDA	#00			Set I/O Port A
00A3	80	01	17	STA	DDRA			as an input.
00A6	A9	FF		LDA	#FF			then toggle
00A8	80	02	17	STA	DRB			the programming
00AB	CE	02	17	DEC	DRB			counters.
00AE	A9	00		LDA	#00			Set KIM pointer
00B1	85	FA		STA	KIM	pointer low		to I/O Port A
00B2	A9	17		LDA	#17			and jump
00B4	85	FB		STA	KIM	pointer high		to KIM program
00B6	4C	4F	1C	JMP	KIM			to display PROM data.

the error load A1 into 17FA and 00 into 17FB. Then go to 1700.

The data should be the first byte in the PROM. To increment the PROM address, hit STOP. The data should now be the second byte in the PROM. Step the PROM to the location of the error.

If the error is a high bit in the PROM (e.g., a 1 in place of a 0), the programming can be attempted again. If it is a 0 in place of a 1, turn off the power and erase the PROM. Then verify that the erasure has returned the problem bit to a 1 and repeat the programming. Always be sure to turn off the power before inserting or removing the PROM. ■

*Program A. The programming program. The PEEK routine is used by entering A1 into 17FA and 00 into 17FB. Go to address 1703, hit the data key and enter C,F,F. This will clear the programming counters. Then go to address 1700. The data word displayed should be the first data byte in the PROM. By hitting the stop key, the PROM address can be incremented, and the data displayed will be the contents of the PROM.*