

# Build a \$20 EPROM Programmer

... for the 5204 4K chip

 


Fig. 1a. Programmer block diagram.

PBDD = \*\*\*11111, \* = don't care, PBDD = 1F  
PB0 = DCLK Clocks data on positive edge ↑ each transition increments the data.  
PB1 = DCLR Clears data to zero on low level. Normally high.  
PB2 = ACLK Clocks address on positive going edge ↑ each transition increments the address.  
PB3 = ACLR Clears address to zero on low level. Normally high.  
PB4 = PGM Provides program pulse to EPROM on low level. Normally high.

 



Fig. 1b. KIM-1 port assignments.

The availability of low-cost electrically programmable read only memory (EPROM) and the convenience of having a few favorite routines permanent as ROM in my KIM system provided the motivation to construct a 5204 EPROM programmer extension for KIM. The programmer design was to be as simple as possi-

ble, minimize I/O pin usage, and have its software completely relocatable to allow the routine to install itself in EPROM and be located in KIM unused memory areas without alteration. To reduce the programmer hardware requirement, the decision was made not to read the EPROM during programming as do most commercial programmers. The read EPROM modification to hardware and software could be added later should the need arise. Normally an EPROM will be programmed and then changed to a memory socket in KIM to be tested. Fig. 1a is a block diagram of the programmer and Fig. 1b details the KIM-1 port assignments for interfacing to the programmer.

## Why the 5204 EPROM?

The 5204 EPROM by

 

KIM-1 and programmer board - a neat combination.

National Semiconductor (MM5204) is a 4K electrically programmable (and erasable) read only memory. The device is a non-volatile memory organized 512 x 8 (½K bytes per chip). The 5204 requires +5 and -12 volt power supplies for ROM operation. Additional noteworthy features are its typical access time of 750 ns typical (1 µs maximum), power saver control for low power applications, and a three state data bus which permits easy memory expansion.

An alternative to the 5204 would be the readily available and inexpensive 1702A EPROM. The 1702A is organized 256 x 8 or ½K bytes. Its access time is 1 µs maximum, identical to the 5204. The cost of a 1702A is about \$7 as compared to \$8 for the 5204. An immediate observation is the smaller cost

per EPROM byte with the 5204. Naturally, if your requirements call for smaller memory blocks, such as a small system application, the 1702A may be a better choice. The 1702A is slightly more difficult to program due to the requirement to complement addressing during programming. This feature could be easily added to my basic programmer if you chose to modify it for the 1702A. The 1976 Intel Data Catalog is a good reference for the 1702A description and programming.

To access slow memory (access time less than 500 ns) with the 6502 a wait cycle is usually forced during memory read or write. The *MCS6500 Microcomputer Hardware Manual* by MOS Technology, Inc. describes a simple circuit to accomplish this wait cycle in section

2.3.4.1. By experimentation, however, I found that the combination of the 6502 having the address valid extended periods and the typical access time for the 5204 of 750 ns this delay circuit could be deleted. The 5204 EPROM has allowed me to expand KIM-1 with inexpensive ROM without affecting processor speed.

#### Programming the 5204 EPROM

Much of the literature I dug into discussed programming of the 1702A, 2708, and the 5204. The general consensus seems to be to not apply excessive voltages to prevent catastrophic failures, not to apply extremely fast waveforms to the address and data lines to prevent capacitive coupling internally from damaging the device, and not to apply excessively high duty cycle waveforms during programming to prevent high power dissipation in the device.

One good source of information is the *PROM User's Guide* published by Prolog

Corporation. Specific information on the 5204 EPROM may be obtained from National Semiconductor's MOS IC Data Book. Although some conflicting information is in these publications, the general guide lines were followed and in turn, good results obtained. For example, the first National MOS book I used indicated the program pulse width should be between 2.5 ms and 5 ms with a duty cycle of less than 25%. With this data in hand I selected a 3 ms program pulse, an off time of 10 ms, and a 23% duty cycle (see Fig. 2). In a later MOS memory publication National specifies the minimum pulse width as .5 ms. I saw no real reason to alter the timing, however, you may want to save time by adjusting the pulse timers in the routine. All you need do is scale down both times by an equal factor. A word of caution is in order though; be aware that the off period will be affected with less than 4.08 ms (1 MHz clock) off time although the programmer will still operate.

 


Fig. 2. Programmer timing diagram.

#### Sockets

- 1 24 pin dip
- 2 14 pin dip
- 3 16 pin dip

#### Miscellaneous

- 1 4½" square, .1 inch center, Vero or Vector board
- 1 44 pin edge connector (use with Vero board)
- 60 component mounting pins

#### Discretes

- 2 100 Ohm 1% ¼W
- 1 1k Ohm 10% ¼W
- 4 15k Ohm 10% ¼W
- 1 10k Ohm 10% ¼W
- 2 2.7k Ohm 10% ¼W
- 1 5.6k Ohm 10% ¼W
- 9 100k Ohm 5% ¼W
- 1 100 pF disk cap
- 2 1.0 uF 50 volt monolithic cap
- 1 10k Ohm trimpot
- 8 IN4002 rectifier
- 1 12 volt, 1 Watt Zener diode
- 1 2N2905A PNP transistor or eq.
- 1 2N5287 PNP transistor or eq. (with heat sink)
- 1 2N1893 NPN transistor or eq.
- 2 500 uF 35 volt electrolytic cap
- 1 100 uF 75 volt electrolytic cap
- 1 7812 +12 volt regulator
- 1 7912 -12 volt regulator
- 1 uA723 precision regulator
- 2 4040 CMOS counter
- 1 LM3900 Op amp
- 1 4050 CMOS buffer
- 2 25.2 VCT transformer (Stancor P8180)

Table 1. Parts list.

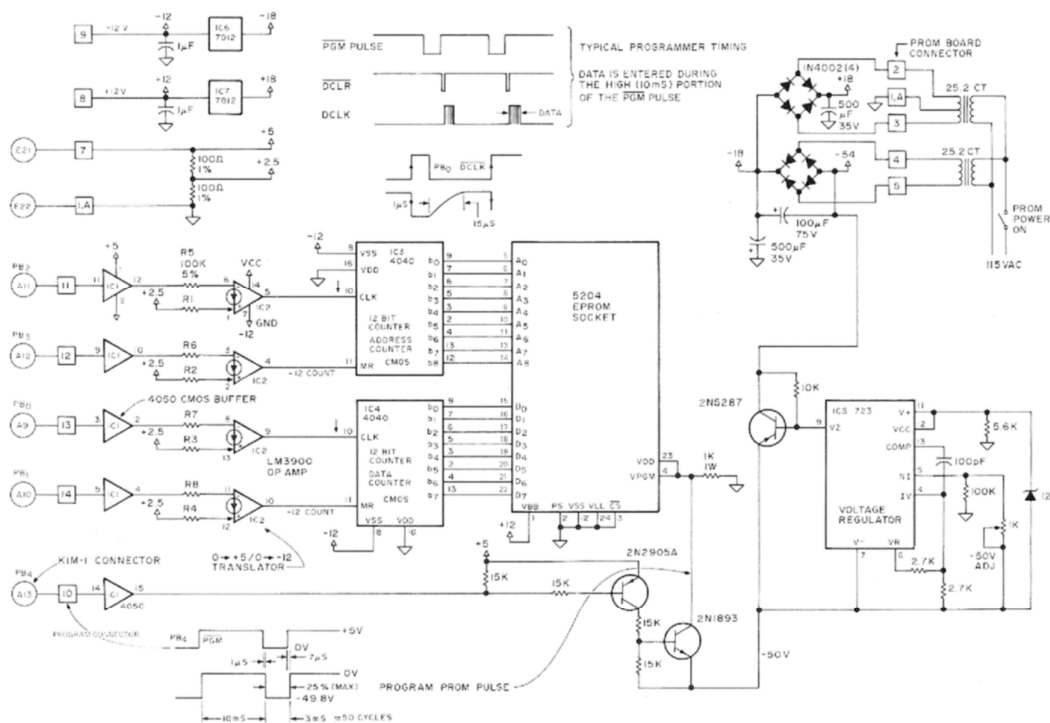


Fig. 3. Schematic diagram of 5204 EPROM Programmer.

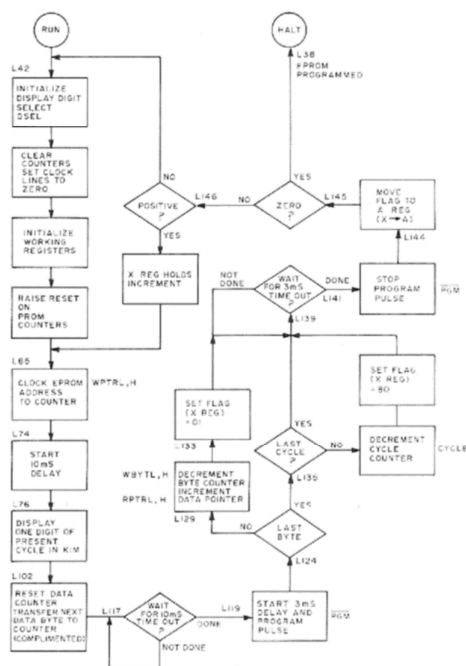


Fig. 4. EPROM Programmer flow diagram.

National suggests the 5204 be overprogrammed sequentially. Overprogramming consists of programming the EPROM in excess of the number of program cycles actually required to establish the correct data pattern. National states that each address location must be programmed for a minimum of 32 cycles with a pulse width of 5 ms or 64 cycles as the pulse width reaches 2.5 ms. I selected 50 cycles for a pulse width of 3 ms. For shorter program pulse widths National notes the EPROM should be programmed until the correct pattern is read back and then overprogrammed five times. This is symbolized by the notation  $x + 5x$  in the National literature. Since my programmer does not read this EPROM during programming the number of cycles are fixed by the routine or the operator at initialization.

The results of the tech-

nique used here have been satisfying and successful. To date I have 100% programmed a dozen EPROMS without a problem, except for one defective EPROM, which was replaced by the supplier at no charge.

## The Programmer Circuit

The circuit shown in Fig. 3 contains three regulator circuits with rectifiers for providing +12, -12, and -50 volts for the programmer. The 4040 CMOS counters provide the EPROM data and address registers. The LM3900 quad op amp translates the KIM 5 volt logic to -12 volt logic to control the counters. Two transistors level shift the program pulse to -50 volts. The third transistor is a series element in the uA723 -50 volt negative voltage regulator circuit. The 4050 CMOS buffer was used to convert the KIM TTL outputs to CMOS to gain the additional voltage swing pro-

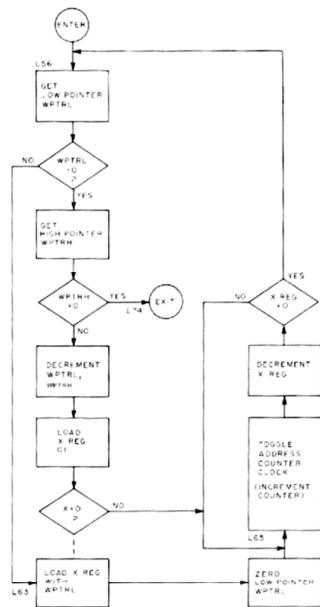


Fig. 5. Increment EPROM address routine flowchart.

vided with CMOS for increased reliability in the voltage translation process.

The address and data counters are operated identically. The counter is reset and then clocked until it contains the proper bit pattern for programming. The address is initialized and incremented to the cycle end. The data counter has the proper data pattern toggled in after being complemented by the programmer routine. The 5204 requires complemented data during programming.

## Construction

My board is constructed on a 4½" x 4½" Vero board which was cut down from a standard 4½" x 6" 44 pin Vero proto board (#10290/FG W44/74). The sockets and components used were non-critical; however, the EPROM socket should be a type that allows the EPROM easy entry and removal. Most economical sockets will fill the requirement. A zero force type socket that is used on commercial programmers would be ideal and expensive.

A standard Augat wire-wrap socket (Augat #324-AG2F) works fine. It all depends if you're going to program thousands of EPROMs. If you are, you should probably purchase one of the zero

force type sockets.

The circuit board power supply rectifiers and regulators are shown in the photos. The transformers, which came from my scrap pile, are mounted adjacent to the card support. The discrete components are all parts which were readily available and are non-critical in nature. The only requirements on the transistors are that they have a breakdown voltage in excess of 50 volts and be capable of dissipating a couple of Watts. The .50 volt regulator series pass transistor should have a small heatsink. If one is not available, fabricate one out of a thin sheet of copper or aluminum.

The complete parts complement should cost about \$20 excluding EPROMS.


## About the Program

The first usage of the program was to program an EPROM with itself to allow the EPROM routine to reside in KIM memory as ROM. I also felt that the program would serve more systems if it is independent of where it resides. You may, for instance want to relocate it

from a cassette into different portions of RAM so as not to disturb the program you want to enter into EPROM.

The programmer routine runs in two sections (see Fig. 4 and 5 and Program A). The first section, beginning with EPROM start, does a little housekeeping and then halts allowing the insertion of the EPROM in the programmer socket. The routine tests the number of bytes to be programmed; if the count is correct, it enters the number of bytes to be programmed into a counter. If the count is incorrect (i.e., if the number of bytes to be programmed is less than zero or greater than  $\frac{1}{2}K$ ), the routine exits to display FFFF in the KIM monitor. Then the break vector is established, the number of cycles is set to 50, and the I/O port to the programmer is initialized. After this the programmer routine halts in the KIM monitor at the first instruction in the next section (run, L42) of the routine.

 The halt allows power down of the programmer to permit the EPROM to be installed in the socket. Power



5204 EPROM Programmer board.

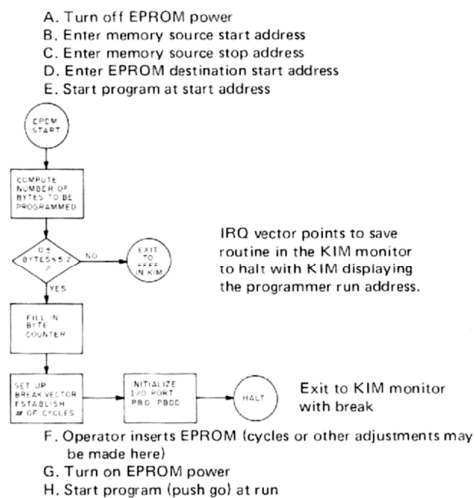


Fig. 6. Running the programmer.

is then restored and the EPROM may now be programmed. Running the routine, at the RUN location, programs the EPROM. While this program runs the present cycle is displayed in the KIM data digits, in hexadecimal, with the address digits dark. When finished the routine halts again at the RUN address. The programmer may now be powered down and the programmed EPROM removed.

The heart of the programmer routine, the RUN section, initializes the counters on the programmer for

address and data entry. The address is entered to the programmer followed by the start of the off period of the programmer 10 ms pulse. During this delay one of the digits of the cycle is displayed and the data is transferred from the RAM byte specified to the EPROM data counter. The routine then waits for the end of the 10 ms period.

At the end of the 10 ms period, the programmer program pulse is started along with the on period time of 3 ms. During this period the routine establishes the next operation by setting pointers

to the next byte of data or cycle through the setting of a flag in the x register. With the termination of the 3 ms period the programmer pulse is turned off, the flag is tested, and the next operation is performed. The operation consists of getting the next byte of data, starting a new cycle, and performing a halt when the EPROM is programmed.

An interesting note is the time consuming loop that clocks the data to the EPROM programmer data counter. Because this loop is completed during the off period of the programmer pulse the time period to program an EPROM is independent of this loop. This technique is an excellent example of how to use the KIM timer and the advantage of such a timer in a microcomputer system. The computer may do other tasks during waiting periods as long as you're back within the time period. With KIM the timer can easily be programmed to interrupt should uncertainties develop in the time required to complete the assigned tasks. Also, since the cycle digit is displayed during this 10 ms period, the digit stays on until the next 10 ms period is entered or the routine halts.

#### Operation

Operator loads via KIM

keyboard the start read, end read, and start write address in page zero. The power to the programmer circuit should be turned off, EPROM removed. (Refer to Fig. 6.)

Operator starts the program at the start (first instruction). At this time the program computes the number of bytes to be programmed, sets up the  $\overline{IRQ}$  vector for a program stop on break to KIM, establishes the number of programmer cycles, (which may be changed when the program halts) establishes the I/O configuration for the programmer, and then halts with the run address displayed by the KIM monitor.

The program will exit to FFFF in KIM if more than 512 bytes are selected to be written or if less than zero bytes were selected.

When the program halts, the number of cycles may be altered if desired.

The next step is to plug a 5204 EPROM into the programmer socket, turn on the programmer power, and then start the program (push go at the displayed address; run).

The cycles are counted down and displayed in the KIM display (in hexadecimal). The program halts back at the run address. Turn off the programmer, remove the programmed EPROM. ■

#### Program A. 5204 EPROM Programmer software routine (continued on page 76).

Page Zero Registers		
Cycle and Display Counters		
00DF	DSEL	DISPLAY DIGIT SELECT CODE
00E0	CYCLE	NUMBER OF PROGRAM CYCLES
Instruction Data		
00E1	ERAL	END READ ADDRESS LOW
00E2	ERAH	END READ ADDRESS HIGH
00E3	SRAL	START READ ADDRESS LOW
00E4	SRAH	START READ ADDRESS HIGH
00E5	SWAL	START WRITE ADDRESS LOW
00E6	SWAH	START WRITE ADDRESS HIGH
Working Registers		
00E7	BYTL	NUMBER OF PROGRAM LOW BYTES
00E8	BYTH	NUMBER OF PROGRAM HIGH BYTES
00E9	RPTRL	NEXT BYTE POINTERS
00EA	RPTRH	FOR DATA SOURCE
00EB	WPTRL	WRITE POINTERS FOR EPROM
00EC	WPTRH	ADDRESS START
00ED	WBYTL	BYTE COUNT WORKING REGISTERS
00EE	WBYTH	
Initialize routine: Establish data pointers, check for number of bytes 0 ≤ bytes ≤ 512 establish cycles, stop at program EPROM start address		
0200	D8	CLD
0201	38	SEC
0202	A5	LDA
0204	E5	SBC
0206	85	STA
	E1	ERAL
	E3	SRAL
	E7	BYTL
		BE
		START PROGRAM
		DETERMINE NUMBER
		OF BYTES
		TO
		BE

0208	A5	E2			LDA	ERAH	PROGRAMMED
020A	E5	E4			SBC	SRAH	
020C	10	03			BPL	L26	TEST IF NEGATIVE
020E	4C	29	19	L25	JMP	FFFF	SOMETHINGS WRONG, EXIT
0211	C9	02		L26	CMP	02	TEST IF $\geq$ 512
0213	10	F9			BPL	L25	EXIT IF POSITIVE (02 OR MORE)
0215	85	E8			STA	BYTH	ELSE, STORE
0217	18				CLC		
0218	A9	00			LDA	00	SET UP
021A	8D	FE	17		STA	17FE	BREAK
021D	A9	1C			LDA	1C	VECTOR
021F	8D	FF	17		STA	17FF	TO POINT AT STOP ROUTINE
0222	A9	31			LDA	31	INITIALIZE NUMBER
0224	85	E0			STA	CYCLE	OF CYCLES TO 50
0226	A9	1F			LDA	1F	ESTABLISH OUTPUT
0228	8D	03	17		STA	PBDD	PORT AND
0223	A9	10		STOP	LDA	10	SET OUTPUT
022D	8D	02	17		STA	PBD	STATUS
0230	00				BRK		BREAK WITH (RUN)
0231	00						NEXT ADDRESS IN KIM
<i>Program EPROM routine, initialize routine stops at run for EPROM setup in programmer circuit</i>							
0232	A9	00			RUN	LDA	00
0234	85	DF			STA	DSEL	INITIALIZE
0236	A9	F0			LDA	F0	DIGIT SELECT
0238	2D	02	17		AND	PBD	CLEAR COUNTERS
023B	8D	02	17		STA	PBD	READY CLOCKS
023E	A2	06			LDX	06	
0240	B5	E2		L48	LDA	L4,X	RESTORE
0242	95	E8			STA	L10,X	WORKING
0244	CA				DEX		REGISTERS
0245	D0	F9			BNE	L48	
0247	A9	0A			LDA	0A	RAISE RESETS
0249	0D	02	17		ORA	PBD	ON
024C	8D	02	17		STA	PBD	COUNTERS
024F	A0	00			LDY	00	ZERO Y (X = 0)
0251	A5	EB		L56	LDA	WPTRL	GET LOW POINTER FOR INCREMENT
0253	D0	0C			BNE	L63	IF NOT ZERO INCREMENT COUNTER
0255	A5	EC			LDA	WPTRH	
0257	F0	21			BEQ	L74	EXIT IF ZERO
0259	C6	EB		L60	DEC	WPTRL	ELSE, INCREMENT
025B	C6	EC		L60A	DEC	WPTRH	TO NEXT
025D	A2	01		L61	LDX	01	PAGE
025F	D0	04			BNE	L65	
0261	A6	EB		L63	LDX	WPTRL	
0263	84	EB			STY	WPTRL	ZERO WPTRL
0265	A9	FB		L65	LDA	FB	ENTER HERE FOR 1 STEP
0267	2D	02	17		AND	PBD	WITH X = 01
026A	8D	02	17		STA	PBD	
026D	A9	04			LDA	04	
026F	0D	02	17		ORA	PBD	
0272	8D	02	17		STA	PBD	
0275	CA				DEX		
0276	D0	ED			BNE	L65	
0278	F0	D7			BEQ	L56	
<i>Start 10 ms delay, display cycle digit</i>							
027A	A9	9C		L74	LDA	9C	START 10ms DELAY
027C	8D	06	17		STA	64	(1706)
027F	A9	7F			LDA	7F	SET UP SEGMENT PORT
0281	8D	41	17		STA	PADD1	FOR OUTPUT
0284	8E	40	17		STX	PAD1	X = 0 FROM ABOVE, SEGMENTS OUT
0287	8E	42	17		STX	PBD1	TURN OFF DIGIT
028A	A5	DF			LDA	DSEL	SELECT DIGIT TO BE DISPLAYED
028C	D0	13			BNE	L91	BRANCH TO DISPLAY HIGH DIGIT
028E	A9	12			LDA	DIG 1	LOAD 12 FOR LOW DIGIT
0290	8D	42	17		STA	PBD1	SELECT DIGIT
0293	A9	0F			LDA	0F	
0295	25	E0			AND	CYCLE	GET LOW DATA
0297	E6	DF			INC	DSEL	SELECT NEXT DIGIT
0299	D0	13			BNE	L99	ALWAYS NOT EQUAL TO ZERO
029B	F0	8E		STOP 1	BEQ	STOP	INTERMEDIATE STOP BRANCH
029D	10	C6		L89	BPL	L65	INTERMEDIATE BRANCH
029F	30	91		RUN 1	BMI	RUN	INTERMEDIATE RUN BRANCH
02A1	A9	10		L91	LDA	DIG2	LOAD 10 FOR HIGH DIGIT
02A3	8D	42	17		STA	PBD1	SELECT DIGIT
02A6	A5	E0			LDA	CYCLE	GET HIGH
02A8	4A				LSR		DIGIT
02A9	4A				LSR		OF CYCLE DATA
02AA	4A				LSR		
02AB	4A				LSR		
02AC	C6	DF			DEC	DSEL	
02AE	A8			L99	TAY		
02AF	B9	E7	1F		LDA	ABS, Y	GET CONVERSION DATA
02B2	8D	40	17		STA	PADD	TURN ON SEGMENTS
<i>Get data byte to EPROM data counter, wait for end of 10 ms pulse, start 3 ms EPROM program pulse</i>							
02B5	A9	FD			LDA	FD	RESET DATA COUNTER
02B7	2D	02	17		AND	PBD	
02BA	8D	02	17		STA	PBD	

02BD	A9	02		LDA	02	
02BF	0D	02	17	ORA	PBD	
02C2	8D	02	17	STA	PBD	
02C5	A9	FF		LDA	FF	GET COMPLEMENTED
02C7	A0	00		LDY	00	DATA
02C9	51	E9		EOR	(IND),Y	FOR COUNTER RPTRL
02CB	F0	0A		BEQ	L117	EXIT IF DATA IS ZERO
02CD	AA			TAX		ELSE INCREMENT COUNT
02CE	EE	02	17	INC	PBD	
02D1	CE	02	17	DEC	PBD	(4.08ms LOOP MAX WITH 1 MHz CLOCK)
02D4	CA			DEX		
02D5	D0	F7		BNE	L113	
02D7	AD	07	17	LDA	1707	GET TIMER STATUS
02DA	F0	FB		BEQ	L117	IF NOT DONE, CHECK
02DC	A9	30		LDA	30	START 3ms TIME
02DE	8D	06	17	STA	-64	FOR PROGRAM PULSE
02E1	A9	EF		LDA	EF	
02E3	2D	02	17	AND	PBD	
02E6	8D	02	17	STA	PBD	START PULSE
<i>Test for last byte, last cycle, wait for 3 ms time-out. Stop program pulse</i>						
02E9	E4	ED		CPX	WBYTL	
02EB	D0	06		BNE	L129	
02ED	E4	EE		CPX	WBYTH	
02EF	F0	0E		BEQ	L135	BOTH ZERO BRANCH TO TEST CYCLE
02F1	C6	EE		DEC	WBYTH	
02F3	C6	ED	L129	DEC	WBYTL	
02F5	E6	E9		INC	RPTRL	
02F7	D0	02		BNE	L133	
02F9	E6	EA		INC	RPTRH	
02FB	A2	01	L133	LDX	01	SET FLAG AND WAIT
02FD	D0	08		BNE	L139	FOR TIME OUT, FLAG = 01, POS
02FF	E4	E0	L135	CPX	CYCLE	
0301	F0	04		BEQ	L139	WAIT FOR TIME OUT FLAG = 00
0303	C6	E0		DEC	CYCLE	
0305	A2	80		LDX	80	
0307	AD	07	17	LDA	1707	TEST FOR TIME OUT
030A	F0	FB		BEQ	L139	
030C	A9	10		LDA	10	STOP PROGRAM
030E	0D	02	17	ORA	PBD	PULSE
0311	8D	02	17	STA	PBD	
0314	8A			TXA		GET FLAG FOR TEST
0315	F0	84		BEQ	STOP1	IF ZERO, ALL DONE, EXIT AT START
0317	10	84		BPL	L89	BRANCH IF POSITIVE TO INC. ADDRESS
0319	30	84		BMI	RUN1	RUN NEXT CYCLE