



# Build the TVT-6: A Low-Cost DIRECT VIDEO DISPLAY

PART I



\$35 microcomputer "add-on" provides:

- User-selectable line lengths
- Scrolling
- Up to 4k on-screen characters with only 3-MHz bandwidth

BY DON LANCASTER

The TVT-6  
connected  
to a KIM-1.

Thanks to some software tricks, a simple and low-cost add-on circuit, and a new way to speed up a microprocessor, you can now build a video interface for your microcomputer for an investment of only \$20 to \$35. The TVT-6 video system described here permits the choice of virtually any format including 16/32 (16 lines of 32 characters), 16/64, or 32/64. It also features full editing capability and full-performance cursor.

In spite of its simplicity (10 low-cost IC's), the circuit employs a new approach to video processing that permits up to 4000 characters to be displayed on-screen within a 3-MHz bandwidth. Although the TVT-6 was designed for the 6502 microprocessor based KIM-1, software can be used to easily map into the JOLT, EBKA, or Ohio Scientific microcomputers. In addition, the TVT-6 can be adapted to other microprocessors, including the popular 6800, 8080, and Z80. It is easiest to use with 16-address-line systems that operate on a single 5-volt supply and 1- $\mu$ s cycle time.

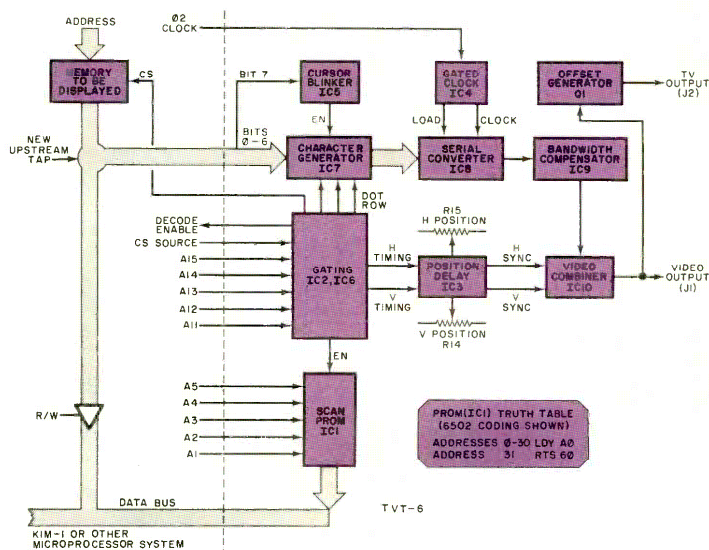


Fig. 1. TVT-6 block diagram and truth table for the PROM.

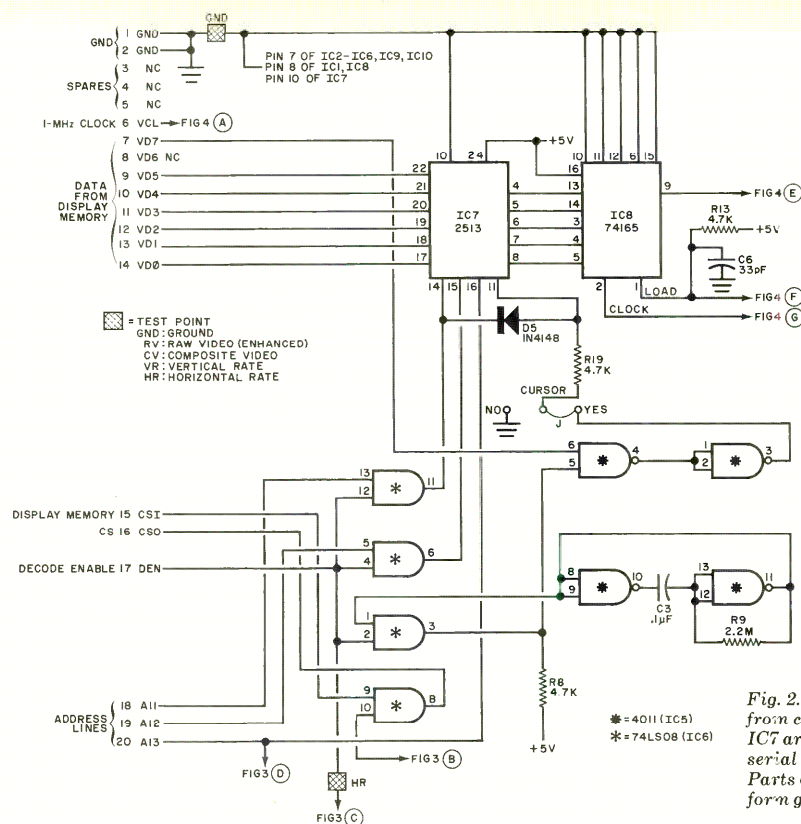


Fig. 2. Parallel outputs from character generator IC7 are converted into serial data in IC8. Parts of IC5 and IC6 form gating circuits.


Other systems will require software and microprogramming translation for their particular machine languages.

In this first of a two-part article, we will cover the hardware and construction details for the TVT-6. Next month, we will cover debugging, some useful software for the system, and provide instructions on how to couple the TVT-6 to other microprocessors.


**Circuit Operation.** A block diagram of the TVT-6, as used with the KIM-1 system, is shown in Fig. 1. The complete schematic diagram of the video system is shown in Figs. 2 through 4.

As shown in Fig. 1, bits 0 through 6 from the "upstream tap" on the KIM display memory drive character generator IC7 whose blanking and formatting are helped along by the AND gates in IC6. The cursor bit (bit 7) is stripped off the upstream tap and routed to cursor blinker IC5, which introduces a blinking cursor into the character generator's enable input.

The parallel outputs from IC7 go to

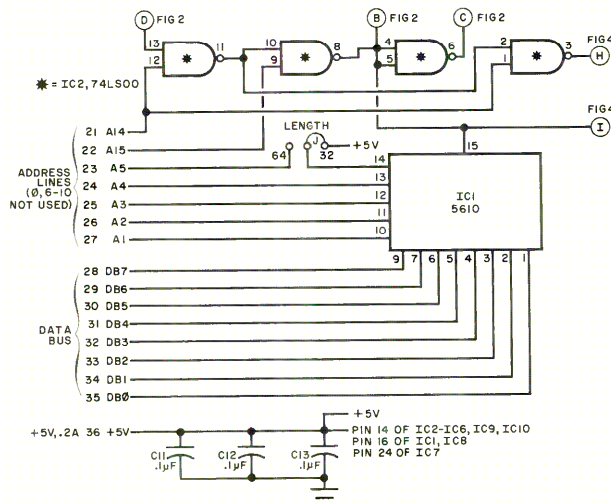



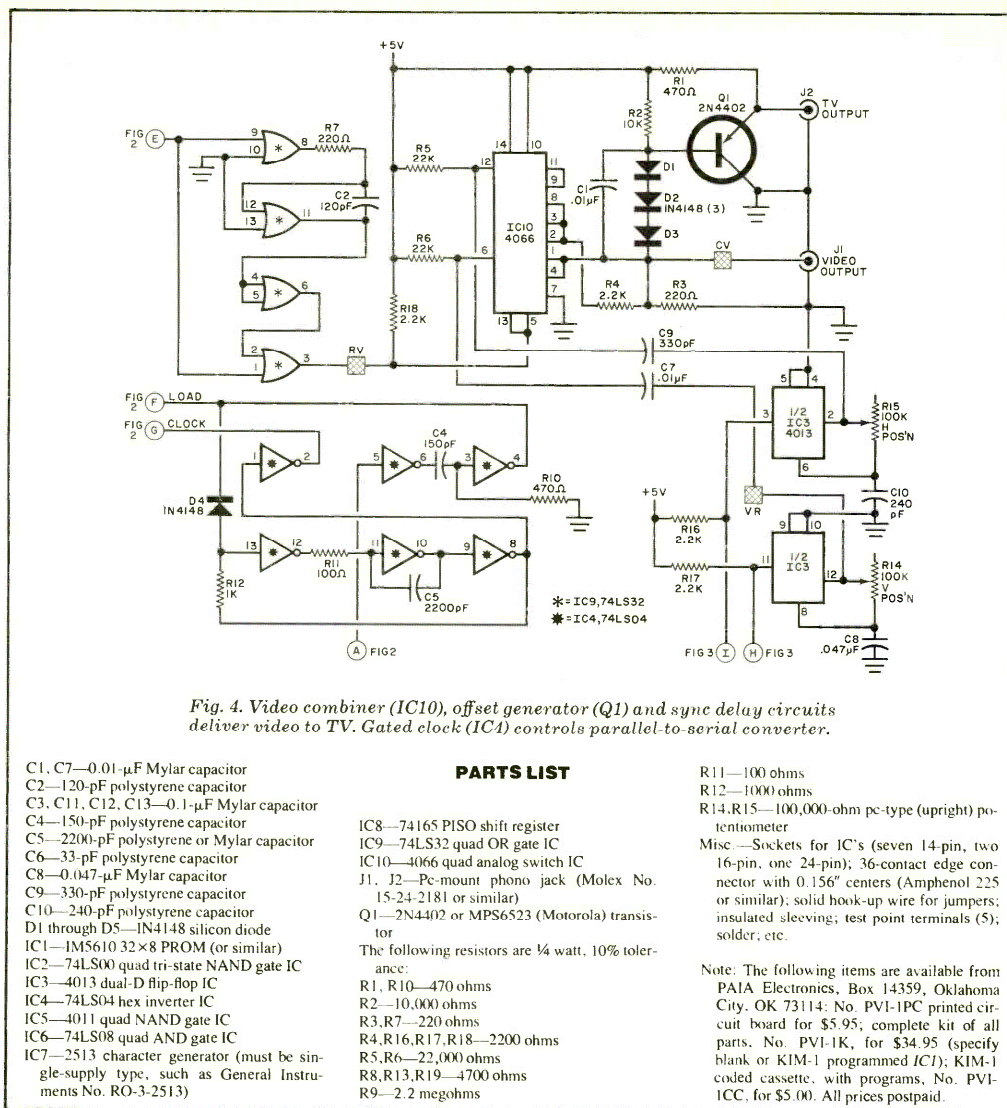

shift register IC8, where they are converted into a serial video signal. The clock and load commands for IC8 come from gated oscillator IC4, which derives its signals from the microcomputer's clock. It is important that the correct clock phase be selected to permit the loading of IC8 to occur when the output of the character generator is valid and settled. This is phase 2 in the KIM-1. (If you are using a different  $\mu$ P based computer, check this detail.)

The serial video from IC8 goes to the TV Bandwidth Compensator in IC9, which predistorts the video by delaying the video output and OR'ing it against itself. This widens the vertical portions of all characters to generate clean and crisp characters that require minimum bandwidth. The amount of widening is determined by C2 (Fig. 4). The optimum value of C2 is obtained when the generated M or W in the video display just barely closes.

The vertical and horizontal timing signals from IC2 in the gating circuit are delayed by IC3. The display positioning can be varied by potentiometers R14 and R15. The vertical and horizontal sync signals are combined with the enhanced video from IC9 into video combiner IC10. The output from IC10, available at J1, is composite video, with the sync tips at ground, black at 0.4 volt, and white at 1.6 volts. This output can be used to drive conventional video moni-



tors and converted TV receivers. The video output from IC10 is also fed to Q1, which is offset to deliver a +4-volt output for the white level. This output, available at J2, can be connected directly to the first video amplifier of most transformer-powered solid-state TV receivers (see box for details) without requiring biasing, coupling, or translation circuits.

Two options are provided with the TVT-6, both of which are jumper selected. The LENGTH option allows a choice of either 32 or 64 characters/line. The CURSOR option gives the choice of either no cursor or allows the cursor to be displayed under software control.

**Construction.** The actual-size etching and drilling guide for the printed circuit board used in the TVT-6 is shown in Fig. 5, along with the component-installation diagram. Start assembly by installing and soldering into place the 21 jumpers and test points. (Note that insulated sleeving must be used on two of the long jumpers.) Install the IC sockets, resistors, capacitors, diodes, jacks, and position controls R14 and R15. Do not install the IC's at this time. The correct IC installation sequence and the waveforms to be observed will be discussed in Part 2 next month.

**Computer Interface.** Detailed in Table I are the requirements of each of the edge connector contacts on the TVT-6 and how to use each contact. Table I also contains the KIM-1 interface connection instructions. The interface consists of adding a new connector and making some add-on connections. One circuit board trace is cut on the KIM-1's pc board to permit an optional change-over switch (or jumper) to be added to the microcomputers. This permits KIM-1 to be used with or without the TVT-6.

**General Operation.** Since most of today's TVT circuits are used with a microprocessor or microcomputer, it is best to do as much of the display control as possible with the microprocessor and some software. What may not be obvious is that almost all of the timing in the system can also be done using the microprocessor. All this takes is a few dozen words of code.

The four key secrets of operation for the TVT-6 are:

1. Carefully choose how the address lines are defined for TVT operation.
2. Add a new instruction, which we call SCAN, to rapidly address 32 or 64 sequential memory locations.
3. Permanently connect an upstream

50


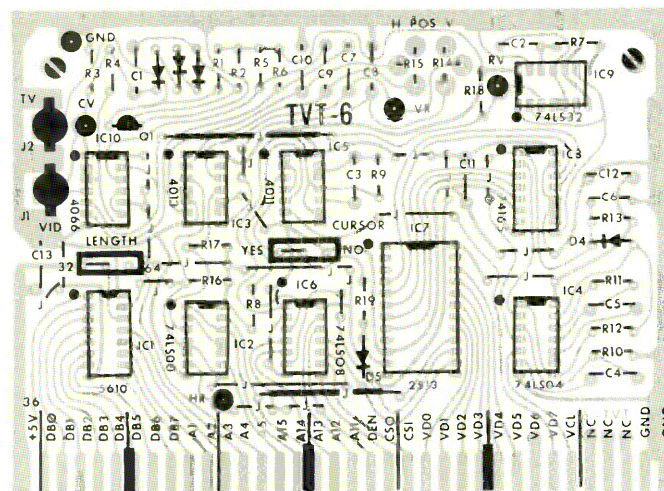


Fig. 5. Actual-size foil pattern (top) and component installation (below). Use sockets for all IC's. Edge connectors go to KIM-1.

POPULAR ELECTRONICS

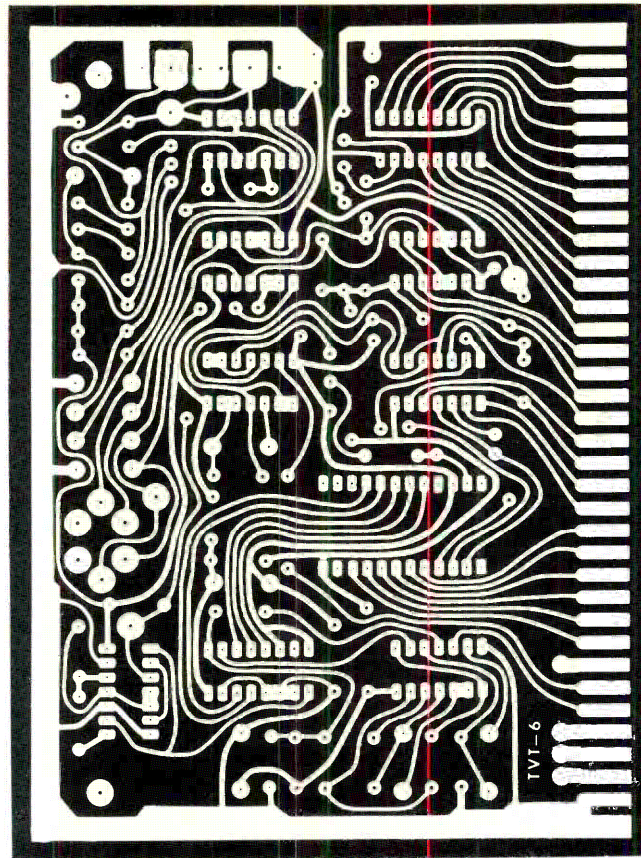

**TABLE I**  
**TVT-6 PINOUT AND KIM-1 INTERFACE**

TVT-6 CONTACT	NAME	REMARKS	A4,	R (A13)	20
1,2	GND	Heavy wire to expansion contact 22 or similar point in KIM-1	A3,	S (A14)	21
3, 4, 5	NC	Spares	A2,	T (A15)	22
6	VCL	1-MHz clock from expansion contact U ( $\phi$ 2). (In other systems clock phase must be selected so that load pulse arrives when CG is valid.)	A1	F (A5)	23
				E (A4)	24
				D (A3)	25
				C (A2)	26
				B (A1)	27
7,8,9,10,11,12,13,14	VD7, VD6, VD5, VD4, VD3, VD2, VD1, VD $\phi$	Data output from memory display; drives character generator. For KIM-1 to display any part of pages 00 through 03, connections must be made as follows: TVT-6 contact: to pin 12 of KIM-1 IC: 7 U5 8 U6 9 U7 10 U8 11 U9 12 U10 13 U11 14 U12	28, 29, 30, 31, 32, 33, 34, 35	DB7, DB6, DB5, DB4, DB3, DB2, DB1, DB $\phi$	$\mu$ P data bus; tri-state active high from IC1 during active scan, not used at other times. Connections to KIM-1 expansion: KIM-1 contact: to TVT-6 contact: 8 (BD7) 28 9 (DB6) 29 10 (DB5) 30 11 (BD4) 31 12 (DB3) 32 13 (DB2) 33 14 (DB1) 34 15 (DB $\phi$ ) 35
15	CSI	Display memory chip select from $\mu$ P; negative logic OR combined with TVT-6 chip select. From pin 1 of U4 on KIM-1.	36	+5V	Regulated +5-volt (200-mA) power bus; should be heavy wire. From KIM-1 expansion contact 21 or similar point to contact 36 in TVT-6.
16	CSO	Display memory chip select source; enables display memory when either TVT-6 is active or contact 15 is low. Goes to pin 13 of U5 through U12 in KIM-1 when displaying any part of pages 00 through 03. Existing K $\phi$ connection in KIM-1 must be broken.			
17	DEN	Decode enable; goes low when $\mu$ P is operated in normal mode, high when TVT-6 is doing an active scan. Goes to KIM-1 Applications contact K. Any external ground on applications contact K should be removed.			
18,19,20,21,22,23,24, 25, 26, 27	A11, A12, A13, A14, A15, A5,	Address inputs from $\mu$ C, positive true. Addresses A $\phi$ A6 through A10 not sent to TVT-6. Connections to KIM-1 expansion: KIM-1 contact: to TVT-6 contact: N (A11) 18 P (A12) 19			


Note: KIM-1 conversion consists of breaking one foil trace and adding a new 36-pin socket (Amphenol 127 or similar). Connection to be broken originates as K $\phi$  (pin 1 of U4). Routing of K $\phi$  that goes to memory chip select pin 13 of U5 through U12 should be broken. Other K $\phi$  connections, such as that to pin 1 of U16 should remain intact. Any external ground connections to Application connector contact K (decode-enable) must be removed. All wiring should be made with a wiring pencil.

When KIM-1 is used *without* displaying video, it will behave normally and transparently as long as TVT-6 is plugged in and addresses 8000 through DFFF are not used. To restore KIM-1 operation with TVT-6 out of socket, or to use available addresses for other programs, jumper pin 15 to pin 16 and separately jumper pin 1 to pin 17 in the KIM-1. Note that this jumpering is to be done only when TVT-6 is out of its connector. If you wish, a dpdt changeover switch can be added to perform the jumpering. Switch positions should be changed only when power is off.

memory tap to the character generator and display circuit.


4. Create special software that will allow TVT-6 scanning.

All 16 address lines are used, assigned as shown in Fig. 6A for a 32-character/line system or as shown in Fig. 6B for a 64-character/line system. Address A15 is the horizontal sync pulse and the key to jumping to the new scan instruction. This pulse is followed in descending address order by the vertical sync (A14) and three lines (L4, L2, L1) that produce the "what row of dots do we want?" information for the character generator. The lower address lines are used to select a page of display memory and to select the character that goes into any particular horizontal and vertical location on the display.

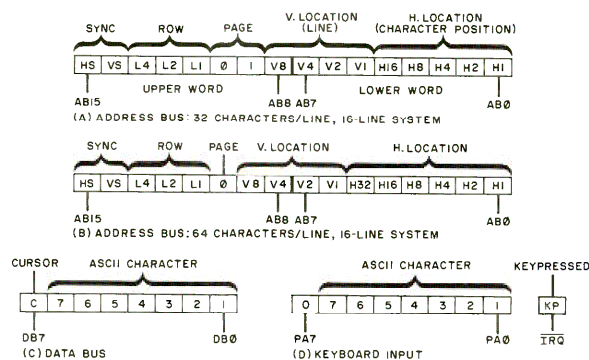

*Fig. 6. Bus definitions as used with the TVT-6.  
All 16 address lines are used as described in text.*

## DIRECT-VIDEO INPUT CONVERSION

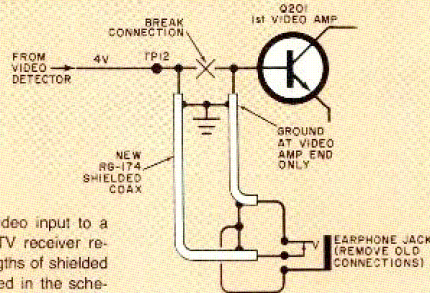

Adding a TVT-6 direct-video input to a small-screen solid-state TV receiver requires only two short lengths of shielded coaxial cable, as illustrated in the schematic. (Important Note: Do not use a hot-chassis TV receiver! Make absolutely certain that the TV receiver you use is transformer powered from the ac line.) The conversion circuit shown here is for the Sears No. 562-50260500 (Sams Photoact No. 1565-1). Other TV receivers can be modified in a similar manner.

The earphone jack in the circuit provides automatic changeover from normal receiver performance to video access. Correct bias is provided by TV output of the TVT-6. As an option, you can defeat the sound trap in the Sears TV receiver by lifting one end of capacitor C201.

The data within the machine (see Fig. 6C) uses the lowest seven bits as ASCII character storage. This is arranged by putting the least-significant ASCII character bit in the least-significant data slot, and so on up through the more significant bits. The eighth data bit (DB7) is reserved for a cursor. If DB7 is a zero, a character is displayed, while if it is a one, a cursor box is optionally displayed.

The existing KIM-1 keypad can be used as an ASCII keyboard for many applications, particularly for setup and debugging. If you wish to add an external ASCII keyboard and encoder, connect it to the KIM-1's parallel interface A, following the assignments shown in Fig. 6D. The seven ASCII bits go to the seven low-order data lines, while PA7 is hard wired for a zero. The keypress, or strobe, signal from the keyboard must pull the IRQ (interrupt request line) to ground for 10  $\mu$ s to enter a character or machine command.

The truth table for PROM IC1 is shown in Fig. 1. This truth table stores the SCAN instruction, activated by addresses 8000 through DFFF. When IC1 is enabled, it causes the microprocessor's program counter to appear on the address lines for 32 or 64 consecutive scans that advance one count per microsecond. This automatically and sequentially addresses the display memory and produces exactly the data needed for a horizontal scan of TVT characters. The scan instruction runs at least twice as fast as the microprocessor normally moves, which is the key to TVT timing with a microprocessor.

To use the SCAN instruction, jump to a subroutine whose starting address is within the 8000 to DFFF range. For example, if you call JRS 8200, the SCAN instruction will deliver a horizontal sync pulse and initiate operation on the top row of characters, starting with the first character on page 2. After a selected 32

interrupt and reset vectors on the KIM-1 so that the operating system will work compatibly and properly with the new SCAN instruction.

There are many possible codings for the SCAN program with the limitation that the last address is a return-to-subroutine (RTS) instruction. The obvious choice of NOP or EA runs at only half speed and can't be used. Of the three dozen instructions that operate at full speed, the choice of LDY is the one that does not disturb the accumulator or its flags. This adds flexibility to other programs. The Y register can be viewed as a write-only memory in the SCAN software and we can think of the whole SCAN instruction as a group of double-speed fetch-but-don't-execute instructions. Theoretically, a 64-word PROM would be required for a 64-character line, but this can be overcome by ignoring address A0 and changing the PROM's address every second cycle of the machine.

**Upstream Tap.** The SCAN instruction will sequentially address 32 or 64 memory slots per horizontal scan line at a rate of one-per-clock cycle (1  $\mu$ s). These addresses are presented to the entire memory in the computer, including the memory to be displayed. However, during the display times, the SCAN instruc-

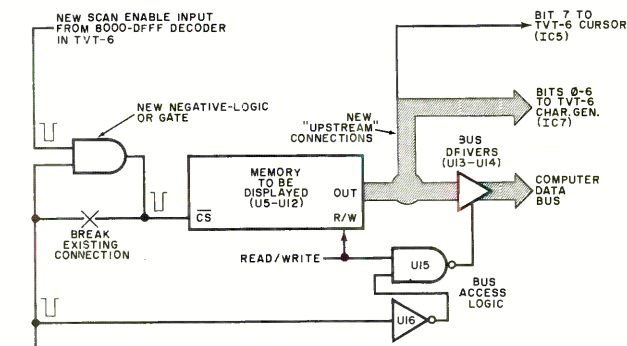


Fig. 7. Adding the upstream tap to the memory to be displayed.


or 64 characters, the SCAN instruction automatically jumps back to the main program.

The SCAN instruction can be viewed as a "portable subroutine" because it readily moves around to automatically output the correct page and character generator's row information, starting with an easily computed JSR address. Addresses above DFFF will not activate the SCAN instruction. This includes the

tion and its PROM have control of the data bus so that the display memory (or anything else) cannot output information to the data bus.

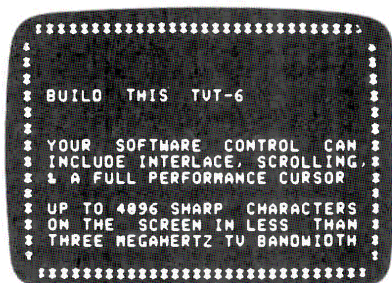The upstream tap is added as shown in Fig. 7. This tap is always outputting information to the character generator in the TVT-6. The output information is present even (and especially) when the display memory data bus drivers have been inactive. ◇





# BUILD THE TVT-6 Part II

*System debugging, software, and how to interface to other processors.*

BY DON LANCASTER

**L**AST MONTH, we discussed construction of the TVT-6 TV typewriter and explained how it works and how it is connected to a KIM-1 microcomputer. We also started a discussion of the operating secrets of the TVT-6. Here, we complete the "secrets" discussion and go on to system debugging, some useful programs, and tell you how to interface the TVT-6 with other microprocessors.

**Software.** Four examples of tested, annotated, and workable KIM-1 software are given in the tables in this article. Table II contains a 16 x 32 scan program with full interface. It automati-

cally generates almost all the timing required by the TVT-6 and its companion TV monitor for this display format. The program is run by jumping to memory location 17Ad. The display is stopped by interrupting with the operating system, the cursor, or other program.

Table III is an optional full-performance cursor for the 16 x 32 system and includes scrolling, full cursor motion, and erase-to-end-of-screen capabilities. It is run by allowing the key-press signal from the keyboard to interrupt the scan program (any of the three Tables) via the IRQ interrupt line. Note that the cursor program is totally inde-

pendent of the SCAN program. The only things the two programs share in common are the same pages of display memory. The screen-read-to-cassette can be performed using the existing KIM-1 operating system programs. You can also load from cassette to display, using the automatic search firmware.

Table IV is a 16-line/64-character scan program that requires only 64 words to be written into memory for the entire program. This program can be used to display the entire 1k of minimum KIM-1 memory for use as a super front-panel display if desired. For display-only applications, 1k of contiguous memory

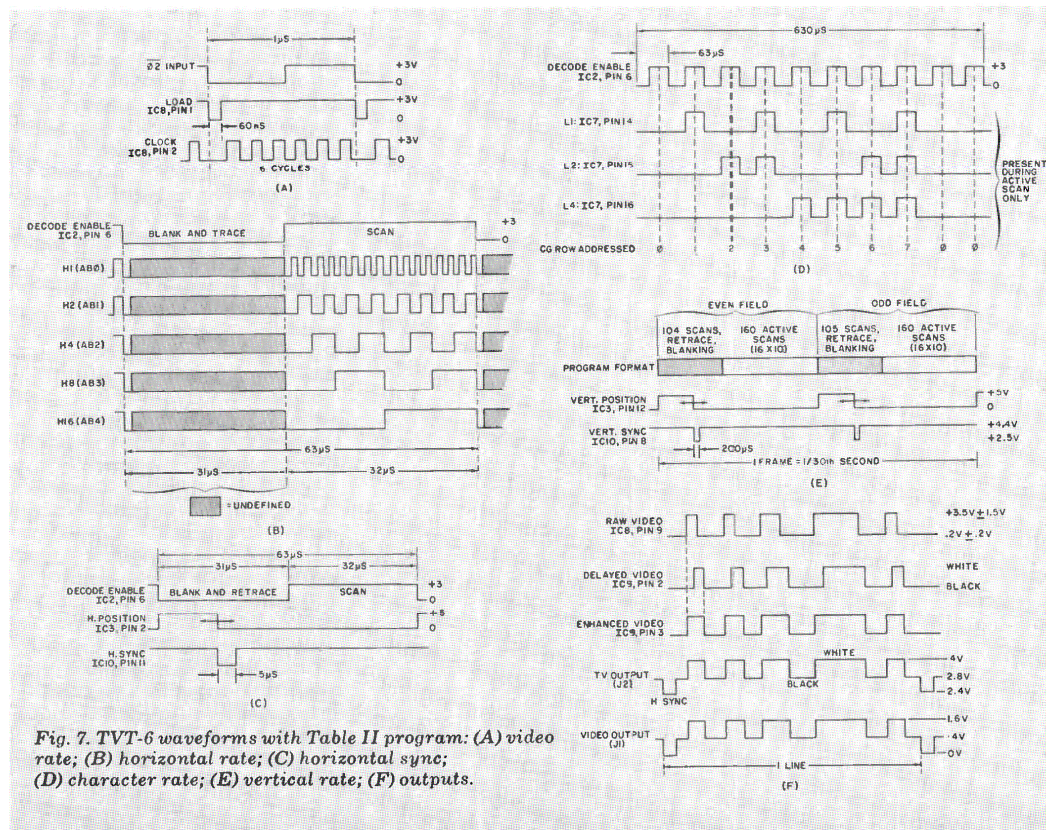


Fig. 7. TVT-6 waveforms with Table II program: (A) video rate; (B) horizontal rate; (C) horizontal sync; (D) character rate; (E) vertical rate; (F) outputs.



TABLE II


16 line X 32 character per line Interlaced  
TV76 Raster Scan:

μP - 6502      Start - JMP 17Ad      Displayed 0200-03FF  
System - KIM-1      End - Interrupt      Program Space 1780-17E2

HS	VS	L4	L2	L1	O	1	VS	V4	V2	V1	H16	H8	H4	H2	H1
----	----	----	----	----	---	---	----	----	----	----	-----	----	----	----	----

Upper Address

Lower Address

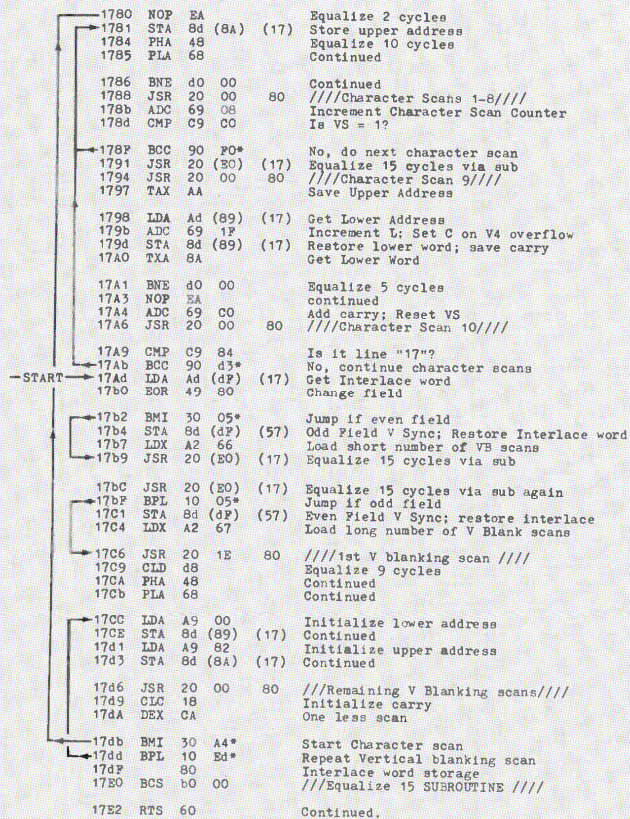

NOTES: TV76 must be connected and scan microprogram PROM (IC1) must be in circuit for program to run.

Both 17b4 and 17c1 require that page 17 be enabled when page 57 is addressed. This is done automatically with KIM-1 circuitry.

Step 1789 goes to where the upper address stored in 178A and the lower address stored in 1789 tells it to. Values in these slots continuously change throughout the program.


For a 525-line system, use 17b8 64 and 17c5 65 and a KIM-1 crystal of 992.250 kHz. This is only needed for video superposition and titling applications.

Normal program horizontal frequency 15,873.015 Hz;  
Vertical frequency 60.0114 Hz. 63 μs per line; 264.5 lines.

\* Denotes a relative branch that is program length sensitive.

( ) Denotes an absolute address that is program location sensitive.

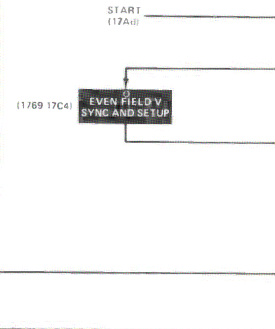TV76 length jumper must be in "32" position.




is required. Keep in mind that the KIM-1 has some operating system slots in the top of page zero and the stack at the top of page one. Unless you actually want to display the stack and operating system parameters, do not use these slots.

The 64-character line makes the TV receiver's horizontal frequency run considerably lower than normal. This will require a readjustment of the horizontal-hold control or some extra capacitance across the existing horizontal-hold capacitor. The width of the raster may also have to be reduced; this is most easily accomplished by adding a low-value inductor in series with the yoke. These changes are best made in a small-screen, transformer-powered monochrome TV receiver. The tradeoff of a lowered horizontal frequency produces a long character line but still allows 1 μs/character. This will not tax the bandwidth restrictions of TV receivers or r-f modulators. (Editor's Note: The small-screen Sears TV receiver we used required adjustment of horizontal size and linearity, a 0.033-μF Mylar capacitor in parallel with the 0.068-μF capacitor used for C408 in the receiver, and an inductor consisting of 60 turns of No. 24 enameled wire on a 1/2" Nylon form in series with the red yoke lead in the receiver. In addition, it was necessary to disconnect one side of C201 in the receiver

POPULAR ELECTRONICS



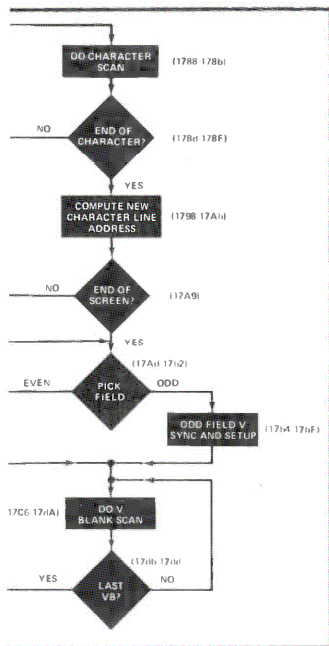

to defeat the sound trap. *Never attempt to modify a TV receiver that is powered directly from the ac line without an isolating transformer.*

Table V contains a program that we call "Cruncher the Bear." This program produces 64 fully interlaced characters in each of 32 rows, for a total of 2048 sharp ASCII characters on-screen at one time within the 3-MHz bandwidth. You can add a hex-to-ASCII converter that slowly sequences high- and low-order machine code characters in the same slot and end up with 4096 hex characters displayed in only 3 MHz of bandwidth.

Table V requires a contiguous 2k of memory with a common upstream tap and separate chip enables. However, it is easily incorporated if you really want or need to display as many characters as the program allows.

Other software is easily written and developed for the TVT-6. For example, you may wish to have a 32 x 44 or a 32 x 48 character display and still use normal, or nearly normal, horizontal scanning rates. This allows for video titling and superimposition, oversize characters, color graphics, lower-case characters, and game displays. There is no lower limit to the number of character rows or characters per line you can use. If you have limited memory available,

AUGUST 1977

Table III

16 X 32 Full-performance Cursor:

uP -- 6502 Start -- IRQ Displayed 0200-03FF  
System -- KIM-1 End -- RTI Program Space 0100-01dF

Input to Parallel Word A 

0	A7	A6	A5	A4	A3	A2	A1
---	----	----	----	----	----	----	----

 IRQ 10 µs

Clear - CAN (18) Cursor Home - SOH (0A)  
Carriage Return - CR (0d) Scroll Up - DC1 (11)  
Cursor Up - VT (0b) Erase to End - DC2 (12)  
Cursor Down - LF (0A) Spare Hook - DC3 (13)  
Cursor Left - BS (08) Enter -- All characters  
Cursor Right - HT (09) Ignore -- All other CTRL

Enter via IRQ	0100 PHA 48	Save A
	0101 LDY A0 00	Reset Y Index
	0103 LDA A5 (2E)	Get Cursor and test for range
	0105 CMP C9 05	Is cursor on page 3?
	0107 BEQ P0 04*	Yes, OK to continue
	0109 CMP C9 02	Is cursor on page 2?
	010b BNE d0 3A*	No, Home cursor
	010d LDA b1 (Ed)	Get old curored character
0147	010F AND 29 7F	Erase old cursor
	0111 STA 91 (Ed)	Replace character without cursor
	0113 LDA Ad 00	Get new character from A parallel Int.
	0116 CMP C9 20	Is it a character to be entered?
0142	0118 BCS b0 2B*	Yes, go and enter character
	011A CMP C9 18	Clear Screen?
015E	011C BEQ P0 40*	Yes, clear screen
	011E CMP C9 0d	Return Carriage?
0152	0120 BEQ P0 30*	Yes, Return carriage
	0122 CMP C9 0b	Cursor Up?
0194	0124 BEQ P0 62*	Yes, Up Cursor
	0126 CMP C9 0A	Cursor Down?
0166	0128 BEQ P0 3C*	Yes, Down Cursor
	012A CMP C9 09	Cursor Right?
0158	012C BEQ P0 2A*	Yes, Right Cursor
	012E CMP C9 08	Cursor Left?
01A7	0130 BEQ P0 75*	Yes, Left Cursor
	0132 CMP C9 01	Cursor Home?
0147	0134 BEQ P0 11*	Yes, Home Cursor
	0136 CMP C9 11	Scroll Up?
0175	0138 BEQ P0 3b*	Yes, Scroll Up
	013A CMP C9 12	Spare Hook?
014A	013C BEQ P0 0C*	Ignore--Restore Cursor
	013E CMP C9 13	Erase to EOS?
01b1	0140 BEQ P0 6F*	Yes, Erase to EOS
	0142 JSR 20 (D3) (01)	Enter Character/////
	0145 BNE d0 03*	End of Screen?
	0147 JSR 20 (C2) (01)	Yes, Home Cursor
	014A LDA b1 (Ed)	Restore Cursor/////
	014C ORA 09 80	Add cursor to curored character
	014E STA 91 (Ed)	Replace curored character
	0150 PLA 68	Get A
Out	0151 RTI 40	Return to Scan
	0152 LDA A5 (Ed)	Carriage Return/////
	0154 ORA 09 1F	Move Cursor to Right End
	0156 STA 85 (Ed)	Restore Cursor
	0158 JSR 20 (d5) (01)	Increment Cursor
	015b JMP 4C (45) (01)	Finish
	015E JSR 20 (C2) (01)	Clear//Home Cursor
	0161 JSR 20 (Cb) (01)	Clear Screen
0147	0164 BEQ P0 E1*	Finish
	0166 LDA A5 (Ed)	Cursor Down///// Get Cursor
	0168 CLC 18	Clear Carry
	0169 ADC 69 20	Move Cursor Down
	016b STA 85 (Ed)	Restore Cursor
	016d BCC 90 03*	Overflow of page?
	016F JSR 20 (49) (01)	Yes, Increment upper page
	0172 JMP 4C (45) (01)	Finish
	0175 JSR 20 (C2) (01)	Scroll Up///// Home Cursor
	0178 LDY A0 20	Add Offset to Index
	017A LDA b1 (Ed)	Get Offset Indexed Character
	017C LDY A0 00	Remove Offset from Index
	017E JSR 20 (d3) (01)	Enter Moved Character and Increment
	0181 BNE 40 P5*	Repeat?
	0183 CLC 18	Clear Carry
	0184 LDA A9 01	Set A to page 3
	0186 STA 85 (2E)	Set Cursor to Page 3
	0188 LDA A9 E0	Set A to start of last line
	018A STA 85 (Ed)	Set Cursor to Start of last line
014A	018C BCS b0 bC*	Finish if carry set

(Continued on next page.)



Table III (Continued)

018E	JSR	20 (Cb)	(01)	Clear last line
0191	SBC	38		Set Carry
0192	BCS	B0 F0*		Restore Cursor to start of last line
0194	LDA	A5 (Ed)		Cursor Up/Get Cursor
0196	SBC	38		Set Carry
0197	SBC	29 20		Move up one line
0199	STA	85 (Ed)		Restore Cursor
014A ← 019b	BCS	B0 Ad*		Underflow of page?
019d	DEC	06 (EE)		Yes, decrement page
019f	LDA	A9 01		Set A to Page 1
01A1	CMP	05 (EE)		Did screen underflow?
014A ← 01A3	BNE	40 A5*		No, Finish
01A7 ← 01A5	BEQ	F0 A0*		Yes, Home Cursor
01A7	DEC	06 (Ed)		Cursor Left/Decrement Cursor
01A9	LDA	A9 FF		Set A to page underflow
01Ab	CMP	05 (Ed)		Test for page underflow
019d ← 01Ad	BEQ	F0 EE*		Change Page if off Page
014A ← 01Af	BNE	40 99*		Finish if on page
01b1	LDA	A5 (EE)		Cursor Erase to EOS/Get Cursor
01b3	PHA	48		Save upper cursor location
01b4	LDA	A5 (Ed)		Get lower cursor location
01b6	PHA	48		Save lower cursor location
01b7	JSR	20 (Cb)	(01)	Clear to End of Screen
01bA	PLA	68		Get lower cursor location
01bb	STA	85 (Ed)		Restore lower cursor
01bd	PLA	68		Get upper cursor location
01be	STA	85 (EE)		Restore upper cursor
014A ← 01c0	BNE	40 88*		Finish
01c2	LDA	A9 00		Cursor Home Cursor
01c4	STA	85 (Ed)		Set lower cursor to zero
01c6	LDA	A9 02		Put page 2 in A
01c8	STA	85 (EE)		Set upper cursor to 0200
01cA	RTS	60		Return to main program
01cb	LDA	A9 20		Cursor Enter Space
01cd	JSR	20 (d3)	(01)	Enter space via Sub
01d0	BNE	d0 F9*		Repeat if not to end
01d2	RTS	60		Return to main program
01d3	STA	91 (Ed)		Cursor Increment/Increment store
01d5	INC	R6 (Ed)		Increment Cursor
01d7	BNE	d0 06*		Overflow?
01d9	INC	R6 (EE)		Yes, Increment cursor page to 03
01db	LDA	A9 04		Load A with page 4
01dd	CMP	05 (EE)		Test for Overflow
01df	RTS	60		Return to main program

NOTES: IRQ vector must be stored in 17F3 00 and 17F4 01.

Total available stack length is 32 words. Approximately 16 are used by operating system, cursor, and scan program. Stack must be initialized to 01FF as is done in KIM-1 operating system. For 30 additional stack locations, relocate subroutines starting at 0102 elsewhere.

To protect page, load 00F3 04. To enable entry load 00F3 00.

Cursor address is stored at 00ED low and 00EE high on page zero.

To display cursor load 014d 80. To not display cursor load 014d 00.

\* Denotes a relative branch that is program length sensitive.


( ) Denotes an absolute address that is program location sensitive.

you can run  $8 \times 32$ ,  $4 \times 64$ ,  $1 \times 64$ , or even  $1 \times 8$  character formats. All this takes is software changes, and the circuitry of the TVT-6 remains the same.

**Initial Debugging.** At this point, there should be no IC's in the sockets of the TVT-6 board assembly. Start by connecting the LENGTH jumper to 32 and the CURSOR jumper to YES on the TVT-6 board. (Note: These points are pads located at the center of the circuit board, not the edge-connector contacts.) Temporarily insert a jumper wire between

pins 3 and 14 on the IC5 socket. Center the two position control potentiometers and install IC1, IC2, and IC6 in their respective sockets.

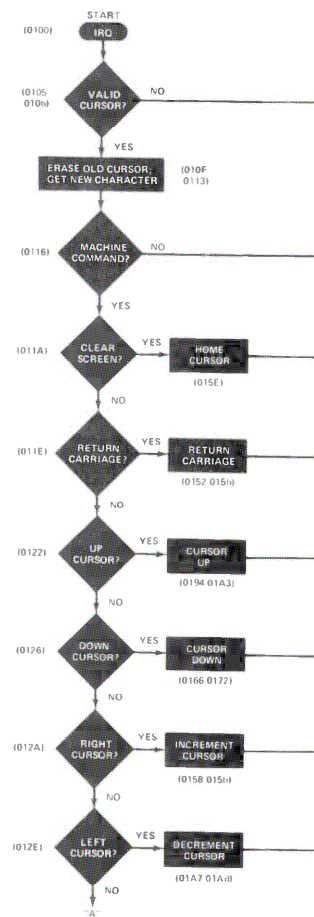Connect your video monitor to the TVT-6 board and power up the system. Check for the presence of the SCAN instructions (see PROM Truth Table in Fig. 1 of Part 1) at hex locations 8000 through 8020. Write a simple program that jumps to a subroutine at location 8000 and then loops. Single-step through this program to verify proper operation of the SCAN instruction. Do not



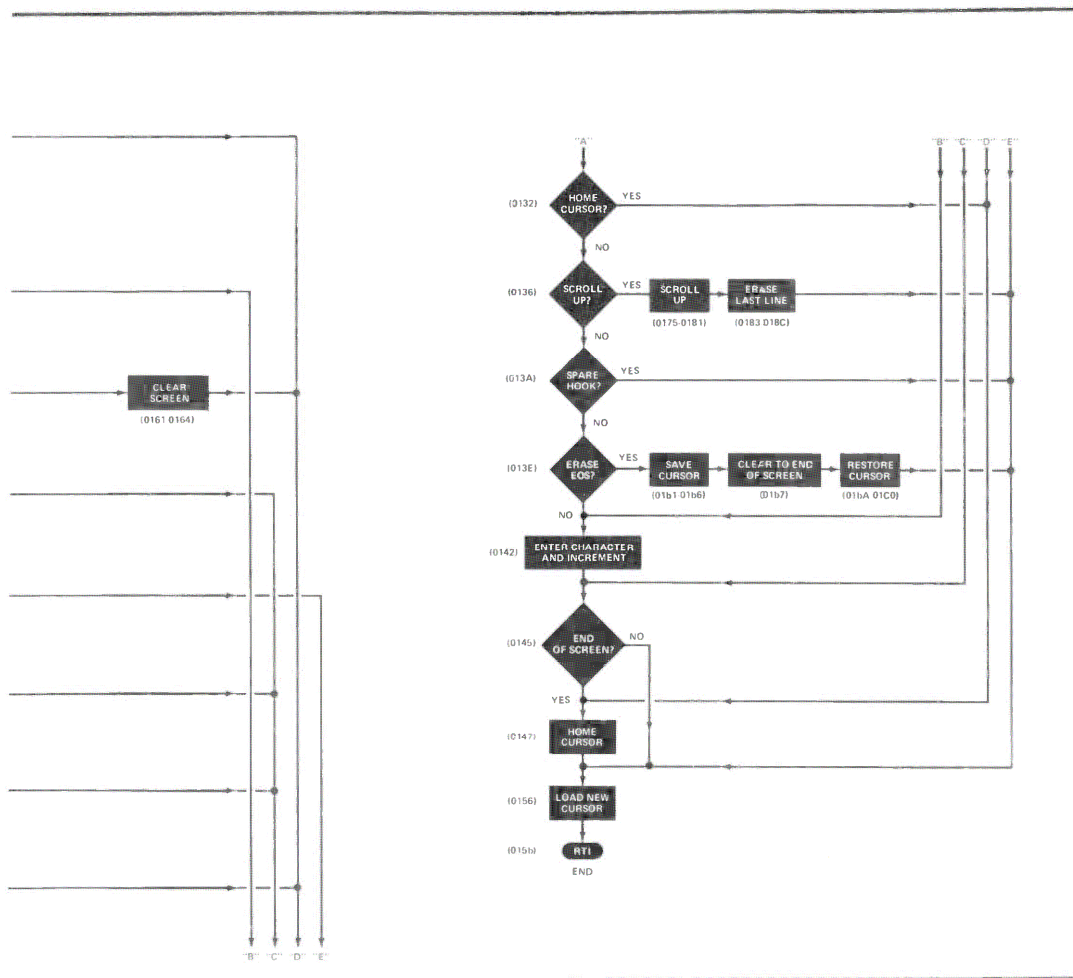
#### USING THE TVT-6 WITH OTHER POPULAR MICROPROCESSORS

Both parts of this article have used the TVT-6 with the 6502 microprocessor-based KIM-1 microcomputer. Here is how to use the TVT-6 in  $\mu$ C's that use other popular microprocessors.

**6800.** The 6800  $\mu$ P is very similar to the 6502 and, therefore, is easiest to convert. The SCAN microprogram can be LDAB(C6) for words 0 through 30 and RTS(39) for word 31. A literal translation of the tightest part of the SCAN program (1D;1782 through 178C) is: STA(B7); JSR(BD); ADDA(8B); CMPA(81); BCC(24). This routine requires 25  $\mu$ s to cycle through as compared to the 21  $\mu$ s required for the 6502.





**8080.** A stock 8080  $\mu$ P can normally change its program counter once every 2  $\mu$ s, but it can be "tricked" into doubling its speed during a SCAN microprogram by driving the usual address line A9 of the display memory from SYNC. The SCAN microprogram is then NOP(00) for words 0 through 30 and RET(A9) for word 31. A tighter than literal translation of the SCAN program (1D;1782 through 178C) is: STAXB(02); CALL(AD); ADD(82); CMP(BB); JNC(DB), which requires 24  $\mu$ s to cycle through. Here, the TVT-6 address lines A5 through A1 must be relabelled A4 through A0, respectively.

**Z80.** The Z80  $\mu$ P can use 8080-developed software with speed-doubling scans, or it can simply be run faster, al-

lowing the program counter to change once every microsecond. Use a literal translation of the program for the 6502.

**12 Address Line  $\mu$ P's.** The four upper address lines of 12 address line  $\mu$ P's can be decoded to allow normal operation, 8 to 12 lines of scan, a vertical sync pulse, an operating return system, and an optional "page-change" command. This leaves a 256-character page on the bottom eight bits, and the "page-change" command can be latched to change to any number of additional pages, as required.

**General Hints.** Horizontal scan should last at least 62, 63.5, or 64  $\mu$ s for conventional horizontal-frequency operation. The microprogram scan must end exactly this number of microseconds lat-

er for each horizontal line in the total scan program. The total number of lines must produce a vertical frequency between 59.9 and 60.1 Hz per field. Note that a portion of the RTS time will be spent during the active (microprogram) scan time. Horizontal scans that last longer than 85  $\mu$ s may make it difficult to obtain TV interface.

You can shorten a blank microprogram active scan by an even number simply by jumping ahead when you call your subroutine. For example, a JSR 8000 may produce a 32-character scan, while a JSR 8002 can produce a 30-character scan. This approach can come in handy when there is a need for equalizing scan lengths between character rows and during vertical retrace.

TABLE IV

16 line X 64 character per line TVT6 Raster Scan:

μP - 6502      Start - JMP 17AA      Displayed 0000 - 01FF  
 System - KIM-1      End - Interrupt      Program Space 1780-17bE

HS	VS	L4	L2	L1	O	V8	V4	V2	V1	H32	H16	H8	H4	H2	H1
Upper Address								Lower Address							

1780	LDA	A9	80												
1782	STA	8d	(87)	(17)											
1785	JSR	20	00	80											
1788	ADC	69	08												
178A	CMP	C9	00												
178C	BCC	90	F4*												
178E	TAX	AA													
178F	LDA	Ad	(86)	(17)											
1792	BCS	b0	00												
1794	JSR	20	04	80											
1797	BCS	b0	00												
1799	ADC	69	3F												
179b	STA	8d	(86)	(17)											
179E	TXA	8A													
179F	JSR	20	00	80											
17A2	ADC	69	C0												
17A4	CMP	C9	84												
17A6	BCC	90	dA*												
17A8	BCS	b0	00												
17AA	CLD	d8													
17Ab	JSR	20	00	C0											
17AE	LDX	A2	22												
17b0	LDA	A9	00												
17b2	STA	8d	(86)	(17)											
17b5	CLC	18													
17b6	BCS	b0	00												
17b8	JSR	20	00	80											
17bb	DEX	CA													
17bc	EMI	30	C2*												
17be	BPL	10	F5*												

NOTES: TVT6 must be connected and scan microprogram FROM (IC1) must be in circuit for program to run.



Step 1785 goes to where the upper address stored in 1787 and the lower address stored in 1786 tells it to. Values in these slots continuously change throughout the program.

Normal program horizontal frequency is 11,764.705 Hz.  
 Vertical Frequency is 60,024 Hz. 85 us per line;  
 196 lines. Character time 1 us. 160 active lines,  
 36 retrace. Needs TV set adjustment and possible modification (hold and width).

\* Denotes a relative branch that is program length sensitive.

( ) Denotes an absolute address that is program location sensitive.

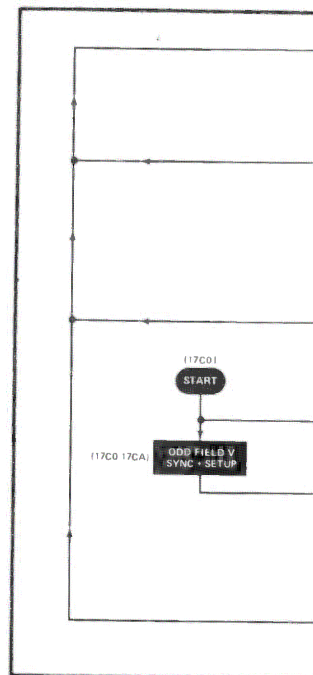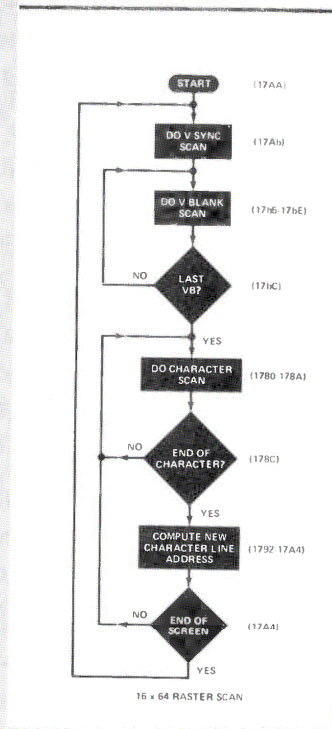TVT6 length jumper must be in "64" position.



POPULAR ELECTRONICS

proceed beyond this point until you are certain that the SCAN subroutine is operating properly. (Critical waveforms to be observed with an oscilloscope are illustrated in Fig. 7 using the program listed in Table II.)

Insert IC3 into its socket and load the program given in Table II. (Never install an IC in a powered circuit; always turn off the power, install the IC, and power up again.) Set the address to 17Ad and depress GO. Using an oscilloscope, check at test point VR for the presence of a 60-Hz pulse. Switch the scope to line-sync and observe that the pulse remains fixed or drifts very slowly across the screen. Again, do not proceed until you are certain that the SCAN program is operating properly.

Install all remaining IC's, except IC5, in their respective sockets on the TVT-6 board. At this point, the screen should be filled with a stable display of 512 cursor boxes. Viewed up close, the boxes should appear to be "hiding" characters. Do not proceed until you have the indicated display.


Checking with Fig. 7, particularly with respect to the LOAD and CLOCK on IC8 (Fig. 7A) verify whether or not the appropriate waveforms are present. If they are, remove the jumper wire from the IC5 socket and install IC5. Now, the screen of the monitor should have displayed on it a full array of characters with about half of them winking cursor blocks. Load the following hex numbers into memory, starting at location 0200:



20, 20, 20, 50, 4F, 50, 55, 4C, 41, 52, 20, 20, 45, 4C, 45, 43, 54, 52, 4F, 4E, 49, 43, 53, 20, 20, 54, 56, 54, 2D, 36, 20, 20. Return to address 17Ad and depress GO. The top display line should now read "POPULAR ELECTRONICS TVT-6" and be indented three spaces. If all is well to this point, you can begin feeding in your cursor programs, add external keyboard and/or cassette loads and dumps, etc.

Should you encounter problems with your TVT-6, always begin debugging by using the 16 x 32 format on a KIM-1, even if you plan on using longer line lengths or plan to translate the code into another coding system. Note that the translation *must* be at the machine-language level because the SCAN program must provide the exact number of machine cycles as well as the proper sequencing. The 64-character lines will require some adjustments to be made in the monitor TV receiver's horizontal circuit as detailed earlier.

**Closing Remarks.** We have presented here full construction and operating details for a very versatile and inexpensive TV typewriter for use with the KIM-1 microcomputer. If you have a computer that uses a microprocessor other than the 6502 used in the KIM-1, we refer you to the box for use details. ◇

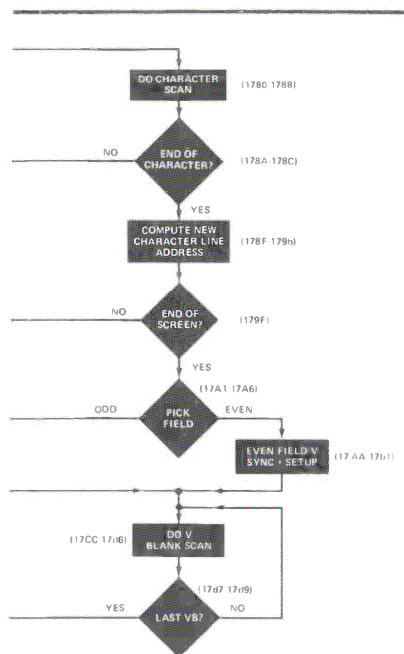

AUGUST 1977

TABLE V

CRUNCHER THE BEAR Program for a 32 line X 64 character per line TVT-6 raster scan:

μP - 6502 Start - JMP 17C0 Displayed 0000-07FF  
System - KIM-1 End - Interrupt Program Space 1780-17dA

HS	VS	L4	L2	L1	V16	V8	V4	V2	V1	N32	H16	H8	H4	H2	H1
Upper Address								Lower Address							

1780	LDA	A9	80												
1782	STA	8d	(87)	(17)											
1785	JSR	20	00	80											
1788	ADC	69	10												
178A	CMP	C9	C0												
178C	BCC	90	F4*												
178E	PHA	48													
178F	LDA	Ad	(86)	(17)											
1792	ADC	69	3F												
1794	STA	8d	(86)	(17)											
1797	PLA	68													
1798	JSR	20	0C	80											
179b	ADC	69	C0												
179d	CMP	C9	88												
179F	BCC	90	E1*												
17A1	LDA	Ad	(81)	(17)											
17A4	ADC	69	78												
17A6	BCC	90	0C*												
17A8	LDX	A2	22												
17AA	LDA	A9	80												
17AC	STA	8d	(81)	(57)											
17AF	LDA	A9	88												
17b1	STA	8d	(9E)	(17)											
17b4	LDA	A9	00												
17b6	STA	8d	(86)	(17)											
17b9	LDY	A0	06												
17bb	DEY	88													
17bc	BPL	10	Fd												
17bE	BCS	b0	0C*												
17C0	LDA	A9	88												
17C2	STA	8d	(81)	(57)											
17C5	LDA	A9	90												
17C7	STA	8d	(9E)	(17)											
17CA	LDX	A2	23												
17CC	JSR	20	3F	80											
17Cf	PHA	48													
17d0	PLA	68													
17d1	CLD	d8													
17d2	CLC	18													
17d3	JSR	20	00	80											
17d6	DEX	CA													
17d7	BMI	30	A7*												
17d9	BPL	10	F6*												

NOTES: TVT6 must be connected and scan microprogram FROM IC1 must be in circuit for program to run. TVT6 length jumper must be in "64" position.

Step 1785 goes to where the upper address stored in 1787 and the lower address stored in 1789 tells it to. Values in these slots continuously change throughout the program.

Step 1781 is 80 for even fields and 88 for odd fields. Step 179E is 88 for even fields and 90 for odd fields.

Both 17AC and 17C2 require that page 17 be enabled when page 57 is addressed. This is done automatically with KIM-1 circuitry.

Note that 2K worth of contiguous memory from 0000 to 07FF is needed. This takes a KIM-1 modification. Both sets of 1k words must share a common upstream tap but be separately enabled.

Normal program horizontal frequency is 11,764.705 Hz. Vertical Frequency is 59.8712 Hz. For 60 Hz vertical use 1.002150 MHz crystal. 85 us per line; 196.5 interlaced lines per field; two fields per frame. One us character time, 160 active lines per field. Needs TV set adjustment and possible modification (hold and width).

\* Denotes a relative branch that is program length sensitive.

( ) Denotes an absolute address that is program location sensitive.



# Hex-to-ASCII Converter for your TVT-6

*Simple module produces op-code  
display for entire computer.*

BY DON LANCASTER

**T**HE LOW-COST "Hex-to-ASCII Converter" described here allows you to simultaneously display the contents of every register, stack location,


and memory slot in your microcomputer. The converter fits easily between the TVT-6 (July 1977) or most any other TVT and the  $\mu$ C with which it is working.

In operation, the video monitor used in the system automatically converts and displays the hex op codes for the ASCII character set. This allows your TVT to act as a super "front panel" that permits you to check as many memory locations as there are in your system. This includes all registers, accumulator, stacks, RAM and ROM programs, I/O, or anything else connected to the system. Properly used, the converter is also an excellent debugging tool.

The complete hex-to-ASCII converter is built on a single compact printed circuit board. The circuit itself consists of three low-cost IC's and only five other parts.

**About the Circuit.** As shown in Fig. 1, the eight input lines from the display memory that normally drive the TVT character generator are intercepted and split into upper- and lower-case charac-

(Continued on page 51)

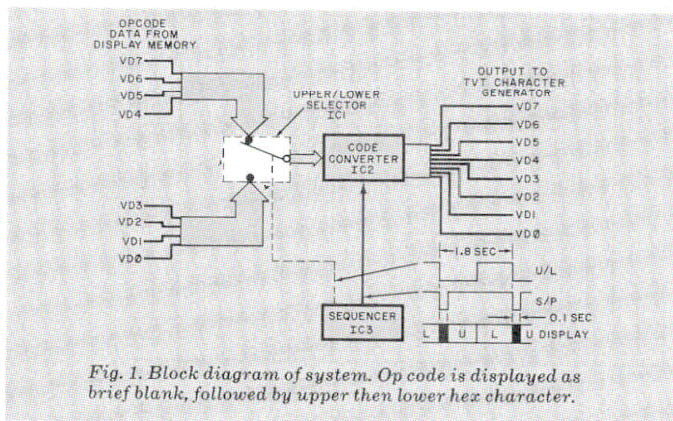



WORD	NOTES	8/17	7/16	6/15	5/14	4/13	3/12	2/11	1/10
0	Blank	0	0	0	0	0	0	0	0
1	"	0	0	0	0	0	0	0	0
2	"	0	0	0	0	0	0	0	0
3	"	0	0	0	0	0	0	0	0
4	"	0	0	0	0	0	0	0	0
5	"	0	0	0	0	0	0	0	0
6	"	0	0	0	0	0	0	0	0
7	"	0	0	0	0	0	0	0	0
8	"	0	0	0	0	0	0	0	0
9	"	0	0	0	0	0	0	0	0
10	"	0	0	0	0	0	0	0	0
11	"	0	0	0	0	0	0	0	0
12	"	0	0	0	0	0	0	0	0
13	"	0	0	0	0	0	0	0	0
14	"	0	0	0	0	0	0	0	0
15	"	0	0	0	0	0	0	0	0
16	0	0	0	0	0	0	0	0	0
17	1	0	0	0	0	0	0	0	0
18	2	0	0	0	0	0	0	0	0
19	3	0	0	0	0	0	0	0	0
20	4	0	0	0	0	0	0	0	0
21	5	0	0	0	0	0	0	0	0
22	6	0	0	0	0	0	0	0	0
23	7	0	0	0	0	0	0	0	0
24	8	0	0	0	0	0	0	0	0
25	9	0	0	0	0	0	0	0	0
26	A	0	0	0	0	0	0	0	0
27	B	0	0	0	0	0	0	0	0
28	C	0	0	0	0	0	0	0	0
29	D	0	0	0	0	0	0	0	0
30	E	0	0	0	0	0	0	0	0
31	F	0	0	0	0	0	0	0	0

0—WHITE; 1—BLACK

Fig. 3. Truth table for PROM IC2.


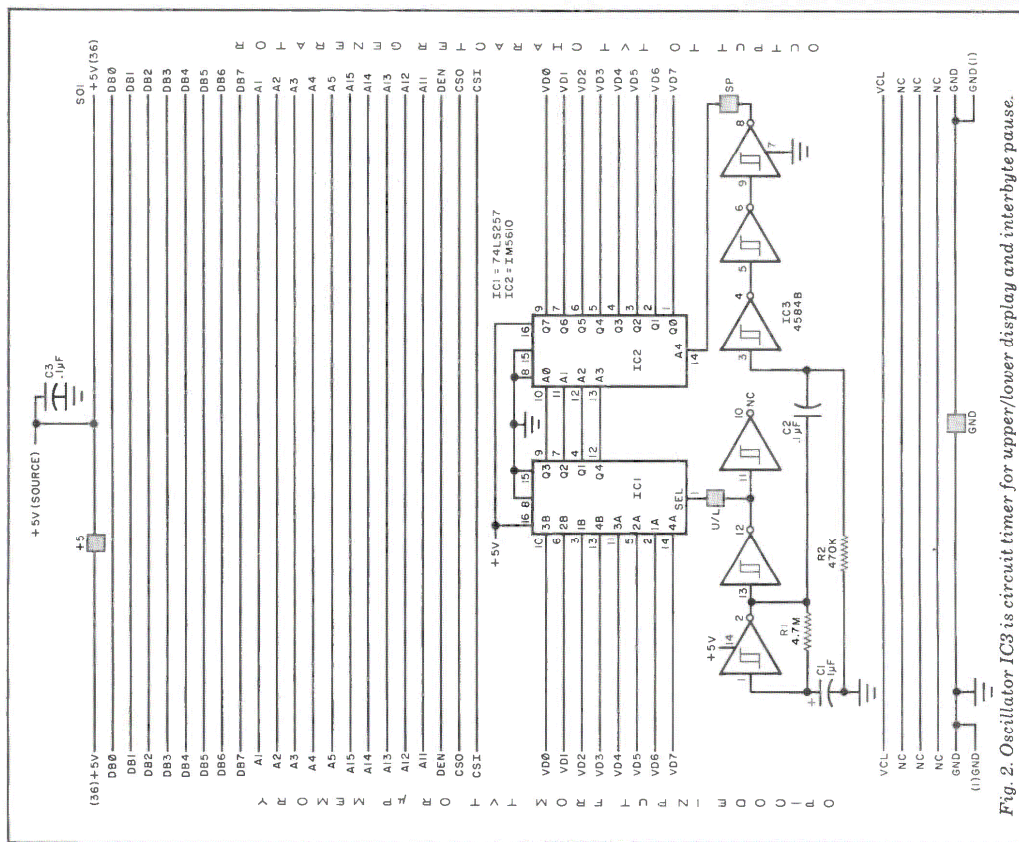


Fig. 2. Oscillator IC3 is circuit timer for upper/lower display and interbyte pause.

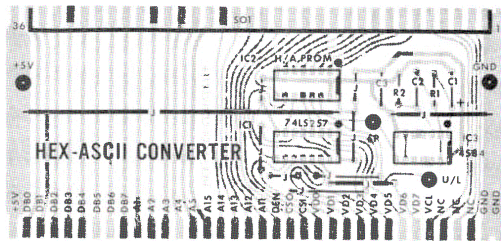



#### PARTS LIST

C1—1- $\mu$ F, low-leakage tantalum electrolytic capacitor  
 C2, C3—0.1- $\mu$ F Mylar capacitor  
 IC1—74LS257 quad 1-of-2 data selector  
 IC2—1M5610 or similar 32X8 bipolar tristate PROM (programmed in accordance with Fig. 3)  
 IC3—4584B CMOS hex Schmitt trigger  
 R1—4.7-megohm, 1/4-watt resistor  
 R2—470,000-ohm, 1/4-watt resistor  
 SO1—36-contact, single-entry edge connector with contacts located on 3.96-mm centers  
 Misc.—Sockets for IC's (one 14-pin, two 16-pin); press-fit test point terminals; printed circuit board; jumper wire; insulated sleeving; solder, etc.  
 Note: The following items are available from PAIA Electronics, Box 14359, Oklahoma City, OK 73114: No. HAC-1B etched and drilled pc board for \$4; No. HAC-1P programmed IC2 for \$5; No. HAC-1K complete kit of all parts for \$14.95. All prices postpaid.

Fig. 4. Actual-size etching and drilling guide (right) and component layout (above) for the pc board. The board is connected between the TVT-6 and the KIM-1 microcomputer.



(Continued from page 49)

ters of four bits each. These two hex characters are alternately routed to a PROM that converts the hexadecimal input code to the equivalent ASCII output. The resultant display alternately flashes the upper hex character and then the lower hex character, with both appearing on-screen at the same location. Each character is displayed for slightly less than a second. A brief space command is sent to the PROM during the transition from the lower character of one set to the upper character of the following set.

To identify the memory locations, an overlay can be used on the CRT screen of the video monitor, or a china marker can be used to label the operating registers and other important slots with which you are working. If the TVT-6 is being used with the "Cruncher the Bear" mode in the August 1977 issue, it is possible to

simultaneously display the 4096 hex characters that result from the 2048 opcode words simultaneously.

The complete schematic diagram of the converter is shown in Fig. 2 and the coding for the 32  $\times$  8 code-converter PROM is shown in Fig. 3.

Integrated circuit IC1 (Fig. 2) is used as a four-pole, double-throw data selector that drives IC2, the code converter. The hex CMOS Schmitt trigger (IC3) serves as a symmetrical oscillator that is used for automatically selecting the upper and lower character and to generate the brief blanking pulse that indicates a new character display.

**Construction.** The converter circuit is best assembled on a printed circuit board. The etching and drilling and components placement guides for the pc board are shown in Fig. 4.

Note on the components placement guide that 10 jumpers are used to interconnect various pads on the board. Only two of these jumpers, indicated by heavy lines, require insulated sleeving to be slipped over them before installation to preclude the possibility of accidental short circuits.

Install and solder into place press-fit terminals at the four test points labelled +5, GND, SP, and U/L. Then install and solder into place the three capacitors, two resistors, and the 36-contact connector. Sockets are recommended for the three IC's. Once the sockets are installed and soldered into place, install the IC's in their respective locations, taking care to properly orient them.

**Checkout.** To initially check out the converter, connect the TVT-6 to the KIM-1 microcomputer and use the



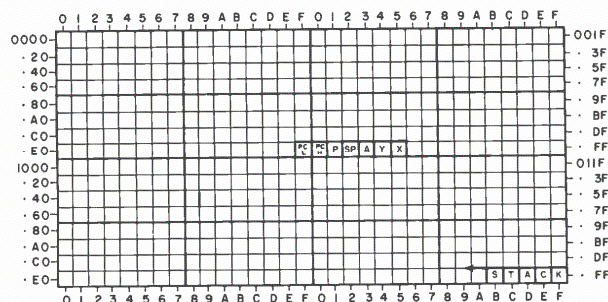


Fig. 5. Overlay mask for the KIM-1. All internal registers are displayed simultaneously with the entire stack.

512-character, page 2 and page 3 display of Table II in the August 1977 TVT-6 article. Make sure that the system is operating properly. Then remove the power and connect the hex-to-ASCII converter between the TVT-6 and  $\mu$ C. Power up again, reload the program, and run the computer. The original ASCII display should now appear in hexadecimal op code.

Test point U/L should have a 1.8-second square wave, while test point SP should be high for 1.7 seconds and low for 0.1 second. It is possible to "force

feed" control signals into these test points. Connecting test point SP to +5 volts displays the characters; grounding SP blanks the screen. Connecting test point U/L to +5 volts displays the lower four bits, while grounding it displays the upper four bits.

**Operation.** If you are planning to run Table II from the August 1977 TVT-6 article, the usual display is of pages 02 and 03. This can be converted to a page 00 and 01 display by changing instruction 17AA to 82 and 17d2 to 80.

An overlay that identifies the stack and all important machine registers is shown in Fig. 5. The physical size of the overlay, of course, depends on the size of the CRT used in the monitor. A sharp china marker can alternatively be used as a low-cost, workable substitute for the overlay.

To debug a program, simply use the hex-to-ASCII converter with the KIM-1 operating system in the single-step mode. Each time the operating system returns to the keyboard display mode, all registers have their values reloaded into the proper slots shown in Fig. 5.

Hit AD 17 80, switch to SST OFF, and press GO to view the accumulator, stack pointer, program counter, status register, and the X and Y index registers simultaneously. To return to the keyboard display mode, simply press ST.

The Hex-to-ASCII converter can be used between memory and the character generator of many other TVT systems as long as an 8-bit word is used in the TVT's page memory. You can ignore the "Pass-through" lines on the converter, or you can redefine them in any way you need. The converter's processing delay is about 100 ns, which is fast enough usually to be ignored. ◇





# Letters

## USE THE OLD APPROXIMATIONS

I am sure you provided a service for many readers with the discussion in "Accurate Milliammeters On a Budget" (June 1977). As an

old Ham, I wonder why you did not give the old approximations for shunt calculations and for determining the internal resistance of a meter movement. They yield results whose scalar accuracy is better than that of the meters themselves.—D. Conover, WA6MVZ, La Mesa, CA.

*The ones presented are more accurate, though both provide results more accurate than meters themselves.*

## SHORTWAVE-LISTENING BOOSTER

Your articles on shortwave listening and reports on SW receivers are excellent. I am just getting started as an SWL'er, and POPULAR

ELECTRONICS is helping me a great deal in my new hobby. Please keep Harry L. Helms's articles, the DX Listening column, and Shortwave Broadcasts Charts coming. —Paul Semenza, Tarrytown, NY.

## TRANSPOSING BITS

In the "Pixie Graphics Display" article (July 1977), if the data pins on the 1861 IC are transposed, the bits will be displayed with the LSB first and the MSB last. This arrangement will be a little easier to use when calculating a display from software or an A/D converter. Just transpose D7 and D0, D6 and D1, D5 and D2, and D4 and D3.—Richard DeLombard, Huron, OH.



# COSMAC VIP

## The computer you can build for the whole family to enjoy.

RCA's new low-cost Video Interface Processor lets you create and play video games, generate graphics, and develop microprocessor control functions. And it's just \$275.\*

Here is an elegant computer-on-a-card. Compact. Clean. Uncluttered. Yet powerful. And the whole idea behind it is fun. For the most serious hobbyist or any member of the family who can get into the challenge, entertainment and education it offers.

The COSMAC VIP is easy to program. And has its own interpretive language to make programs simple to create.

The VIP is supplied in kit form, with a cookbook written by hobbyists for hobbyists. It contains complete instructions for assembly, set-up and

operation. And it includes programs for twenty games. Some strictly fun. Some educational. All ready to load and record into your cassette.

Then all you have to do is hook your VIP up to a video monitor or your B/W TV through an rf modulator.

The VIP computer kit is available through these Distributors: American Used Computer Corporation, Arrow Electronics, Inc., Cramer Electronics, Inc., Hamilton-Avnet Electronics, Schweber Electronics Corp., Semiconductor Specialists, Inc., and Taylor Electric Co.

For additional information write RCA Solid State, VIP Marketing, Box 3200, Somerville, NJ 08876.

\*Suggested retail price, optional with Distributors.

# RCA

## TVT-6 DISPLAY UNCROWDING

We built a "TVT-6 Video Display" unit (July 1977) and interfaced it with a KIM microcomputer. While following your published debugging instructions, we noted that our video monitor was displaying letters that were not complete because they were crowded together. Signal tracing revealed that the LOAD signal was okay but the CLOCK signal presented only 3 cycles/ $\mu$ s instead of the specified 6 cycles/ $\mu$ s. I tried replacing C5 with a smaller value of capacitance, with the result that the display was greatly improved. After some cut-and-try experimenting, we ended up with a 390-pF value and a perfect display. Anyone who runs into a similar problem with one of these video-display units might want to take note of our experience. —David A. Byrd, Memphis, TN.

## ENLARGER REGULATOR PRECAUTION

Since your enlarger voltage-regulator project in the November 1977 issue is specifically aimed at the color darkroom worker, it would be well to point out that this regulator cannot be used with some enlarger color heads that have built-in filtration. Such heads usually have low-voltage, high-intensity lamps and transformer power supplies. Use of a dc supply, like that shown for the regulator in the November issue, can result in damage to the transformer. —Bennett Evans, New York, NY.

# Out of Tune

In "How to Convert a 'Four Banger' for Stopwatch Functions" (August 1977), the IC2 and IC3 designations are shown transposed in Fig. 2. The Fig. 1 schematic diagram is correct.

In the Parts List in "Build a Digital Camera Shutter Timer" (August 1977), DIS1 through DIS5 are described as common-anode displays; they are actually common-cathode displays.