
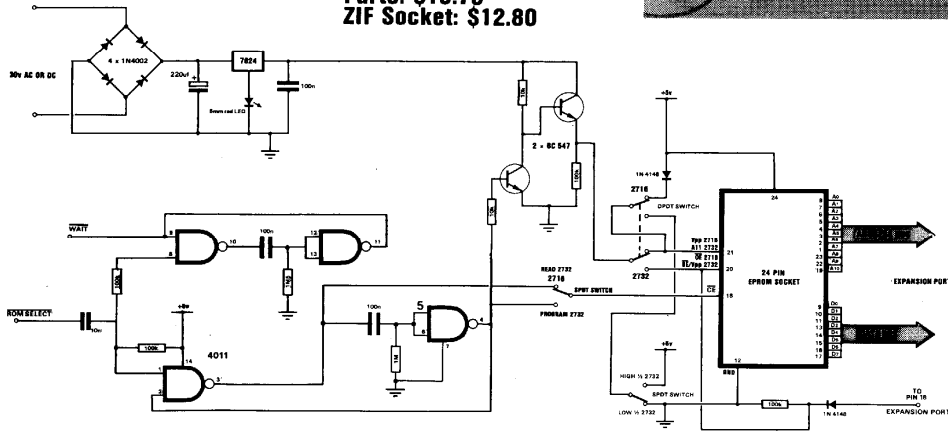


EPROM BURNER

 PC Board: \$3.50
Parts: \$13.70
ZIF Socket: \$12.80



An EPROM BURNER is the greatest thing to hit the TEC since the regulator was put under the board!

It adds the versatility you have wanted for ages.

To be able to save a program in a permanent form is the final goal of programming.

The TEC RAM CARD and EPROM BURNER combine to make a system capable of generating, testing and producing programs in hard form which can be saved, stored or sold - programs capable of emulating almost any task imaginable.

You can take any project from any magazine or book and convert it to a micro design with a consequent saving in parts, space and cost. Its capability can be increased and its reliability improved by using a tried-and-proven micro design.

By using the NON-VOLATILE RAM as the intermediate stage and the MON 2 monitor (with insert and delete functions) for the production of the program, you can generate, and have running, any machine code program, before burning it permanently into an EPROM.

Burning an EPROM is the final stage and you should be thoroughly satisfied with the performance of a program BEFORE-HAND as it cannot be changed once it is burnt.

This is not entirely true as you can change some values and 'burn-down' any value to zero.

This is an important fact to remember when programming and we will explain what we mean:

EPROMs are purchased in blank form and this means the cells (of which there are 16,384 in a 2716 and 32,768 in a 2732) do not hold any charges of electricity.

Due to buffering circuits in the EPROM, the output from a blank device will be a set of HIGHs. Advantage is made of this as you will see. Eight cells are accessed at a time and if the value is read, it will be 1, 1, 1, 1, 1, 1, 1, 1. But we don't want to read a blank ROM - we want to program it with useful commands and data.

In Hexadecimal notation, the blank EPROM produces FF's from each set of 8 locations. This is called a byte and as we burn each byte in the EPROM burner, we convert the FF's into a lower value. If we don't burn a particular location, its value remains FF.

If we burn all 8 cells, the resulting value will be 00 and the designers of micro-processors (such as the Z-80) have given a very clever command to this value. It is "NO-OPERATION" in which the processor glides over the location without affecting any of the remaining program.

PARTS LIST

- 2 - 10k
- 3 - 100k
- 1 - 1M
- 1 - 1M5
- 1 - 10n greencap
- 3 - 100n
- 1 - 220uf 35v electro
- 2 - 1N 4148 signal diodes
- 4 - 1N 4002 power diodes
- 1 - red LED
- 2 - BC 547 transistors
- 1 - 4011 IC
- 1 - 7824 regulator
- 1 - 14 pin IC socket
- 1 - 24 pin wire-wrap socket
- 1 - 24 pin DIP header
- 1 - 24 pin ZIF socket 12.80 EXTRA
- 2 - 10cm hook-up flex
- 2 - matrix pins (for TEC)
- 2 - matrix pin connectors
- 4cm heat-shrink tubing
- 1 - 6BA nut and bolt
- 3 - DPDT slide switches
- 1 - EPROM BURNER PC BOARD

The advantage of having a No-Operation command as 00 means any location can be 'burnt-down' to 00 if it is required to be removed.

This is where the term 'burn-down' comes from. Whenever an EPROM is burnt or programmed, the value produced is less than the starting value for the location.

We said values cannot be changed once burnt, but in some cases you can reduce the value if the following conditions are met:

The main criteria is: **the cells you wish to change must be 1's.**

The table below shows the values which can be burnt down and those which cannot.

BURN-DOWN TABLE:

	F	E	D	C	B	A	9	8	7	6	5	4	3	2	1	0
ANY VALUE	C	8	8	8	8	8	0	6	4	4	0	2	0	0	0	0
ANY VALUE	A	9	4	0	0	0	0	5	4	0	0	0	0	0	0	0
ANY VALUE	8	8	5	4	1	0	0	3	2	1	0	0	0	0	0	0
ANY VALUE	6	6	5	4	1	0	0	3	2	1	0	0	0	0	0	0
ANY VALUE	4	4	1	0	0	0	0	1	0	0	0	0	0	0	0	0
ANY VALUE	2	2	1	0	0	0	0	0	0	0	0	0	0	0	0	0
ANY VALUE	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

The bold value can be burnt down to the values shown in the column.

Values cannot be 'burnt-up' as we cannot produce HIGHS in an EPROM BURNER.

The only way we can restore HIGHS or 1's to the cells of an EPROM is to put it under an ultra violet light source, whereby ALL the locations will be erased and converted to 1's.

THE CONCEPT

Locations in an EPROM can be burnt if a voltage of 25v is applied to the Vpp pin and pin CE pulsed for 50 milliseconds.

The cells which will be given a charge of electricity will depend on the address which is being accessed and the value of data present on the data lines.

These are the only requirements and programming can be done with a simple set of switches. Unfortunately this would take an enormous length of time as 11 switches would be required for the address lines 8 switches for the data lines and each would have to be set for each byte of information.

A 2716 contains 2048 bytes and if a byte is burnt incorrectly, the whole procedure would have to be repeated.

The other inconvenience is all the bytes in the program would have to be converted to binary so that they can be loaded via the switches.

All this would take so long that the operation of burning would become a head-ache.

By using the TEC, the address values increment automatically as the program advances and the values of data are automatically converted to binary when each location is being burnt. This means you can program in Hex.

In this way an hours' work is converted to only a few minutes.

This is the function of an EPROM BURNER. It connects an EPROM to the address and data buses, provides the necessary 50 millisecond programming pulse and the 25v supply.

To hold the data steady on the data bus for the duration of the burn, it is necessary to HALT the computer. This is achieved by using another monostable connected to the WAIT line, with a pulse length which is slightly longer than 50 milliseconds.

When you think of it, 50 milliseconds is 20Hz and when you include a short additional delay for the wait function and a number of machine cycles for the execution of a program to carry out the burn operation, you arrive at a burn rate of about 15 locations per second.

Divide this value into the number of locations you wish to burn and you arrive at the length of time for burning an EPROM. That's why it may take a minute or so.

HOW THE CIRCUIT WORKS

The circuit is very simple and consists of a number of building blocks which come together via the ROM SELECT line from the computer.




Starting at the top of the diagram, the 25v is derived from a 7824 voltage regulator which has been 'jacked up' by 1.7v by the inclusion of a red LED in the COMMON line. This gives an output of 25.7v and by the time it reaches the EPROM, a voltage drop of .5v has occurred across the switching transistor. This transistor is switched via the output line of the 50 millisecond monostable.

The 25v line need not be switched ON and OFF when programming but must not be present when the EPROM is to be removed from the socket. By switching the voltage as we have done, the EPROM can be removed without damage.

In this article we have included only a very simple burning routine which you can load into 0000 and get the project working.


The final two circuit blocks are monostables or one-shots, created from NAND gates. The lower monostable produces a 50 millisecond delay and the upper a 65 millisecond delay.

   It places data on the data lines, turns on the required address lines and turns on a Chip Select line (located near the edge of the TEC PC).



Switch positions for programming and reading 2716's and 2732's

 The programming pulses differ between the 2716 and 2732.



EPROM BURNER

... cont. from P. 22.

The lower switches must be set for 2716 or 2732.

When burning 2716's the upper switch position does not matter as it is not in circuit.

When burning 2732's the upper slide switch selects the UPPER 2k or LOWER 2k of the 2732.

The switch closest to the EPROM is placed in the upper position when programming 2732's and in the lower position to read them.

This switch is placed in the lower position when programming and reading 2716's. Refer to the set of diagrams before carrying out any operation.

The high voltage is derived from a 30v supply. This can be the TEC POWER SUPPLY or from a 30v AC transformer. Very little current is required, however the voltage must not go below 30v or the regulator will drop out. This is because we are generating 25.7v and the regulator requires 3-4v across it for regulation.

Connection of the EPROM BURNER board to the TEC is via a 24 pin wire-wrap and DIP header plug. The board fits in the expansion socket and requires a WAIT line and ROM SELECT line.

The ROM SELECT line is pin 12 of the 74LS138 and WAIT is pin 24 of the Z-80.

Connect these lines to the TEC and plug the EPROM BURNER board into the expansion socket. Connect the 30v supply and the red LED will illuminate to indicate all is ready.

You can burn a new EPROM or blank locations in an old ROM. You can even burn old locations providing they fulfill the requirements mentioned previously.

THE PROGRAM

The BURN PROGRAM can be placed anywhere in the Monitor ROM or typed into the RAM. If placed in the RAM, it will need to be typed each time an EPROM is to be burnt.

The program is very simple and does not have any checking facility to prevent it burning over previous program.

The absence of this means you can burn or reburn any location(s) anywhere without having to break a safety lock.

The first three lines of the program contain variables which have to be set each time you want to burn an EPROM. For this reason, the three lines must be typed into RAM with a fourth line to provide a call or jump to the remainder of the program. The rest of the program can be located in ROM (at say 0700).

Here's how it is done:

You will need a blank 2716.

The first stage is to transfer the MONitor program into the new EPROM. Load the following into 0800:

```
LD DE 1800      800  11 00 18
LD HL 0000      803  21 00 00
LD BC 06FF      806  01 FF 06
LD A(HL),A      809  7E
LD (DE),A       80A  12
PUSH BC         80B  C5
DJNZ FE         80C  10 FE
DJNZ FE         80E  10 FE
POP BC          810  C1
INC HL          811  23
INC DE          812  13
DEC BC          813  0B
LD A,B         814  78
OR C           815  B1
JR NZ          816  20 F1
Restart 0000    818  C7
```

Make sure the switch selects 2716. Push RESET, GO. The TEC screen will blank for about 2 minutes while the program is burning.

When the screen reappears you can check the operation by addressing 1000 and read the locations. Compare them with 0000 and confirm the program has been transferred.

The next stage is to add the burn routine to the MONitor ROM. This is done at 0700. Change the values at 0800 to:

```
11 00 1F
21 09 08
01 10 00
```

Push RESET GO and the program will be transferred in a few seconds.

You have now produced a MONitor ROM with a burn routine at 0700. Place the new ROM into the TEC and it will start up with 0800.

To use the BURN ROUTINE, type the following at 0800:

```
11 _____ TO: ROM address + 1800H
21 _____ FROM: RAM address
01 _____ No of hex bytes
C3 00 07
```

Programs to be burnt into EPROM are placed at 0900 and can extend to 0FF0. To transfer these programs to EPROM, place the following at 0800:

```
11 00 18
21 00 09
01 F0 0E
C3 00 07      Push RESET GO.
```

EX: 80 byte program at 0900 to 0000 in EPROM:

```
at 0800:
11 00 18
21 00 09
01 80 00
C3 00 07      Push: RESET, GO.
```

A6 byte program at 0A00 to 0180 in EPROM:

```
at 0800:
11 80 19
21 00 0A
01 A6 00
C3 00 07      Push: RESET, GO.
```

40 byte program at 0C00 to 02C0 in EPROM:

```
at 0800:
11 C0 0A
21 00 0C
01 40 00
C3 00 07      Push: RESET, GO.
```

If you type a program at 0800, the BURN ROUTINE can be located at 0900:

```
11 xx xx
21 00 08
01 xx xx
C3 00 07
decrement to 0900 Push: GO, GO.
```

Before starting any programming you should fill the TEC RAM with FF's. This will allow any non-program locations to be transferred and retain the value FF.

To fill RAM with FF's:

```
11 FF FF
D5
C3 03 08
Reset, GO.
```

Programs can be transferred from EPROM to the TEC memory via the following routine:

```
at 0C00:
11 00 08
21 00 10
01 _____ (No of bytes)
ED B0
C7
decrement to 0C00 Push: GO, GO.
```

Program will transfer very quickly - This is not a burn routine but a DUMP ROUTINE which can also be used for the non-volatile RAM project.

Example: 80 bytes in EPROM at 0000 to 0900 in TEC RAM.

```
at 0800:
11 00 09
21 00 10
01 80 00
ED B0
C7      Push Reset, Go.
(0000 in EPROM means page-zero in EPROM).
```

EX: 80 bytes in EPROM at 0630 to 0900 in TEC RAM.


```
at 0800:
11 00 09
21 30 16
01 B0 00
ED B0
C7      Push: Reset, Go.
```

Before attempting any transfer, you must write the necessary program on a piece of paper using one of the examples in the text. Check it carefully then type it into the TEC at 0800 (or other location as explained).

Using the programmer and the non-volatile RAM in conjunction with the TEC will open up lots of possibilities. Programs can be used on the TEC or MICROCOMP and you will begin to see how everything is going together.

EPROM PROGRAMMER REVISITED

Parts \$2.30

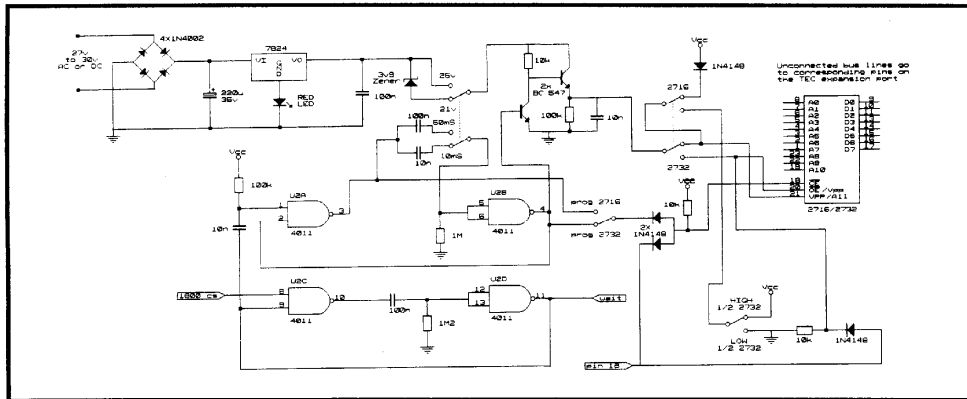

Circuit diagram showing all corrections and modifications

CIRCUIT DIAGRAM CORRECTION

A mistake has been made with the circuit diagram on page 20 in issue 13.

The 100k resistor between pins 8 and 1 of the 4011 does not exist on the board and pin 8 is actually directly connected to the ROM SELECT LINE. It is not coupled through the 10n capacitor (via the 100k mentioned above) as shown.

CIRCUIT UP-GRADES

If your EPROM programmer is working ok and you're completely satisfied with its performance, perhaps it is best left alone. There are two modifications though, that are HIGHLY RECOMMENDED:

The first is the 100k resistor on the left-hand side of the EPROM socket (next to a diode) SHOULD BE REDUCED to 10k. This will allow for far more reliable readings (if yours doesn't read at all or very poorly, then this will almost certainly fix it).

The second is a 10n greencap is connected across the 100k resistor next to the EPROM socket on the right-hand side of the board (when looking at it from the top).

This 10n greencap is to prevent spikes from damaging the EPROM.

There are some other very handy mods to make. This next one will make it possible to read from 2732 (4k EPROMs) without having to slide the

switch across. The BIG advantage of this is that it is possible for the software to read from the 2732 just after you have programmed each location. The software can then diagnose a failure and re-try or abort quickly. The software routine is provided below which will do this for either a 2716 or 2732.

Three additional parts are required for this mod. They are two 1N 4148 diodes and a 10k resistor.

The first diode is soldered between the DIP-HEADER and the EPROM socket. The cathode (the end with the band on it) is soldered to pin 18 of the DIP-HEADER and the anode is soldered to pin 18 of the EPROM socket. Next, the track running between pin 18 of the EPROM socket and the middle of (program 2716 read 2732)/program 2732 switch is cut. The anode of the second diode is soldered to the pin 18 side of the cut and the cathode is soldered onto the middle terminal of the switch. One end of the 10k resistor is soldered to the anode side of the second diode (the end connected to pin 18). The other end of the resistor is soldered to ground.

Once you have fitted this modification, it may be tested by fitting a 4k ROM into the socket and addressing 1000. You should be able to read the contents regardless of the position of the read/program 2732 switch. The high/low switch is still used to select

PARTS LIST

(For all mods)

- 2 - 10k
- 1 - 10n greencap
- 1 - 100n greencap
- 2 - 1N4148 diodes
- 1 - 3v9 Zener diode
- 1 - DPDT switch
- 1 - 10cm tinned copper wire
- 1 - 10cm hook-up wire

which half of the EPROM you wish to read and the read/program switch is used to select the type of EPROM you wish to program.

The next mod is a little more involved but is an important one if you wish to re-program some of the EPROMs supplied by TE.

The programming requirements of some types of more modern (but now obsolete) EPROMs are not compatible with the current set-up of the EPROM programmer. This mod allows the EPROM programmer to be used with a wider variety of EPROMs. The mod does this by switching the programming voltage from 25v to 21v and reduces the programming pulse from 50mS to 10mS.

The parts required for this mod are: one DPDT switch, one 10n greencap, one 100n greencap, a 3v9 zener diode


cont. P 45

...from P. 32.

and some hook-up wire. To start, mount the switch on the bottom of the PCB by drilling two holes and wrapping tinned copper wire around the switch (see photo). Next cut the track between the output of the 24v regulator and the transistor switching block. The bottom middle terminal of the switch is connected to the transistor side of the cut. Connect the bottom right-hand side terminal to the regulator output and also solder the cathode end of the zener to this junction. The anode end of the zener is soldered to the bottom left-hand side of the switch. The zener, which is connected between the regulator and the high voltage switching section, drops the programming voltage by about 4v.

This completes the voltage switching section. Below is the programming pulse length mod.

 The photograph on the right shows how the parts on our prototype are mounted. The description of the parts placement in the text, corresponds to this photo.



Remove the 100nF greencap on the extreme left-hand side of the board (top view). Solder one end of the new 100nF to the top right-hand side of the switch. Take the 10nF cap and solder one side of this to the top left-hand side of the switch. The other ends of the caps are soldered together and a jumper is also soldered onto this junction. The jumper is then soldered to pin 3 of the 4011. Another jumper is soldered between pin 6 of the 4011 and the top middle terminal of the switch.

When the switch is in the right-hand position (top view), the EPROM programmer is set up for the modern 21v/10mS EPROMs.

One of these types of EPROM is being supplied by TE. It can be identified by the following markings:

TMS
2732A-25JL
LHE XXXX (DATE CODE)

To increase the reliability of the programmer, another mod is suggested. Follow the track from the ROM select line to where it joins the 10nF cap.

Cut both the tracks that join to the cap at this junction. Then run a link from the ROM select input pad to pin 8 of the 4011. Now run a jumper from the wait pin to the now isolated end of the greencap.

This mod slightly delays the programming pulse to the EPROM by triggering it from the wait line, not the input ROM select line.

The software for burning EPROMs provided in issue 13 is only very basic. There is one VERY IMPORTANT ADDITION to make to the issue 13 software. After you have loaded BC, DE and HL, as described in issue 13, add the following:

XOR A (AF)
LD I,A (ED 47)
JUMP 0700 (C3 00 07)

These instructions stop the noise on the expansion port which is a result of several TEC design oversights.

The following software is designed to be burnt into either a MON-1 or MON-2 EPROM at 0700.

The software is JUMP TO with the "from address" in HL, the "to address" in DE and the number of bytes in BC.

Before it attempts to burn into the EPROM, it checks that the area to be programmed contains only FF's. If not, the routine displays an "F", for FULL in the data display and halts. You may continue on and burn the EPROM by hitting "GO". Each location is checked after it is burnt and if not correct, it is reprogrammed several more times before being aborted. The routine then displays "E" for ERROR.

You must do the "read 2732" mod to program 2732 EPROMS.

An added feature to this software is that it flashes the address being programmed on the TEC display.

EPROM BURNING SOFTWARE

```

0700 AF XOR A
0701 ED 47 LD I,A
0703 CD 90 07 CALL 0790
0706 7E LD A,(HL)
0707 12 LD (DE),A
0708 D5 PUSH DE
0709 D9 EXX
070A D1 POP DE
070B CB 9A RES 3,D
070D D5 PUSH DE
070E 01 F0 0F LD BC,0FF0
0711 C5 PUSH BC
0712 CD 5A 07 CALL 075A
0715 7B LD A,E
0716 CD 5A 07 CALL 075A
0719 7A LD A,D
071A CD 5A 07 CALL 075A
071D C1 POP BC
071E 01 10 00 LD BC,0010
0721 C5 PUSH BC
0722 CD 6E 07 CALL 076E
0725 C1 POP BC
0726 0B DEC BC
0727 78 LD A,B
0728 B1 OR C
0729 20 F6 JR NZ,0721
072B D1 POP DE
072C 1A LD A,(DE)
072D D9 EXX
072E BE CP (HL)
072F 20 08 JR NZ,0739
0731 23 INC HL
0732 13 INC DE
0733 0B DEC BC
0734 78 LD A,B
0735 B1 OR C
0736 20 CE JR NZ,0706
0738 C7 RST 00
0739 C5 PUSH BC
073A 01 05 00 LD BC,0005
073D CB DA SET 3,D
073F 7E LD A,(HL)
0740 12 LD (DE),A
0741 10 FE DJNZ,0741
0743 CB 9A RES 3,D
0745 1A LD A,(DE)
0746 BE CP (HL)
0707 20 03 JR NZ,074C
0749 C1 POP BC
074A 18 E5 JR 0731
074C 0D DEC C
074D 20 EE JR NZ,073D
074F C1 POP BC
0750 3E C7 LD A,C7
0752 D3 02 OUT (02),A
0754 3E 01 LD A,01
0756 D3 01 OUT (01),A
0758 76 HALT
0759 C7 RST 00
075A F5 PUSH AF
075B CD 63 07 CALL 0763
075E F1 POP AF
075F 0F RRCA

```

```

0760 0F RRCA
0761 0F RRCA
0762 0F RRCA
0763 E6 0F AND 0F
0765 21 B0 07 LD HL,07B0
0768 85 ADD A,L
0769 6F LD L,A
076A 7E LD A,(HL)
076B 02 LD (BC),A
076C 03 INC BC
076D C9 RET
076E 21 F0 0F LD HL,0FF0
0771 06 06 LD B,06
0773 0E 01 LD C,01
0775 7E LD A,(HL)
0776 D3 02 OUT (02),A
0778 79 LD A,C
0779 D3 01 OUT (01),A
077B 0E 40 LD C,40
077D 0D DEC C
077E 20 FD JR NZ,077D
0780 07 RLCA
0781 4F LD C,A
0782 AF XOR A
0783 D3 01 OUT (01),A
0785 23 INC HL
0786 10 ED DJNZ,0775
0788 C9 RET
0789 FF RST 38
078A FF RST 38
078B FF RST 38
078C FF RST 38
078D FF RST 38
078E FF RST 38
078F FF RST 38
0790 D5 PUSH DE
0791 C5 PUSH BC
0792 CB 9A RES 3,D
0794 1A LD A,(DE)
0795 FE FF CP FF
0797 20 09 JR NZ,07A2
0799 13 INC DE
079A 0B DEC BC
079B 78 LD A,B
079C B1 OR C
079D 20 F5 JR NZ,0794
079F C1 POP BC
07A0 D1 POP DE
07A1 C9 RET
07A2 3E 47 LD A,47
07A4 D3 02 OUT (02),A
07A6 3E 01 LD A,01
07A8 D3 01 OUT (01),A
07AA 76 HALT
07AB 18 F2 JR 079F

```

```

07B0 EB 28 CD AD 2E A7 E7 29
EF 2F 6F E6 C3 EC C7 47

```

PRINT-2 AND PRINT-3 SOFTWARE

With the changes to the keyboard handler routines in both MON-2 and JMON, an up-dated printer ROM has been produced.

The new software is burnt into the same ROM at higher locations. When MON-2 was released, an up-dated ROM called print-2 was included in the printer interface kits. This gave you the same routines with an altered keyboard section. It was also a little more fancy as it showed the start address on the LED display as you typed it in. Unfortunately, Print-2 did not include a "dump string at 0900" routine to replace the dump from 0800 which is now unusable as MON-2 uses 0800 for its variable storage.

With the advent of JMON, the same arrangement has been used. The JMON printer routines are located higher again, so in the one ROM you have the printer software for all three MONitors. The list routine for JMON is an improvement on both earlier software packages, as JMON's routine uses the perimeter handler to allow you to enter both a START and END address. Print-3 includes a "dump from 0900" routine which can be used with MON-2.

The ROM with the JMON routines in it is called PRINT-3 and is supplied with the printer interface as standard.

JMON's hex dump routine is at 1A20, the typing routine at 1AA0 and the "dump string at 0900" routine is at 1AC0.

Below is a dump of PRINT-3. Burn the additional section(s) in PRINT-1/2 ROM.

The graphic demonstration routines in PRINT-1 will work with all MONitors.

```

1800 3E 0D D3 06 3E 0A D3 06
76 ED 57 17 17 17 17 57
1810 CD 5D 18 76 ED 57 82 57
CD 61 18 76 ED 57 17 17
1820 17 17 5F CD 5D 18 76 ED
57 83 5F CD 61 18 C3 49
1830 18 3E 0D D3 06 3E 0A D3
06 7A CD 5D 18 7A CD 61
1840 18 7B CD 5D 18 7B CD 61
18 06 08 3E 20 D3 06 1A
1850 CD 5D 18 1A CD 61 18 13
10 F1 C3 31 18 1F 1F 1F
1860 1F 21 6C 18 E6 0F 85 6F
7E D3 06 C9 30 31 32 33
1870 34 35 36 37 38 39 41 42
43 44 45 46 FF FF FF FF
1880 21 00 08 7E FE FF 20 05
3E 11 D3 06 C7 D3 06 23
1890 18 F1 FF FF FF FF FF FF
FF FF FF FF FF FF FF FF
18A0 21 C3 18 7E FE FF 28 05
D3 06 23 18 F6 06 0A 21
18B0 CF 18 7E FE FF 28 05 D3
06 23 18 F6 10 F1 3E 11
18C0 D3 06 C7 0D 0A 0A 0A 0A
0A 0A 12 43 30 0D FF 49
18D0 2C 44 33 32 30 2C 30 0D
4D 31 32 30 2C 30 0D 44
18E0 38 30 2C 2D 31 36 30 0D
4D 32 32 30 2C 2D 38 30
18F0 0D 44 31 36 30 2C 2D 38
30 2C 31 34 30 2C 2D 31

```

```

1900 36 30 2C 32 30 30 2C 2D
31 36 30 0D 4D 31 35 30
1910 2C 2D 31 32 30 0D 44 32
30 30 2C 2D 31 32 30 0D
1920 4D 33 32 30 2C 2D 38 30
0D 44 32 36 30 2C 2D 38
1930 30 2C 32 34 30 2C 2D 31
36 30 2C 33 30 30 2C 2D
1940 31 36 30 0D 4D 33 36 30
2C 2D 31 32 30 0D 44 34
1950 30 30 2C 2D 31 32 30 0D
4D 34 36 30 2C 2D 38 30
1960 0D 44 34 34 30 2C 2D 31
36 30 0D 4D 32 2C 2D 32
1970 0D 43 33 0D FF FF FF FF
FF FF FF FF FF FF FF FF
1980 76 ED 57 E6 0F 17 17 17
17 57 76 ED 57 E6 0F 82
1990 D3 06 18 EC FF FF FF FF
FF FF FF FF FF FF FF FF

```

The next block is the PRINT-2 additions:

```

19A0 76 3A E0 08 E6 0F 17 17
17 17 57 76 3A E0 08 E6
19B0 0F 82 D3 06 18 EA FF FF
FF FF FF FF FF FF FF FF
19C0 3E 0D D3 06 3E 0A D3 06
3E 29 21 D8 08 06 06 77
19D0 23 10 FC CD 00 1A 32 D8
08 CD 00 1A 32 D9 08 CD
19E0 00 1A 32 DA 08 CD 00 1A
32 DB 08 CD D8 01 CD 89
19F0 02 50 59 C3 31 18 FF FF
FF FF FF FF FF FF FF FF
1A00 3E FF 32 E0 08 CD A0 02
3A E0 08 FE FF 28 F6 E6
1A10 0F C6 FF CD 70 01 D6 01
C9 FF FF FF FF FF FF FF FF

```

Below is PRINT-3 additions:

```

1A20 21 34 1A 11 80 08 01 0A
00 ED B0 21 00 00 22 9C
1A30 08 C3 44 00 00 00 3E 1A
99 08 00 01 50 1A 04 A7
1A40 04 C7 04 EB FF FF FF FF
FF FF FF FF FF FF FF FF
1A50 3E 0D D3 06 2A 98 08 7C
CD 82 1A 7D CD 82 1A 06
1A60 08 C5 3E 20 D3 06 7E CD
82 1A 23 C1 10 F3 3E 0D
1A70 D3 06 3E 0A D3 06 ED 5B
9A 08 E5 B7 ED 52 E1 38
1A80 D6 C9 F5 0F FF 0F 0F CD
8B 1A F1 E6 0F C6 90 27
1A90 CE 40 27 D3 06 C9 FF FF
FF FF FF FF FF FF FF FF
1AA0 CF E6 0F 07 07 07 07 57
CF E6 0F 82 D3 06 18 F0
1AB0 D3 06 18 EC FF FF FF FF
FF FF FF FF FF FF FF FF
1AC0 21 00 09 7E FE FF 20 05
3E 11 D3 06 C7 D3 06 23
1AD0 18 F1 FF FF FF FF FF FF
FF FF FF FF FF FF FF FF

```

TE

