# MIM-16502 USER NOTES

SEPTEMBER 1976

REPRINT

VOLUME 1 ISSUE 1

PAGE 1

First of all, I would like to thank you for your response to the newsletter. There are about 200 of us now and our number continues to grow daily. The creativity in this group has not ceased to amaze me since the first letters started rolling in. The most noteworthy has been in the area of games, and demonstration programs in general without the use of any additional I/O devices.

Instead of standing there with a blank look on your face when your family and/or friends say "That's nice, but what can it do?", you can load up with a neat demo program and dazzle them to no end. Jim Butterfields' Real-time Lunar Lander should go a long way toward this end (and you don't need a terminal).

It would be beneficial to publish a list of all the members in the next issue so local people can communicate directly. If you don't want yourname & address published for any reason, please drop me a note very soon and I'll keep your name off the list.

Several Amateur Radio operators have suggested starting a Kim Users Net to meet on the ham bands. This is an excellent idea - as there are quite a few Hams in the group (myself included). Would anyone like to coordinate activities in this area?

Any of you wishing to start local groups of Kim-1/6502 users should let me know - I'll pass it on. Here's one:

Buffalo New York - Kim-1 group no forming. Call (716) 634-6844 for information.

 ${\rm H}_{\rm a}{\rm ve}$  you been waiting for an assembler, or perhaps Tiny Basic? Well wait no longer.

Kim-1 Tiny Basic for \$5.00 is now being offered by: Itty Bitty Computers F.O. Box 23189
San Jose, Calif. 95153

and

Included in the deal, is a 26 page user manual, a hexidecimal paper in the MOS Technology loader format. A hex listing will be substituted for the tape for those who don't have paper tape equipment. They also have versions of TB for 6800 systems, Jolt, Apple, and Homebrew 6502 systems.

A note from: Bob Grater, Microfit Systems, 1595-21 Laurelwood Rd.
Santa Clara, Calif. 95050 Phone (408) 246-481 Phone (408) 246-4813

Just a short one with some infor for the next newsletter. Steve Pittman here in San Jose has just finished a 2K "Tiny Basic" for KIM, and we'll have it on the market probably in the next couple of weeks (will give you more info as things jell). It should run about \$7.00 on paper tape ppd. and will be sold thru the "Byte Shop" in Santa Clara.

What we would like to do is get it on cassettes and offer it in that form for the basic price plus the cost of a cassette. I don't have any additional RAM tacked onto KIM yet and would like to find someone in the area that has at least 2K of memory so we can transfer the BASIC on to a master cassette. A free copy on either paper tape or cassette will go to anyone who will help us on this and they may contact me at the above address & number.

Will let you know when everything is tied-down as to form, price, ect.

I completed my SAB-1 interface adaptor board and we are having the boards made now. The complete kit should be available by 1 Oct. from the "Byte Shop #2" in Santa Clara. Don't have price yet and am researching that now (estimate around \$25). The adaptor board will interface KIM's TTY port to any parallel TV Typewriter and Keyboard, with selectable baud rates from 100 to 1760. It is aimed at an easy jumper selectable interface with the "Byte Shop's" TVT kit that runs \$120 for the kit and \$35 for the bare board. his should give a good alternative to anyone who doesn't want to go out and spend 900 clams for a TTY! (and they are noisey).

Still don't have Tom Pittman's 2K TINY BASIC in hand, but it should be here soon and will let you know on that also.

Just to give you an update on the latest happenings "out this Way".

Bob Grater

Editors Note:

I've heard mention of a method for improving KIM TTY operation by raising the voltage on the TTY resistive divider network R48,R49. Can anyone supply the data on this modification?

OUR FILE OF ARTICLES FOR UPCOMING ISSUES IS RUNNING LOW!!! PLEASE SEND MORE MATERIAL!!! ANY SUBJECT THAT INTERESTS YOU WILL INTEREST OTHER MEMBERS!!!!

To prevent duplication of efforts in the areas of software and hardware design projects for the Kim or 6502 based machine, the <u>User Notes</u> will publish your name together with others who are working on similar projects.

Need some ideas?

Here's a note from Jim Butterfield, 14 Brooklyn Avenue, Toronto M4M 2X5 Canada.

Thought I'd produce something to fire up the imaginations of those KIMmers who'd like to start a project, but just can't think of a good one. The dozen I outline are just a sample... there are lots more, like GOLF, FACTORS OF AN INTEGER, MAD CHEMIST, etc. etc... this list could go on endlessly; many are games, some are physically useful. I've stayed out of diagnostics (SCAN MEMORY, RELOCATE PROGRAM, etc.), mostly because they could change in character for those lucky enough to have printer/keyboard. And I've tried to make the descriptions fuzzy enough so that the programmer can create a system which is still truly his own concept. Last thought: I want to deliver the idea that you can have lots of fun without a terminal.

Has anyone thought of building a light pen for use with the KIM-1 display?

The following programs are <u>concepts</u>. None of them have been written (by me, at any rate). So if you want to take them on as a project, you'll be creating a new KIM capability. (Don't forget to send 'em to USER NOTES when they're ready; or, if you get stuck, call for help in USER NOTES!).

They can also be used as 'kicking off' points for other concepts; after all, ideas often generate new ideas.

Some projects are tougher than others. You may find one that's exactly your speed.

1. SUPER-CLOCK.

The six digits of the KIM-1 display are ideal for showing time in hours, minutes, and seconds. With the speed of the 6502, your main job will be killing time (no pun intended) until the next second needs to be added.

A simple wait loop will do the job for a basic clock. Each time you call the display (using SCANDS) you'll use up a bit over 3 milliseconds. (Has anyone worked out the exact timing of this subroutine?) So calling the display two or three hundred times before adding to the seconds should get you into the right ball park.

A more advanced approach is to use the KIM-1 timer. This will free you from having to count your loops and instructions so exactly, and you'll be able to add extra goodies to the clock with more freedom.

How about these for super-clock options? (a) 12-hour or 24-hour timing; (b) a Minute-Minder option with audible alarm; (c) stopwatch capability; (d) alarm clock with audible alarm; (e) Westminster chimes or Cuckoo selectable by pushbutton; (f) a chess clock - check with a chess maniac friend for the rules on this one. There are lots more - use your imagination.

# 2. PONY RACE.

Three horses race across the KIM-1 display. They are represented by dashes in the top, middle, and bottom positions respectively. The race in run in, say, four laps; as the first horse moves off the display to the right, the display "hops" over to the next lap (you won't see the following horses until they reach this area). On the final lap, the finish line is visible as a vertical line. When the first horse reaches it, the display freezes, so that bets can be paid off without dispute. Sample display:

• \_ .

You'll need a random number generator, of course, so the ponies will travel at varing speeds and the winner will be unpredictable. Random number generators are a whole study in themselves, of course. You might like to wright your own; or the following one, which requires six data locations (from RND to RND+5):

CLD
SEC
LDA RND+1
ADC RND+4
ADC RND+5
STA RND
LDX #\$04
LOOP LDA RND,X
STA RND +1,X
DEX
BPL LOOP

The random number (from 0 to 255) will be available in either the accumulator or location RND. Each time you execute the above program, a new random number will be generated.

Be sure to slow the action down so that the horses can be "seen" to move.

# 3. DECIMAL-HEXIDECIMAL CONVERSION.

This could be handy to have while you're writing programs! The first four digits of the display might represent a decimal number, while the last two digits its hexadecimal equivalent.

You should be able to enter either decimal or hex, and get the equivalent instantly. (How about signed decimal?)

# 4. LE MANS.

You've got four-on-th-floor and lots of horsepower. Buttons A to D put you into the various gears (A is low, D is high, and maybe E is neutral).

Your gas pedal is the numbered keys: 9 is maximum power. Choose your gears carefully: too high a gear and you'll stall, except in low gear; too low a gear and you'll lose acceleration as your speed increases. To complicate the situation, you'll blow the motor if your RIM exceed a given limit.

This one should come with sound; the noise of the "motor" is vital to the realism of the game.

When no key is being pressed, the motor is "idling" at minimum power. When you're in gear, the motor RPM and the vehicle speed are locked together in the proper ratio for that gear. Each gas pedal key corresponds to a certain motor RPM, but you won't reach that RPM immediately; your speed will creep up (or down) depending on what gear is engaged.

There are lots of different ways you can set up the display. A digital speedometer is the most obvious. As an alternative, how about "telephone poles" (vertical lines on the display) which move from the center of the display to the outside according to your speed?

#### 5. COSMIC RAY DETECTOR.

A great "do nothing" program. It doesn't really detect cosmic rays, but the effect is nice. Little "blips" dash erratically across the display: up and down, left to right, etc. Many of them have an audio output associated with them (bleep! plunk!)

You can use a random number generator, or simply scan memory for your data (which will be random enough).

If you want to wire out to a temperature/skin resistance detector, you could cause the display rate to change if someone touches the sensor. Might make a great "sex appeal" meter.

# 6. CRAPS (dice game).

Using the random number generator, roll a pair of dice. Seven and eleven win; two, three, or twelve lose; any other number is a "point" and requires extra rolls.

Each roll may be initiated by pushing a button; or the machine may keep rolling until it wins or loses. The player could "bet" certain amounts before any play; and the computer would keep a tally on how he's done so far.

# 7. AUNTIE GRISELDA'S FORTUNE TELLING MACHINE.

Think of a question that can be answered Yes or No. Push the button - any button - and Auntie Griselda will answer.

She might just say YES of NO - but you could also insert any other messages that might fit on the KIM-1 display, such as:

> dunno huh? BUGoff OY

or even the FRENCH OUI or NON.

PAGE 5

Since only one random number is needed each time the button is pushed, you might like to try a true "randomizing" program. Keep incrementing your random value with an INC command until the button is pushed. The result will be truly random, since there's no predicting when the questioner will hit it.

#### 8. SIX-DIGIT CALCULATOR.

Since you can't light the decimal point on the KIM-1 display, you can't do fractions; but you can add and subtract, and even multiply and divide with a little effort.

Decimal arithmetic seems easiest for addition or subtraction, but you'll probably find that you'll be better off doing everything in binary, and then converting for display purposes.

"A" seems to be a good key for Add, with B for Subtract, C for Multiply, and D for divide. E might be good for "Divide and show the <u>remainder</u>", which turns out to be very handy for fixed-point work. And you should have lots of Store (DA) and Recall (AD) capability.

Of course, you can't easily compete with a pocket calculator. But you can sharpen up your arithmetic ability on the KIM, and at least show visitors that the capability is there.

## 9. NIM.

The game of NIM is pretty well documented, in several texts, but here are the brief rules: you have three piles of objects. The number of objects in each pile is a two-digit number, shown on the display. You play against the computer in the following manner: you may take from any pile, 1 to 9 objects, up to the maximum in that pile. Then the computer plays the same way. Objective: the player who picks up the last remaining objects wins.

If you know the theory, you can program the computer to play a perfect game (providing the deck isn't stacked against it).

The player's interface must be two-stop. First, he must say which pile he wants to draw from; then, how many he wants to take. He must be prevented from taking more units from a pile than exist on the pile; or from drawing from an empty pile.

The game should be set up using random numbers, of course.

How about making the computer less-than-perfect... maybe one out of every then moves or so (randomly) it will make a mistake? How about setting the computer's I before playing?

## 10. TIC-TAC-TOE.

Most people don't give this game enough credit. It has some interesting (but not terribly deep) strategies, particularly if you vary the opening move.

The board positions are represented by "segments" on the display. Your moves are permanently illuminated; the computer's moves flash on and off.

A simple game, where the computer always takes the first move and always plays a relatively fixed strategy, isn't hard to program - once you have solved the logistics of running the display and keeping trach of the moves (which is a fair sized job).

But if you open up the game - allowing the computer to select randomly among several preferred moves - you can be into quite a project. Might lend itself quite well to a team or class project (arranging to split up a job into several tasks is a whole art in itself).

Don't forget that you can also set the computers IQ before a series of games. Or try this: it gets smarter every time it loses, and dumber every time it wins. So eventually it will always be evenly matched against every opponent!

## 11. RHYTHM BOX.

This is the type of device that comes on electronic organs to add drums, etc. to the music. It's valuable for professional musicians, but can also come in handy for kazoo bands, or even people who just like to hum along.

First, you have to generate the "sounds". You should have five instruments - four are basically different frequencies:

Bass drum - lowest frequency
Conga - about 50% faster than the Bass
Wood block-much faster (several times) the Conga
Clave - about 50% faster than the Wood block

And finally the Snare drum - this, instead of being a frequency, is "white noise" - a random series of bits.

As a first step, you can set these up to sound when an appropriately numbered key is pressed - 1 for the Bass, 2 for the Conga, etc. (Hardware hackers can build the oscillators externally, if they wish - programming pundits will of course generate the sounds directly in software).

Now comes the slick part. You can set up a program to output many rhythms directly - waltz, march, bossa nova, etc. Be sure to make it variable in speed. Another hint: many professional rhythm boxes have a foot pedal to allow the artist to start and stop it at will.

# 12. DARKROOM TIMER.

Photography hobbyists will go for this one. More than just a minute minder. This device could: measure the light from the enlarger, and set the print exposure time automatically; control both safelight and enlarger lamp; measure negative contrast and suggest the grade of paper (or variable contrast filter); or even, if desired, compensate for developer temperature and/or exhaustion!

The red LED display doesn't seem to affect most black-and-white papers. It's almost as if it were designed for the job!

Con't.

You'll need relays or SCR circuits, of course, to control power to safelights and enlarger. An audible output might be useful if you want to use KIM to signal developing times (and if you want to control your exposure manually).

Question: Has anybody made an AC controller yet by modifying one of those inexpensive Triac lamp dimmers? I would think an optical coupler would replace the variable resistor and give highly desirable isolation.

Regards.

Jim Butterfield

Some more project ideas from the Editor:

An automated I.C. tester - hardware & software project - should test any standard 7400 series chip (such as 7400, 7404, 7474, 7475, 7490, 7493 etc.) - 1 or 2 I/O ports would be necessary along with support logic. Each type of chip to be tested would require a special software routine. The program would go through all possible signal combinations and indicate go/no go on the KIM display. Open collector logic would require special interface considerations. A low insertion socket would be useful.

Digital Voltmeter, frequency meter, thermometer, capacity meter etc etc. (using the KIM-1 display)

By utilizing the correct input conditioning logic for the desired function any of these possibilities can be realized. For the DVM, see the low cost A/D in the last issue which utilizes a single LM311. A schmitt trigger input could be set up to increment some internal counters for a DFM. The thermometer and capacity meter would be additions to the basic DVM and DFM functions. With all the neat transducer chips coming out, all kinds of possibilities are open.

A programmable function generator - by hooking a D/A chip and a current/ voltage converter on an output port you could set programs up to give you - positive ramp, negative ramp, triangular, staircase waveforms or any other complex waveforms you desire.

**'** 

Along these lines - from Bob McCulla, 20333-15 N.E. #28, Seattle, Wash.98155

One of our people has discovered a little jewel from Motorola - The MC3408 8 bit DAC at \$4.00 a shot. He lost little time in connecting it to the applications connector of his KIM board and is using it to control the sweep input of his H.P. function generator. He says that by offsetting the op amp at the output of the DAC, he can get both + and (-) voltage swings out of the unit - works great.

Another use of the applications connector could be to control the input pins of the MC14410 touch tone encoder. I use one of these encoders to dial numbers and control one of our local Amateur Radio 144MH FM Repeaters and can see a good use of the KIM system here for telephone number storage and auto repeater control from my car. Along these lines, I understand that some Amateur Radio people in our area are using their systems for contact logging, Morse Code generations and the control of frequency synthesizers and frequency readout units.

A vary interesting article appeared in the EDN Magazine for May 5, 1976, "A/D Conversion Systems: let your uP do the Working". It was written by an Engineer from Motorola and even though it was written about the 6800 uP, the information is directly useable for 6502 systems.

Sincerely, Bob McCulla

Further hints on the KIM cassette interface from John P. Oliver, Asst. Professor of Astronomy, University of Florida, Gainesville, Florida 32611.

......

Be certain to turn off the interval timer interrupt (READ or WRITE to 1706) before using the audio tape dump routine. Otherwise disaster results - that is, you get unreadable tapes. (This will only be necessary if you have run a program that uses the interval timer.)

For those who wonder what Baud rates are possible with the KIM teletype interface, we have one of ours hooked (through an RS232 converter similar to the one in KUN #1) to a Hazeltine CRT terminal. We can work reliable to 1200 Baud and most of the time we can work at 9600 Baud. At 9600 Baud it sometimes takes several RST, RUBOUT cycles before KIM gets the timing right but the results are well worth

.....

Sincerely, John P. Oliver

From Jim Butterfield
LIGHTING THE KIM-1 DISPLAY
A. SIX-DIGIT HEXADECIMAL.

The easiest way to display six digits of data is to use the KIM-1 Monitor subroutine SCAND.

Calling JSR SCAND (20 19 1F) will cause the first four digits to show the address stored in POINTH (COFA and COFB), while the last two digits of the display show the contents of that address.

If you look at the first three lines of subroutine SCAND (lines 1057 to 1059 on page 25 of the listing), you'll see how the program "digs out" the contents of the address given by POINTL/POINTH and stores it in location INH (OOF9). It's neat programming, and worth studying if you're not completely familiar with the 6502's indirect addressing operation.

Thus, if you skip these three lines, and call JSR SCANDS (20 IF 1F) you will be displaying, in hexidecimal, the contents of three locations: POINTH, POINTL, and INH. This, of course, takes six digits.

Con't.

## LIGHTING THE KIM-1 DISPLAY - Con't.

To recap: SCAND will display four digits of address and two digits on contents. SCANDS will display six digits of data.

Important: in both cases, the display will be illuminated for only a few milliseconds. You must call the subroutine repeatedly in order to obtain a steady display.

- B. DRIVING THE BITS OF THE DISPLAY DIRECTLY.
- 1. Store the value \$7F into PADD (1741). This sets the directional registers.
- 2. To select each digit of the display, you will want to store the following values in location SBD (1742):

Digit 1: \$09 Digit 2: \$0B

Digit 3: \$0D Digit 4: \$OF

Digit 5: \$11

Digit 6: \$13

Note that this can easily be done in a loop, adding two to the value as you move to the next digit.

3. Now that you have selected a particular digit, light the segments you want by storing a "segment control" byte into location SAD (1740). The segments will be lit by setting the appropriate bit to 1 in SAD according to the following table:

Bit:	7	6	5	4	3	2	1	0
Segment:	••	Center	Upper Left	Lower Left	Bottom	Lower Right	Upper Right	Тор

For example, to generate a small letter "t", we would store \$78 (center, upper left, lower left, bottom) into SAD.

4. Now that you have picked a digit and lit the appropriate segments, wait a while. Sit in a delay loop for about 1/2 milisecond before moving on to the next digit.

# THE KIM-1 ALPHABET.

Some letter, like M and W, just won't go onto a 7-segment display. Some, like E, are only possible in capitals; others, like T, can only be done in lower case. So here's an alphabet of possibles:

A - \$F7	H - \$F6	U - \$BE h - \$F4	r - \$D0	4 - \$E6
B - \$FF	I - \$86	Y - \$EE i - \$84	t - \$F8	5 - \$ED
C - \$B9	J - \$9E	b - \$FC j - \$9E	u - \$90	6 \$FD
D - \$BF	L - \$B8	c - \$D8 1 - \$86	y - \$EE	7 - \$87
E - \$F9	O - \$BF	d - \$DE n - \$D4	1 - \$86	8 - \$FF
F - \$F1	P - \$F3	f - \$F1 0 - 1DC	2 - \$DB	9 - \$EF
G - \$BD	S - \$ED	g - \$EF p - \$F3	3 - \$CF	0 - \$BF
		g - \$EF p - \$F3 PAGE 10	3 - \$CF	,

From Stan Ockers, RR#4, Box 209, Lockport, Illinois 60441 Alphanumerics on the KIM Display.

For many, one of the first peripherals they consider adding to their KIM-l is some sort of alpha-numeric device, a mechanical printer or keyboard and video display unit for example. Unfortunately, such devices involve considerable expense and make your KIM slightly less than portable to say the least. The KIM already has a built in display. Isn't there some way to make use of this for alphanumeric output? Is it worth it? Well, with a few concessions for a slightly strange character set, it is possible as I will try to show. Why not try it on your KIM and see if you think it offers any promise. The following program displays six characters, delays for a set time, shifts each character one space to the left and enters new characters from the right giving a scanning billboard effect.

#### Basic Display Routine.

The core of the alphanumeric method is contained in the basic display routine starting at \$\pi269\$. The subroutine follows the same general pattern of Scand, (page 25 of the KIM listing), as a comparison of the two will show. Where Scand jumps to Convd, (1F2F), however this subroutine picks up characters stored in \$\piE8 - \pi\pi\text{DD}\$. Convd uses the table starting at 1FE7 to get bytes representing the characters to be displayed. We must generate our own bytes and store them in \$\phiE8 - \pi\text{DD}\$. This is done according to the diagram in figure 1 where the numbers represent bit locations. The most significant bit (8\$\pi\$) must be equal to one. For example, to generate a "y" the following bit pattern would be required: lll\$\pi\text{ll}\pi\text{ll}\$. The hex byte representing the letter "y" would then be EE. While the whole alphabet can't be generated, with a little imagination a fairly good substitute can be found. Figure 2 lists the set I've been using. If you wish to use the same table Scand uses and put the hex numbers to be displayed in \$\pi\pi\pi\text{E} - \pi\pi\pi\text{DD}\$, just jump in at 1F4A instead of 1F4E (\$\pi277\$). All that is needed now is some way to get our characters into the zero page locations and some way to continually call this routine while we want a display (a delay-display routine).

## Key-Entry Routine.

You may wish to slow down or speed up the display or you may wish to back up to catch something you missed. The key-entry routine allows these functions while the display is operating. Pressing a low numbered key will speed the display up, (shorten delay), while a high value key will slow it down. Zero gives a very long delay (25 sec) and if you press another key after zero you will have to wait for it to time out. Pressing "F" will cause the display to move forward while "B" will make it go backward.

# Delay-Display Routine.

The delay display routine ( $\emptyset$ 228) is set up in tenth of a second multiples. A  $\emptyset$ A in  $\emptyset$ 229 give  $1\emptyset$  tenths or a one second delay. For any other delay you can load X with a multiple of  $\emptyset$ .1 seconds and jump in at  $\emptyset$ 22A. The key-entry routine enters the key value in  $\emptyset$ 029, (unless it is a "F" or "B").

## Scan Routine.

The routine that picks up the characters to be displayed and puts them in  $\beta\beta E8$  -  $\beta\beta ED$  starts at  $\beta 2\beta\beta$ . You must tell the routine where the characters are located, so Y should contain a pointer value high and the accumulator a pointer value low upon entry. You'll notice that there is no way to get out of this routine unless a null character  $(\beta\beta)$  is encountered, (see  $\beta 21\beta$ ).

## Driver.

I've covered the preceding in some detail because you may want to play around with using some of the subroutines individually. All you really need to know about though is the driver and character set. a typical driver to tell where the characters are stored is shown beginning at \$283. It is set up to use page three. It starts at \$300 because you should put a \$60 in \$300 so that if scanning backwards, the message will turn around. Write your own message starting at \$500 using the hex equivalent of characters described in figure 2, (or make up your own), one byte per character. End with a \$60. The program is started at \$283. That's all there is to it but no provision has been made for page crossing so you are limited to 256 characters.

I would like to thank Roy Hinman who showed me how to use the display.

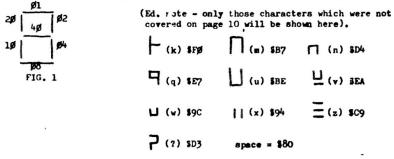


FIG. 2

# \*\*\*\*SCAN ROUTINE\*\*\*\*

Ø2ØØ Ø2Ø2	84 85	DE DD	STY ØØDE STA ØØDD	; Transfer pointer high ; Transfer pointer low
Ø2Ø4	A9	Ø7	LDA #8Ø7	; Initialize to scan forward
Ø2Ø6	85	DF	STA ØØDF	;
<b>ø</b> 2 <b>ø</b> 8	ΑØ	Ø5	LDY #\$Ø5	; Initialize Y
3) Ø2ØA	<b>A2</b>	Ø5	LDX #8Ø5	: Initialize X
Ø2ØC	Bl	DD	LDA ØØDD (Ind),Y	Get character
Ø2ØE	95	E8	STA ØØE8.X	: Store it
Ø21Ø	C9	ØØ	CMP #800	Last character ?
<b>Ø</b> 212	DØ	Ø1	BNE (1)	: If not, continue
_ Ø214	60		RTS	: If sp. exit subroutine
(1) Ø215	88		DEY	set up next character
Ø216	CA		DEX	set up next store location
Ø217	10	F3	BPL(2)	: loop if not 6th character
Ø219	D8	1,5)	cro C	Put in binary mode
Ø21A	18 -		CLC	prepare to add
Ø21B	98		TYA	get character pointer
<b>Ø</b> 21C	65	DF	ADC ØØDF	update for new 6 characters
#21E	85	DC	STA ØØDC	: Save new pointer
Ø2 <b>2</b> Ø	20	28 <b>Ø2</b>	JSR Ø228	Jmp to delay-display

Con't.

```
SCAN ROUTINE CON'T.
                         LDY ØØDC
JMP (3)
                                              ; restore pointer
           A4 DC
   Ø223
           4C ØA Ø2
                                              ; continue rest of message
   Ø225
                                 ....DELAY-DISPLAY ROUTINE....
   ø228
ø22a
                ØA
DB
                          LDX#$ØA
                                              ; set rate
                                              ; put in decrement location ; load timer ( O.1 seconds)
                          STX ØØDB
           A9
8D
(5) Ø22C
                52
                          LDA #$52
                Ø7 17
3E Ø2
Ø7 17
                          STA 1797
                                               ; start timer
   Ø22E
(4) Ø231
           2Ø
2C
                                               ; jmp to key entry subroutine
                          JSR Ø23E
                          BIT 1797
BPL 4
                                               ; timer done?
                                               ; if not, loop
   Ø237
           1Ø
                F8
                          DEC ØØDB
BNE 5
                                               ; decrement timer
           C6
                DB
                                               ; time completed?
   Ø23B
           DØ
                EF
                                               ; go get 6 new characters
   Ø230
            6ø
                          RTS
                                    ****KEY ENTRY ROUTINE****
⑥Ø23E
Ø241
                8C 1E
                          JSR INIT 1
                                               ; set up
           20
20
40
60
20
D0
                          JSR Ø269
                69 Ø2
                                               ; display-entry
                          BNE
                                               ; skip if key depressed
    Ø244
                Ø1
                                               exit subroutine
    Ø246
                          RTS
Ø247
Ø24A
Ø24C
                          JSR #269
BNE (8)
                                               ; display-entry
                69 Ø2
                                               ; key still depressed
                Ø1
                                               ; exit if no
           60
20
09
10
09
09
                          RTS
                                               ; get key value
; valid key?
8 Ø24D
                          JSR GET KEY
                6A 1F
                          JSR GET N
CMP #$15
BPL 6
CMP #$ØF
BNE 9
LDA #3Ø7
BPL 00
    Ø25Ø
                15
                                               ; if not - try again
    Ø252
                E5
    Ø254
                                               forward?
                                               ; if not, continue
                ø7
ø6
    Ø258
           A9
1Ø
C9
DØ
A9
85
                                               ; set forward shift
    Ø25A
                                               ; store it
                          CMP #$ØB
BNE (11)
LDA #$Ø5
@ Ø25C
                                               backwards?
                ØB
                Ø5
Ø5
DF
    Ø25E
                                               ; if not, continue
                                               set backward shift
    Ø26Ø
(10) Ø262
                          STA ØØDF
                                               ; store shift
                                               ; exit
    Ø264
            6ø
                          RTS
(1) Ø265
            8D
                29 Ø2
                          STA Ø229
                                               ; put key entry in timer
    Ø268
            6ø
                          RTS
                                               ; exit
                                  ****BASIC DISPLAY ROUTINE****
            A9
8D
                7F
                          LDA #$7F
    Ø269
                                               ; change seg.
    Ø26B
                41 17
                          STA PADD
                                               ; to output
            AØ
                øø
                           LDY #$00
    Ø26E
                                               ; init recall index
           A2
B9
84
2Ø
C8
                ø9
E8 øø
                           LDX #109
                                               ; init digit number
    Ø27Ø
(12) Ø272
                          LDA ØØE8.Y
STY ØØFC
                                                ; get character
    Ø275
Ø277
Ø27A
                FC
                                                ; save Y
                 4E 1F
                           JSR 1F4E
                                                ; display character
                           TNY
                                                ; set up for next character
                           CMP #106
BCC (12)
            CØ
                 ø6
    Ø27B
                                                ; 6 Char. displayed?
    Ø27D
            90
                 F3
                                                ; if not, get another
    Ø27F
            2ø
                 3D 1F
                           JSR 1F3D
                                                key down?
                                                ; exit
    Ø282
                           RTS
```

# ····DRIVER····

① Ø283 AØ Ø3 LDY #\$Ø3 ; init. point high Ø285 A9 Ø1 LDA #\$Ø1 ; init. point low Ø287 2Ø ØØ Ø2 JSR Ø2ØØ ; write Ø28A 4C 83 Ø2 JMP ① ; repeat

## DIRECTIONS:

1. Put a 00 in 0300

2. Enter your characters 1 byte per character (see char. set)

3. End with a pp

- 4. Program starts at \$283
- A low number pressed speeds u display high number slows it down. A "F"
  makes it go forward, "B" backward. Ø gives a delay of about 25 seconds
  between shifts.

\*\*\*\*\*\*\*\*\*\*\*\*\*\*\*\*\*

MOON LANDER by Jim Butterfield - Fly in real time with fuel constraints; this involves interface to display, keyboard monitor; requires active and real-time user interface.

- . 1. Program starts at location 0000. Press AD 0 0 0 0 00, you will find your-self at 4500 feet and falling. The thrust on your machine is set to low; so you'll pick up speed due to the force of gravity.
- . 2. You can look at your fuel any time by pressing the F button, your fuel (initially 800 pounds) will be shown in the first four digits of the KIM display.
- 3. You can look at your altitude any time by pressing the A button. Your initial altitude is 4500 feet, and is shown in the first four digits of the KIM display.
- 4. The last two digits of the KIM display always show your rate of descent or ascent.
- 5. Set your thrust by pressing buttons 1 through 9. (Warning: button 0 turns your motor off, and it will not reignite! Be prepared for a very hard landing if you press this one!) A thrust of 1, minimum burns very little fuel; but gravity will be pulling your craft down faster and faster. A thrust of 9, maximum, overcomes gravity and reduces your rate of descent very sharply. A thrust of 5 exactly counterbalances gravity; you will continue to descend (or ascend) at a constant rate.

If you run out of fuel, your thrust controls will become inoperative.

- 6. A safe landing is considered to be one where you land at a descent rate of 5 or less. After you land, your thrust controls will be inoperative, since the motor in automatically turned off; but you can still press F to look at your fuel.
  - 7. Suggestions for a safe flight:
    - Conserve fuel at the beginning by pressing 1. You will begin to pick up speed downwards.
    - When your rate of descent gets up to the 90's, you're falling fast enough. Fress 5 to steady the rate.
    - When your altitude reaches about 1500 feet, you'll need to slow down.
       Press 9 and slow down fast.

PAGE 14

# MOON LANDER - Con't.

4. When your rate of descent has dropped to 15 to 20, steady the craft by pressing 5 or 6. Now you're on your own.

```
0000 A2 OC
0002 B5 B8
0004 95 E2
                              LDX #SOC
                  GO
                              LDA INIT, X
                                                    'set up initial flite.
                  LP1
                              STA ALT, X
0006 CA
0007 10 F9
                              DEX
                              BPL LP1
0009 A2 05
000B A0 01
                              LDX #$05
LDY #$01
                                                   acceleration/velocity update
                  CALO
                  RECAL
000D F8
                              SED
OOOE 18
                              CLC
                              LDA ALT, X
000F B5 E2
0011 75 E4
                  DIGIT
                                                   add each digit
                              ADC ALT+2,X
0013 95 E2
0015 CA
0016 88
                              STA ALT,X
                                                   next digit
                              DEX
                              DEY
                              BPL DIGIT
0017 10 F6
                              LDA ALT+3.X
0019 B5 E5
                              BPL INCR
001B 10 02
001D A9 99
001F 75 E2
                              LDA #$99
                  INCR
                              ADC ALT.X
0021 95 E2
0023 CA
                              STA ALT,X
                              DEX
                              BPL RECAL
0024 10 E5
0026 A5 E2
0028 10 0B :
                              LDA ALT
BPL UP
                                                   still flying?
                              IDA #$00
IDA #$02
002A A9 00
002C A2 02
002E 95 E2
                                                   NOPE, turn off
                              STA ALT,X
STA TH2,X
                  DD
0036 95 E8
0032 CA
0033 10 F9
0035 38
0036 A5 ED
                              DEX
                              BPL DD
                              SEC
                                                   update fuel
                              LDA FUEL+2
0038 E5 EA
                              SBC THRUST
003A 85 ED
                              STA FUEL+2
 003C A2 01
                              LDX #$O1
003E B5 EB
                  LP2
                              LDA FUEL,X
0040 E9 00
0042 95 EB
0044 CA
0045 10 F7
0047 BO 00
                              SBC #$00
                              STA FUEL, X
                              DEX
                              BPL LP2
                              BCS TANK
                                                   Any fuel left?
0049 A9 00
004B A2 03
                              LDA #$00
                              LDX #803
                                                   nope, turn off engine
 004D 95 EA
                              STA THRUST, X
OO4F CA
                              DEX
 0050 10 FB
                              BPL LP3
                   show altitude or fuel according to flag
                              JSR THRSET
 0052 20 AA 00
0055 A5 EE
0057 DO OA
                  TANK
                              LDA MODE
                              BNE SHOFL
0059 A5 E2
                              LDA ALT
```

```
MOON LANDER - Con't.
   005B A6 E3
005D F0 08
005F D0 06
                                LDX ALT+1
                                BEQ ST
BNE ST
   0061 FO A6
                    LINK
                                BEQ CALC
   0063 A5 EB
0065 A6 EC
0067 85 FB
0069 86 FA
                    SHOFL
                                LDA FUEL
                                LDX FUEL+1
                     ST
                                STA POINTH
                                STX POINTL
                     show velocity as absolute
LDA VEL
   006B A5 E5
   006D 30 06
                                BMI DOWN
   006F A5 E6
                                LDA VEL+1
   0071 F0 07
                                BEQ FLY
   0073 DO 05
0075 38
0076 A9 00
0078 E5 E6
007A 85 F9
                                BNE FLY
                     DOWN
                                SEC
                                LDA #$00
                                SEC VEL+1
                     FLY
                                STA INH
                     ;display the bird
   007C A9 02
007E 85 E1
0080 20 1F 1F Flite
0083 F0 06
0085 20 6A 1F
0088 20 91 00
                                LDA #$02
                                                     'suddenness' factor
                                STA DECK
                                JSR SCANDS
                                                                                                 energe
                                BEQ NOKEY
                                JSR GETKEY
                                JSR DOKEY
   008B C6 E1
                     NOKEY
                                DEC DECK
   008D DO F1
                                BNE FLITE
                                                                                    Sometimes
   008F FO DO
                                BEQ LINK
                     subroutine for reading keys
DOKEY CMP#$15 fue
   0091 09 15
                                                     fuel mode?
   0093 DO 03
                                BNE NALT
   0095 85 EE
                                STA MODE
   0097 60
                                RTS
   0098 C9 10
                                CMP #$10
                     NALT
                                                     altitude mode?
   009A DO 05
                                BNE NAL2
   009C A9 00
009E 85 EE
                                LDA #$00
                                STA MODE
   00A0 60
                     RET1
                                RTS
    00A1 10 FD
                                BPL RET1
                     NALZ
   00A3 AA
00A4 A5 EA
                                TAX
                                LDA THRUST
                                                     dead stick?
   00A6 FO F8
                                BEQ RET1
    00A8 86 EA
                                STX THRUST
   OOAA A5 EA
OOAC 38
                     THRSET
                                LDA THRUST
                                SEC
                                SBC #$05
STA TH2+1
   OOAD E9 05
   OOAF 85 E9
                                LDA #500
SEC #500
   00B1 A9 00
   00B3 E9 00
   OOB5 85 E8
                                 STA TH2
   00B7 60
                                 KTS
   00В8
                     INIT
                                 45/00/00//99/80/00//99/98//02//08/00/00//00
to 0005
                                 (height) (speed) (acc) (thr) (fuel)
```

PAGE 16

# FROM THE EDITOR:

I would like to clear up any misunderstanding there may be concerning the relationship between our <u>User Notes</u> and MOS Technology. This newsletter is being financed wholly by the subscribers. MOS was kind enough to print and mail the complementary issue so the newsletter could get started but we are self supporting now.

If you didn't get a particular application note or if you want your address changed on MOS Technology mailing list - please write to - KIM-1 Customer Support c/o MOS Technology 950 Rittenhouse Rd.
Norristown, Pa. 19401

Any correspondence concerning the <u>User Notes</u> should, of course, be addressed to: KIM-1 User Notes c/o Eric C. Rehnke 7656 Broadview Rd. #207 Parma, Ohio 44134

The subscription rate is \$5.00 for issues #1 thru #6 which includes 1st Class postage for U.S. and Canadian subscribers. Foreign subscribers should write for rates.

Payments should be made with check or money order in U.S. funds, no cash or purchase orders please.

# FOR YOUR INFORMATION:

Contact for course hardware etc., from Microprocessor Seminar: Joe Williams, School of Engineering, Materials Engineering Dept., Rensselaer Polytechnic Instituté, Troy, New York 12181.

Machine Language Programming for the 8008 and similiar microcomputers \$19.95: Scelbi Computer Consulting, Inc., 1322 Rear Boston Post Road, Dept. DJ. Milford Connecticut 06460.

From Robert G. Lloyd, 7554 Southgate Rd., Fayetteville, N. C. 28304:

Here is my program for THERE'S MORE TO BLINKING LIGHTS THAN MEETS THE EYE (January 76, BYTE, Page 52)

0300 A9 FF Caterpil LDA #\$FF 0302 8D 01 17 STA PADD Set PADD & PBDD to 0305 8D 03 17 STA PBDD OUTPUT 0308 38 SEC 0309 A9 OF Newmove LDA #\$OF 030B 8D 00 17 STA PAD Set march on I/O STA PBD output 030E 8D 02 17 TO APPLICATIONS 0311 A2 FF Loop 1 LDX #\$FF CONNECTOR 0313 AO 55 Loop 2 LDY #\$55 Set speed of bug 0315 88 DEY INSTALL ONE LED/RESISTOR ON EACH 0316 DO FD BNE LOOP 2 OF THE FOLLOWING APP. CONNECTOR 0318 CA DEX PINS IN THE FOLLOWING ORDER: 0319 DO F8 BNE LOOP 1 14,9,4,10,3,11,2,12,5,13,6,16, 7,15,8. (the first LED goes to 031B 2E 0A 03 ROL 031E 4C 09 03 JMP NEWMOVE pin 14, the second goes to 9, etc.)

```
OO E2. Uses OO E3, OO E4, and OO E5 to store calculated conversion factors for each of 16 binary bits. Length: 67 bytes. Conversion times: 0.7 millisec for hex 0000, 1.5 for hex 1111, 1.4 for hex 8080, 2.12 for hex FFFF. Times are proport—
ional to the number of binary 1 bits, not to the numerical value.
0200 F8
                     (sets decimal mode)
       98
                    (pushes Y, then X, index into stack)
       48
       84
       48
0205 A9 00
                    (zeroes 00 E0 to 00 E; in a loop)
      A2 06
                     (sets X-index for 6 operations) . (zero-page, X storing)
      95 DF
020C DO FB
      E6 E5
                    (increments 00 E5 to 01, to be first conversion factor)
0210 A5 E7
                     (accumulator pick-up of lo hex byte)
0212 48
                     (stored in stack)
      AO 08
                     (sets Y index for testing of 8 bits)
0215 68
                     (pulls hex byte from stack)
      4 A
                     (one logical shift right, lowest bit in carry)
      48
                     (stores shifted hex byte in stack)
0218 90 OC
                    (if carry clear, bit was a zero, skip to 0226)
      A2 03
18
                    (if not, do triple-precision add of conversion factor to the decimal locations)
021D B5 E2
      75 DF
95 DF
      CA
0224 DO F7
                    (next conversion factor always calculated, doubling previous factor by adding it to itself, giving sequence 1, 2, 4, 8,..... to final
0226 A2 03
      18
      B5 E2
                     65536 (not used))
      75 E2
      95 E2
      CA
0230 DO F7
      88
                    (DEY)
0233 DO EO
0235 68
                    (if not zero, back to 0215 for next bit)
                    (this PLA stack pull needed to equalize PHAs and PLAs)
A5 E3
0238 DO 04
                    (LDA highest conversion factor location)
                    (if not zero, job is finished, so exit)
      A5 E6
                    (if zero, load hi hex byte)
023C DO D4
                    (if not zero, back to 0212 for bit testing) (restore X, then Y, indexes)
023E 68
      AA
      68
      A8
0242 D8
0243 60
                    (clear decimal mode)
                    (RTS)
                                      ..................
```

From H. T. Gordon, Univ. of Calif., College of Agriculture, Berkeley, Calif. 94720
Listing of Third Version of HEDEC. Converts 4-digit hex number in OO E6
(hi byte) and OO E7 (lo byte) into decimal equivalent stored in OO E0, OO E1, and